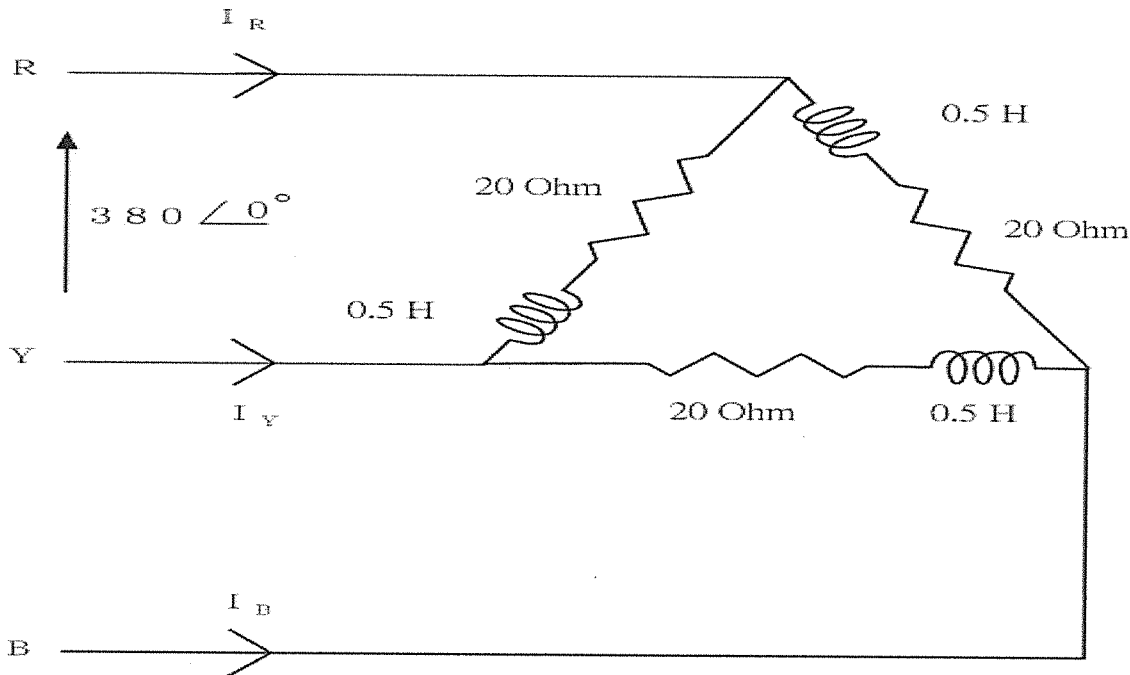


- Q1 Three identical loads each consists of a 20 Ohm resistance in series with a 0.5 Henry inductor are delta connected to a 380 V, 50 Hz, 3 phase supply. Calculate:
- The magnitude of the phase currents  $\uparrow \quad \downarrow V_L$
  - The magnitude of the line currents
  - The power taken from the supply



$$\text{Reactance of the load} = 2\pi fL = 2 \times \pi \times 50 \times 0.5 = j 157.1 \Omega \quad \checkmark$$

$$\text{Impedance of each load} = 20 + j 157.1 \Omega = 158.37 \angle 82.7^\circ \quad \checkmark$$

$$\text{i) Magnitude of phase current} = \frac{380}{158.37} = 2.399 \text{ A} \quad \frac{V_L}{Z}$$

$$\text{ii) Magnitude of Line current} = \sqrt{3} \times 2.399 = 4.155 \text{ A}$$

iii) Total three phase power

$$\begin{aligned} &= \sqrt{3} \times \text{Line Voltage} \times \text{Line Current} \times \text{Cos } \Phi \\ &= \sqrt{3} \times V_L \times I_L \times \text{Cos } \Phi \\ &= \sqrt{3} \times 380 \times 4.155 \times \text{Cos } \angle 82.7^\circ \\ &= 347.49 \text{ W.} \end{aligned}$$

**Q2** Calculate the line currents, neutral current and the total three phase power dissipation.

$L = 2\pi fL$ , the load impedances are:

$$Z_R = 30 + j 2 \times \pi \times 50 \times 0.1$$


$$= 30 + j 31.42 \Omega = 43.44 \angle 46^\circ$$

$$Z_Y = 30 + j 2 \times \pi \times 50 \times 0.15$$

$$= 30 + j 47.12 \Omega = 55.86 \angle 57.5^\circ$$

$$Z_B = 60 - j 1 / (2 \times \pi \times 50 \times 30 \times 10^{-6})$$
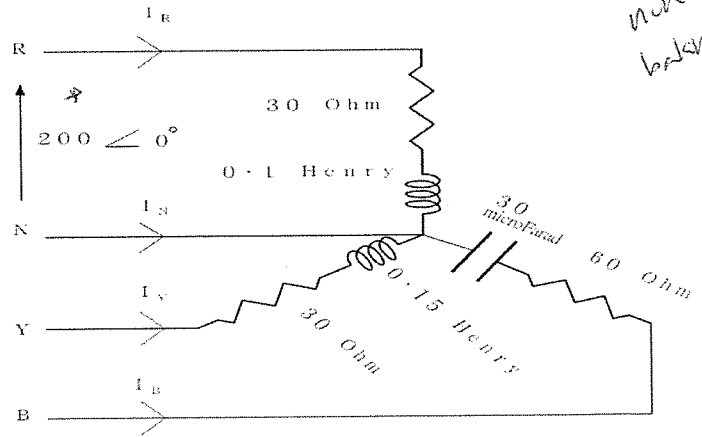
$$= 60 - j 106.1 \Omega = 121.89 \angle -60.5^\circ$$



non balanced

**Line current :**

$$I_R = \frac{200 \angle 0^\circ}{43.44 \angle 46^\circ} = 4.604 \angle -46^\circ A = 3.1982 - j3.3118 A$$


$$I_Y = \frac{200 \angle -120^\circ}{55.86 \angle 57.5^\circ} = 3.58 \angle -177^\circ A = -3.5751 - j0.1874 A$$

$$I_B = \frac{200 \angle 120^\circ}{121.89 \angle -60.5^\circ} = 1.6408 \angle 180.5^\circ A = -1.6407 - j0.0143 A$$

Neutral current :  $I_N = I_R + I_Y + I_B = -2.0176 - j 3.5135 = 4.0516 \angle -119.9^\circ A$

Total power =  $I_R^2 R_R + I_Y^2 R_Y + I_B^2 R_B = 4.604^2 \times 30 + 3.58^2 \times 30 + 1.6408^2 \times 60 = 1182W$   
 50Hz

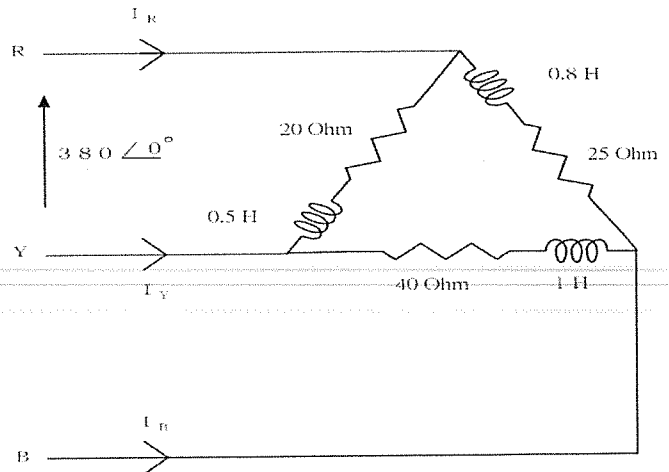- Q3** Find (i) The load impedance in each phase  
 (ii) The phase current  
 (iii) The line currents  
 (iv) The power dissipated in each phase



(i)  $L = 2\pi fL$ , the load impedances are:

$$Z_{RY} = 20 + j157.1 \Omega = 158.37 \angle 82.7^\circ$$

$$Z_{YB} = 40 + j314.1 \Omega = 316.64 \angle 82.8^\circ$$

$$Z_{BR} = 25 + j251.3 \Omega = 252.54 \angle 84.3^\circ$$

(ii) **Phase current :**  $I_{RY} = \frac{380 \angle 0^\circ}{158.37 \angle 82.3^\circ} = 2.399 \angle -82.7^\circ = 0.305 - j2.38 A$

$$I_{YB} = \frac{380 \angle -120^\circ}{316.64 \angle 82.8^\circ} = 1.2 \angle -202.7^\circ = -1.107 + j0.464 A$$

$$I_{BR} = \frac{380 \angle 120^\circ}{252.54 \angle 84.3^\circ} = 1.505 \angle 35.7^\circ = 1.222 + j0.878 A$$

(iii) **Line current :**  $I_R = I_{RY} - I_{YB} = 0.305 - j2.38 - (-1.107 + j0.464) = -0.917 - j3.258 = 3.385 \angle -105^\circ$

$$I_Y = I_{YB} - I_{BR} = -1.107 + j0.464 - (1.222 + j0.878) = -2.329 - j0.414 = 2.366 \angle 10.1^\circ$$

$$I_B = I_{BR} - I_{RY} = 1.222 + j0.878 - (0.305 - j2.38) = 0.917 + j3.258 = 3.385 \angle 105^\circ$$

(iv) **Power dissipated due to  $I_{RY} = 2.399^2 \times 20 = 115.1W$**

**Power dissipated due to  $I_{YB} = 1.2^2 \times 40 = 57.6W$**

**Power dissipated due to  $I_{RY} = 1.505^2 \times 25 = 56.25W$**