

MATERIALS

1. Function Generator / Oscilloscope
2. (1) 0.100 μ F Capacitor
3. (1) 220 Ω Resistor
4. Digital Multimeter (DMM)

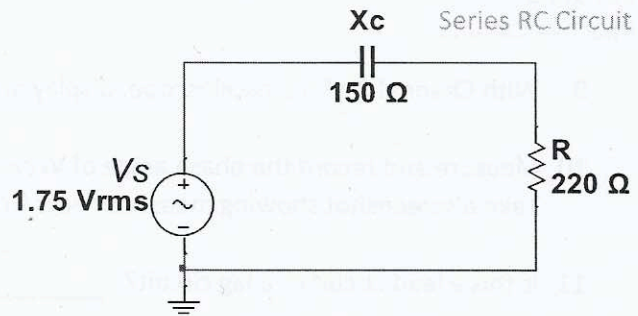


Figure 6-1

QUICK INITIAL SURVEY (SIMPLE VOLTAGE DIVIDER):

1. Given the circuit in **Figure 6-1** above, what do you expect the voltage drop to be across R using a voltage divider of the 'resistances'?

$V_R =$ 0.826 \angle 34.29 $^\circ$

2. What do you expect the voltage drop to be across C using a voltage divider of the 'resistances'?

$V_C =$ ~~0.924~~ 0.563 \angle -55.71 $^\circ$

3. Do you expect the sum of V_C and V_R to be 1.75 Vrms? yes

PROCEDURE

1. Construct the circuit above in Figure 6-1 on your breadboard using a 0.100 μ F Capacitor.
2. Using this capacitor, what frequency will cause $X_C = 150 \Omega$?

$f =$ ~~10.610 kHz~~ 10.610 kHz

3. Turn on the Function Generator/Oscilloscope and adjust the generated signal to 1.75 Vrms and the frequency calculated above.
4. Using the DMM, measure the voltage drop across R:

$V_R =$ 1.23 V

5. Using the DMM, measure the voltage across X_C :

$V_C =$ 0.845 V

6. How do these measured voltages compare to the 'expected' voltages in steps 1 and 2 above?

They don't match

7. Do the measured voltage drops equal the source voltage? _____

8. With Channel 1 of the oscilloscope, display the source voltage and measure it.

9. With Channel 2 of the oscilloscope, display and measure the voltage across the resistor.
10. Measure and record the phase angle of V_R (with respect to V_s)? _____
Take a screenshot showing measurements from steps 8 through 10.
11. Is this a lead circuit or a lag circuit? _____
12. Now, reverse the polarity of the source and again use Channel 1 to display the source voltage, but now use Channel 2 to display the capacitor voltage.
13. Again, measure V_s , V_C and θ . Record the phase angle of V_C ? _____
Take a screenshot.
14. Is this a lead circuit or a lag circuit? _____
15. Using the magnitudes and phases measured in Steps 9 and 10 and 13, then :

$$V_R = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}} = \underline{\hspace{2cm}} j \underline{\hspace{2cm}} V$$

$$V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}} = \underline{\hspace{2cm}} j \underline{\hspace{2cm}} V$$

Now add them:

$$\underline{\hspace{2cm}} j \underline{\hspace{2cm}} V$$

Is this equal to the source voltage? _____

16. What is the impedance of the circuit in Figure 6-1? $Z_T = \underline{\hspace{2cm}} j \underline{\hspace{2cm}} \Omega$
 $Z_T = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}} \Omega$
17. What is the current of the circuit in Figure 6-1? $I_T = \underline{\hspace{2cm}} j \underline{\hspace{2cm}} A$
 $I_T = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}} A$
18. Why does I_T have the same phase as V_R ? _____

19. What is V_{out} of the lead circuit?


$$V_{OUT} = V_R = I_T * R = \underline{\hspace{2cm}} + j \underline{\hspace{2cm}} V$$

20. What is V_{out} of the lag circuit?

$$V_{OUT} = V_C = I_T * X_C = \underline{\hspace{2cm}} - j \underline{\hspace{2cm}} V$$

21. In the circuit below, what is the relationship between the voltages of the resistor and capacitor?

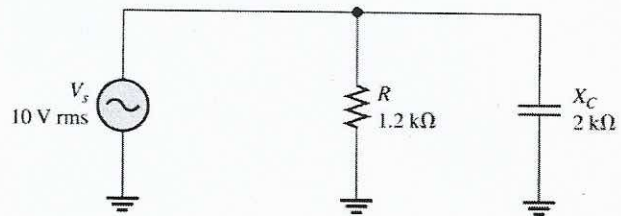- a) They have the same magnitude
- b) They have different magnitudes
- c) They have the same phase
- d) They have different phases



SUBMITTAL – Complete this handout and submit along with 2 screenshots.