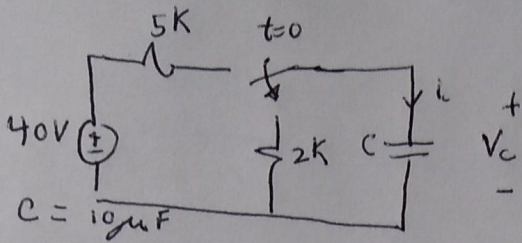



Show all models. Complete the table. Show work.

1]




	$t=0^-$	$t=0^+$	$t=\infty$
V_c			
i_c			

2]

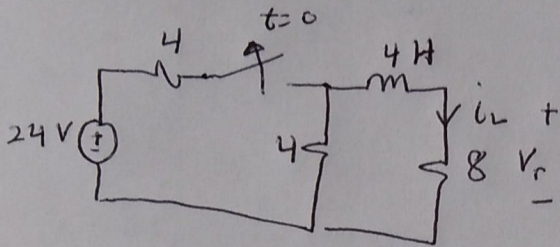


	$t=0^-$	$t=0^+$	$t=\infty$
i_L			
V_r			

3]

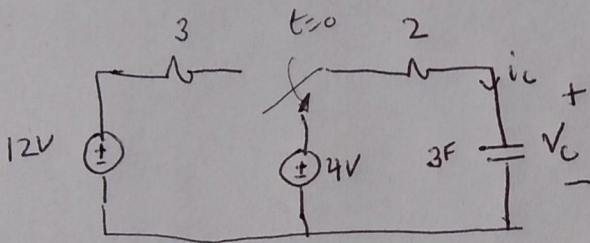


	$t=0^-$	$t=0^+$	$t=\infty$
V_c			
i_c			

4]

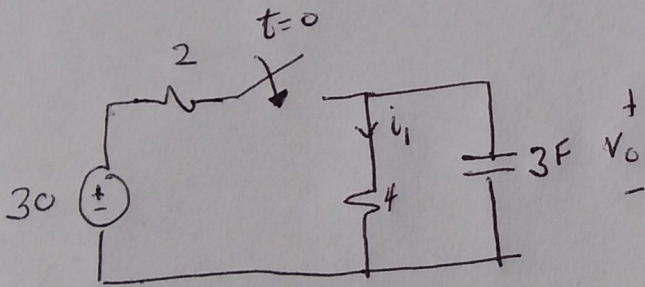

	$t=0^-$	$t=0^+$	$t=\infty$
V_c			
i_1			

5]

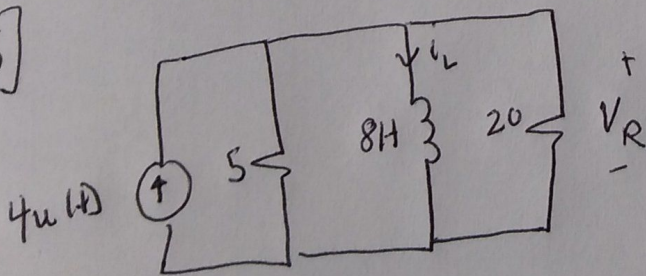

	$t=0^-$	$t=0^+$	$t=\infty$
i_L			
V_R			

Note the all circuits are in DCSS at $t=0^-$