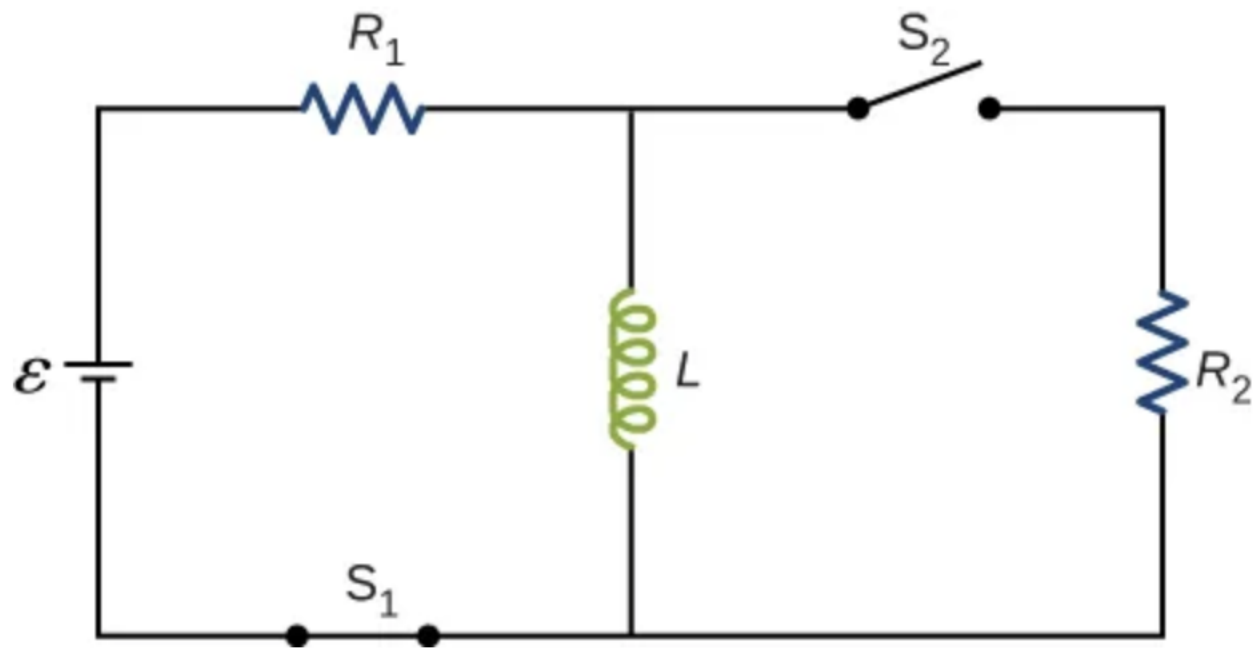


**29.** An emf of  $9.7 \times 10^{-3} \text{ V}$  is induced in a coil while the current in a nearby coil is decreasing at a rate of  $2.7 \text{ A/s}$ . What is the mutual inductance of the two coils?

**35.** An emf of  $0.40\text{ V}$  is induced across a coil when the current through it changes uniformly from  $0.10$  to  $0.60\text{ A}$  in  $0.30\text{ s}$ . What is the self-inductance of the coil?

**47.** Suppose that a rectangular toroid has 2000 windings and a self-inductance of 0.040 H. If  $h = 0.10$  m, what is the current flowing through a rectangular toroid when the energy in its magnetic field is  $2.0 \times 10^{-6}$  J?

**53.** For the circuit shown below,  $\mathcal{E} = 20 \text{ V}$ ,  $L = 4.0 \text{ mH}$ , and  $R = 5.0 \Omega$ . After steady state is reached with  $S_1$  closed and  $S_2$  open,  $S_2$  is closed and immediately thereafter (at  $t = 0$ )  $S_1$  is opened. Determine (a) the current through  $L$  at  $t = 0$ , (b) the current through  $L$  at  $t = 4.0 \times 10^{-4} \text{ s}$ , and (c) the voltages across  $L$  and  $R_1$  at  $t = 4.0 \times 10^{-4} \text{ s}$ .  $R_1 = R_2 = R$ .



**63.** The self-inductance and capacitance of an  $LC$  circuit are  $0.20\text{ mH}$  and  $5.0\text{ pF}$ . What is the angular frequency at which the circuit oscillates?

**71.** In an oscillating  $RLC$  circuit with  $L = 10 \text{ mH}$ ,  $C = 1.5 \mu\text{F}$ , and  $R = 2.0 \Omega$ , how much time elapses before the amplitude of the oscillations drops to half its initial value?