

---

# Physics for Scientists and Engineers II

Physics 202

Sample Exam #2

---

## Useful Information

Kirchhoff's Laws

$$\sum_i (\Delta V)_i = 0$$

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

Capacitors

$$C = \frac{Q}{\Delta V_C}$$

$$C = \frac{\epsilon_0 A}{d}$$

$$u_C = \frac{1}{2} C (\Delta V_C)^2$$

$$\frac{1}{C_{\text{eq}}} = \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \cdots \right) \quad \text{series circuit}$$

$$C_{\text{eq}} = C_1 + C_2 + C_3 + \cdots \quad \text{parallel circuit}$$

Resistors

$$\Delta V_R = IR$$

$$R = \frac{\rho L}{A}$$

$$P = I \Delta V_R = I^2 R = \frac{(\Delta V_R)^2}{R}$$

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \cdots \quad \text{series circuit}$$

$$\frac{1}{R_{\text{eq}}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \cdots \right) \quad \text{parallel circuit}$$

Constants


$$\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N m}^2$$

Name:

ID:

---

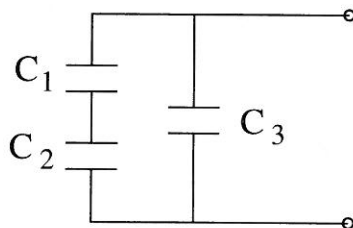1. Three capacitors of equal capacitance are arranged as shown. The voltage drop across  $C_1$  is 90.0 V. What is the voltage drops across  $C_2$  and  $C_3$ ?



Since the capacitors are equal and  $C_1$  and  $C_2$  are in series ( $Q_1 = Q_2$ ), then the voltage drops are equal.

$$\Rightarrow V_2 = \underline{\underline{90\text{ V}}}$$

Since  $C_3$  is in parallel with the combination of  $C_1$  and  $C_2$ , then the voltage drop equals  $V_1 + V_2$


$$\Rightarrow V_3 = V_1 + V_2 = \underline{\underline{180\text{ V}}}$$

Name:

ID:

---

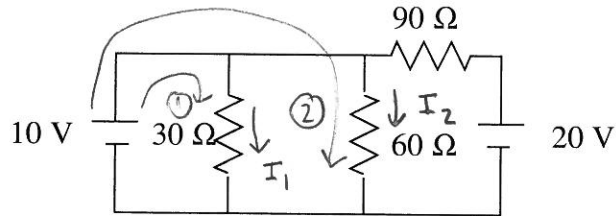2. What is the current through the  $30\ \Omega$  and  $60\ \Omega$  resistors in the circuit below?



For loop 1,

$$\sum (\Delta V) = 0$$

$$10\text{ V} - I_1 (30\ \Omega) = 0$$

$$I_1 = \frac{10\text{ V}}{30\ \Omega} = \underline{\underline{0.33\text{ A}}}$$

For loop 2,

$$\sum (\Delta V) = 0$$

$$10\text{ V} - I_2 (60\ \Omega) = 0$$

$$I_2 = \frac{10\text{ V}}{60\ \Omega} = \underline{\underline{0.17\text{ A}}}$$

Name:

ID:

---

3. A 1.0 m length of gold wire is connected to a 1.5 V battery, and a current of 2.0 mA flows through it. What is the diameter of the wire? (The resistivity of gold is  $2.24 \times 10^{-8} \Omega \cdot \text{m}$ .)

By Ohm's Law, the resistance is

$$R = \frac{V}{I} = \frac{1.5 \text{ V}}{0.002 \text{ A}} = 750 \Omega$$

The radius of the wire is

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$$

$$r = \sqrt{\frac{\rho L}{\pi R}}$$

$$= \sqrt{\frac{(2.24 \times 10^{-8} \Omega \cdot \text{m})(1.0 \text{ m})}{\pi (750 \Omega)}}$$

$$= 3.08 \times 10^{-6} \text{ m}$$


Thus, the diameter is

$$d = 2r = \underline{\underline{6.2 \times 10^{-6} \text{ m}}} = \underline{\underline{6.2 \mu\text{m}}}$$

Name:

ID:

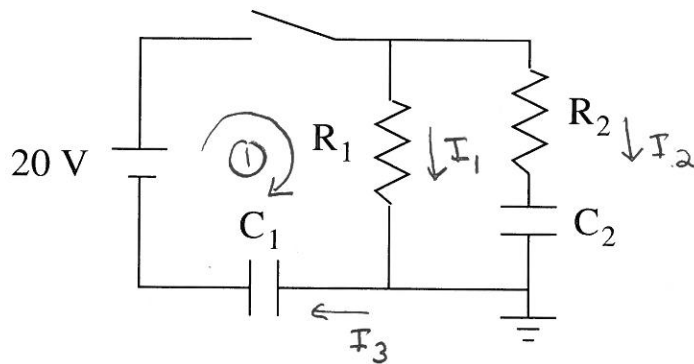4. For the circuit below,  $R_1 = 120 \Omega$ ,  $R_2 = 300 \Omega$ ,  $C_1 = 25 \text{ pF}$ , and  $C_2 = 40 \text{ pF}$ . All the capacitors are initially uncharged. What is the power dissipated by  $R_1$ , (a) just after the switch is closed and (b) when the switch was been closed for a very long time?



A single ground does not affect the operation of the circuit.

a) For loop 1 just after the switch is closed,

$$\sum (V) = 0$$

$$\mathcal{E} - I_1 R_1 - \frac{Q_1}{C_1} = 0$$

$$I_1 = \frac{\mathcal{E}}{R_1} = \frac{20 \text{ V}}{120 \Omega} = 0.167 \text{ A}$$

Thus, the power dissipated by  $R_1$  is

$$P = I_1^2 R_1 = (0.167 \text{ A})^2 (120 \Omega) = \underline{\underline{3.3 \text{ W}}}$$

b) when  $C_1$  and  $C_2$  are fully charged,  $I_2 = I_3 = 0$

By the junction law

$$I_1 + I_2 = I_3 \Rightarrow I_1 = 0$$

Thus, the power dissipated by  $R_1$  is

$$P = I_1^2 R_1 = \underline{\underline{0 \text{ W}}}$$