

* The Experiment

~~30V~~
~~1000Ω~~
~~10000Ω~~
~~30kΩ~~

The balanced bridge

$$R_{app} = 5k\Omega$$

V	R_v	E_{RW}
* 30V	$3k\Omega$ 5	800Ω
* 10V	5kΩ 4700Ω	300Ω
* 3V	4700Ω	1800Ω
* 1V	4700Ω	50Ω
* 0.3V	4730Ω	10Ω
* 0.1V	4730Ω	2Ω
* 0.03V	4718Ω	1Ω
* 0.01V	4718.5Ω	0.4Ω
* 0.003V	4718.6Ω	0.1Ω
* 0.0001V	4718.6Ω 4720Ω	0.05Ω

Bridge Sensitivity

49 V_Δ

$R_V (\Omega)$	$V (v)$
4720.2	
4720.6	-1.8
4721.0	0.8
4721.4	-0.6 ± 2
4721.8	-0.4 ± 2
4722.2	-0.2 ± 2
4722.6	0
4723.0	0.8
4723.4	0.3 ± 6
4723.8	0.5 ± 6
4724.2	0.7 ± 4
	0.9 ± 6

$V (v)$	$R_V (\Omega)$	$E_{R_V} (\Omega)$
30	5000	1000
10	5000	300
3	4700	100
1	4700	30
0.3	4700	4
0.1	4708	2
0.03	4708	1
0.01	4707.6	0.2
0.003	4707.7	0.1
0.001	4707.7	

2

Bridge Sensitivity

$R_v (\Omega)$	$V (v)$
4715.0	-0.26
4715.5	-0.78
4716.0	-0.52
4716.5	-0.26
4717.0	-0.18
4717.5	0
4718.0	0.16
4718.5	0.32
4719.0	0.48
4719.5	0.66
4720.0	0.84


Dynamic bridge


$R_v (\Omega)$	$V (v)$
4727.0	-0.70
4727.3	-0.56
4727.6	-0.40
4727.9	-0.26
4728.2	-0.12
4728.5	0
4728.8	0.18
4729.1	0.32
4729.4	0.46
4729.7	0.60
4730.0	0.76

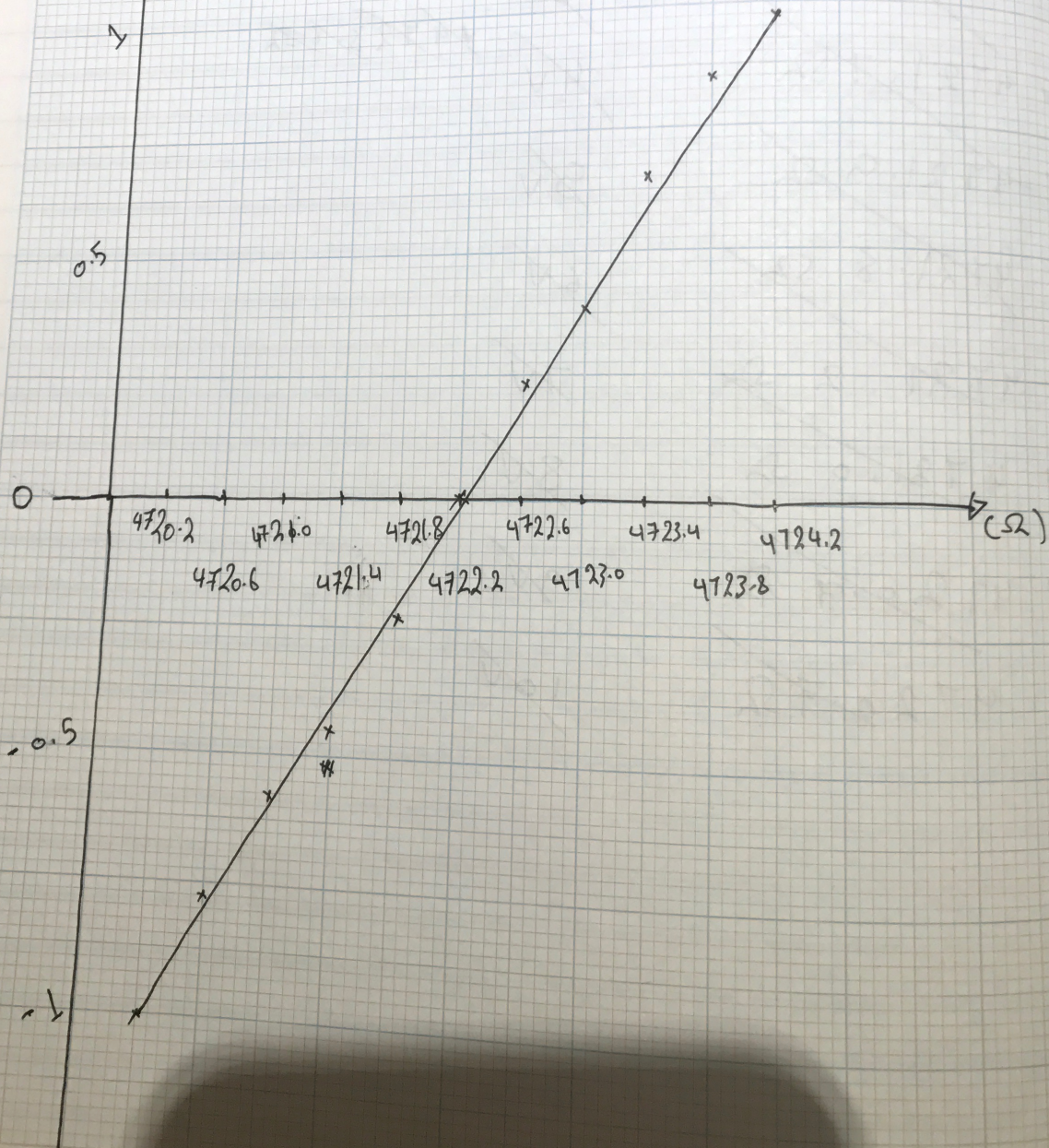
(3)

$$S = \frac{\Delta V_{1,2}}{\Delta R} \quad \text{V}\Omega^{-1}$$


$$S = \frac{0.96 - (-1.00)}{4724.2 - 4720.2} = \frac{1.96}{4} = 0.49 \text{ V}\Omega^{-1}$$



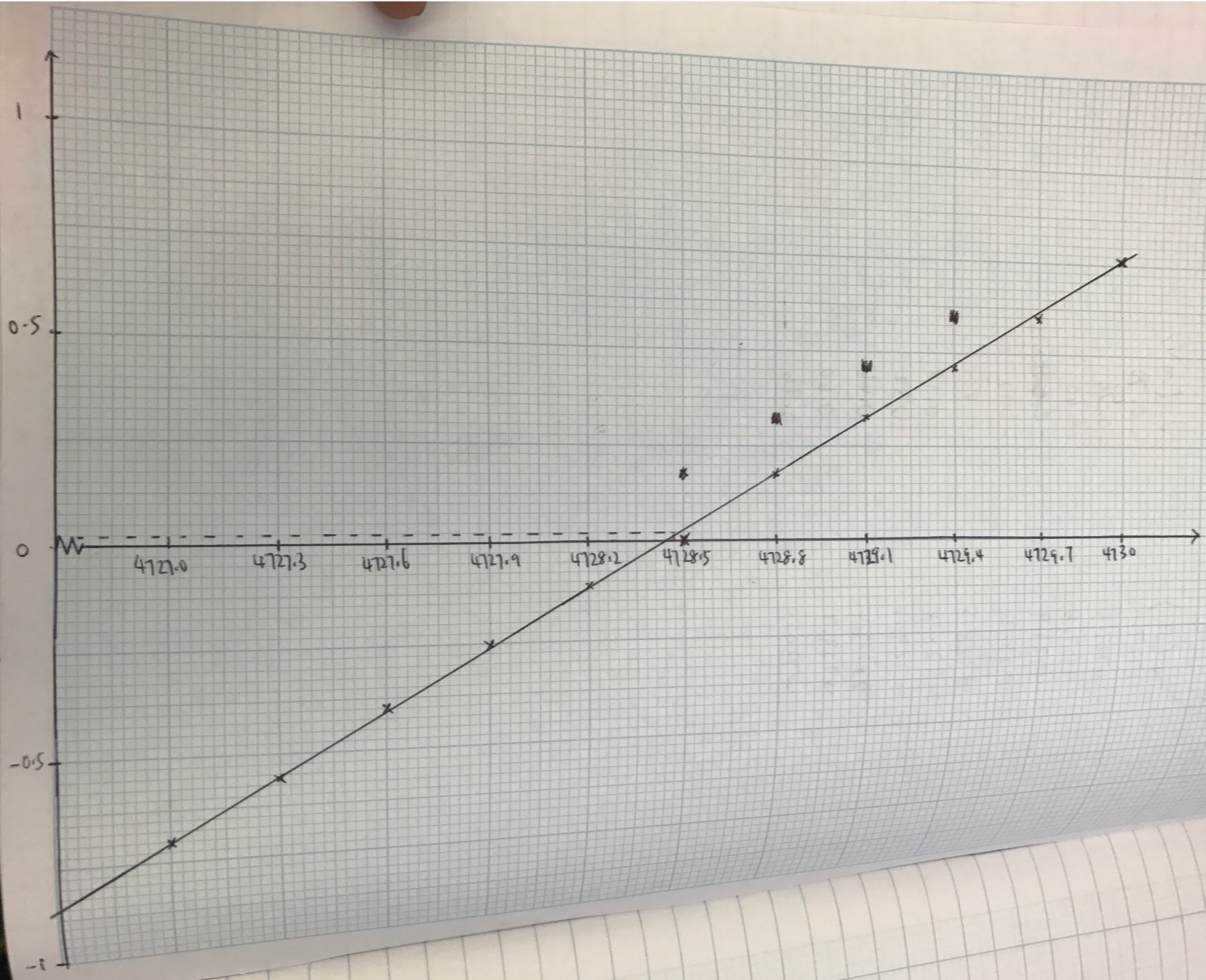

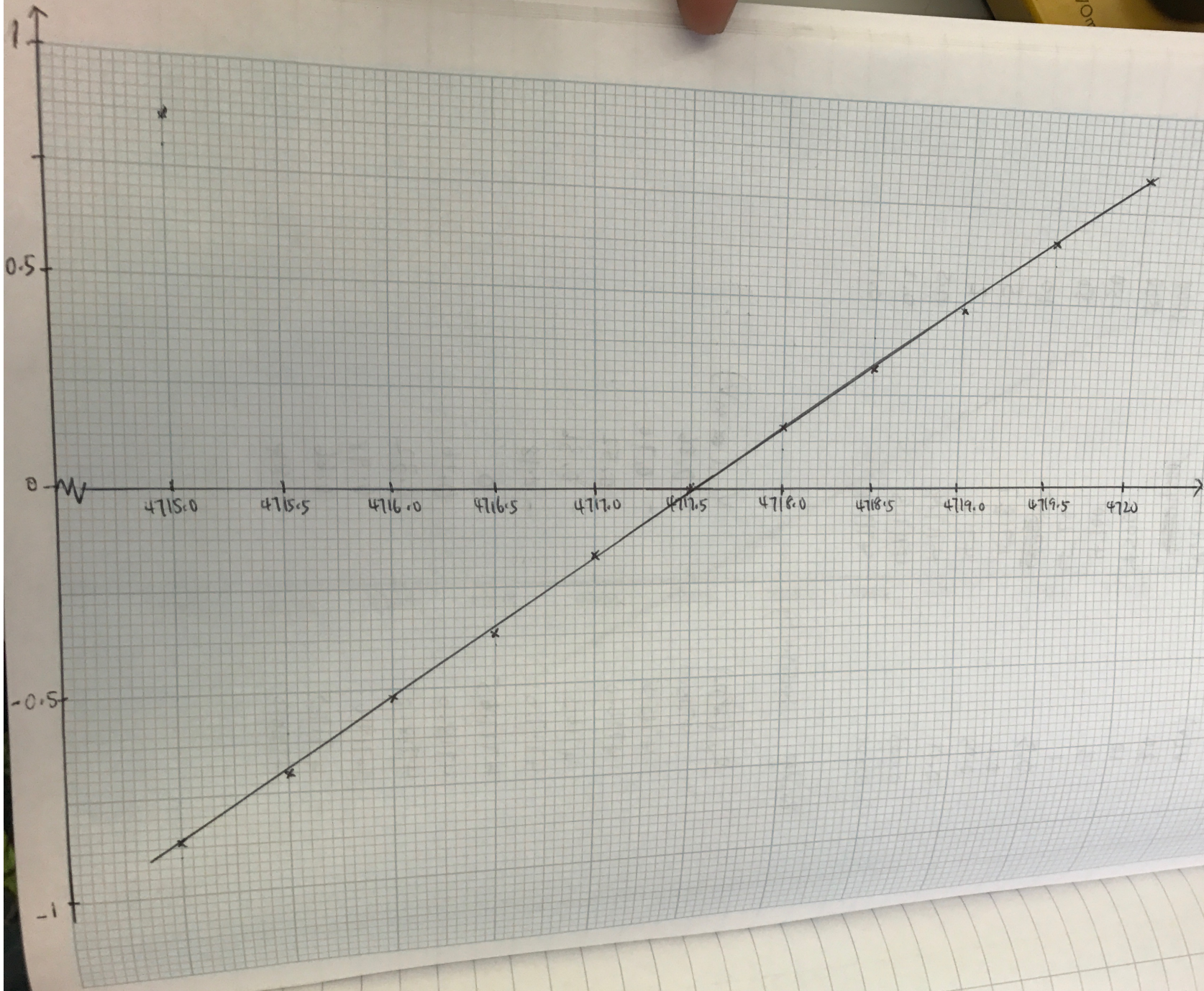

Dynam
Bridge

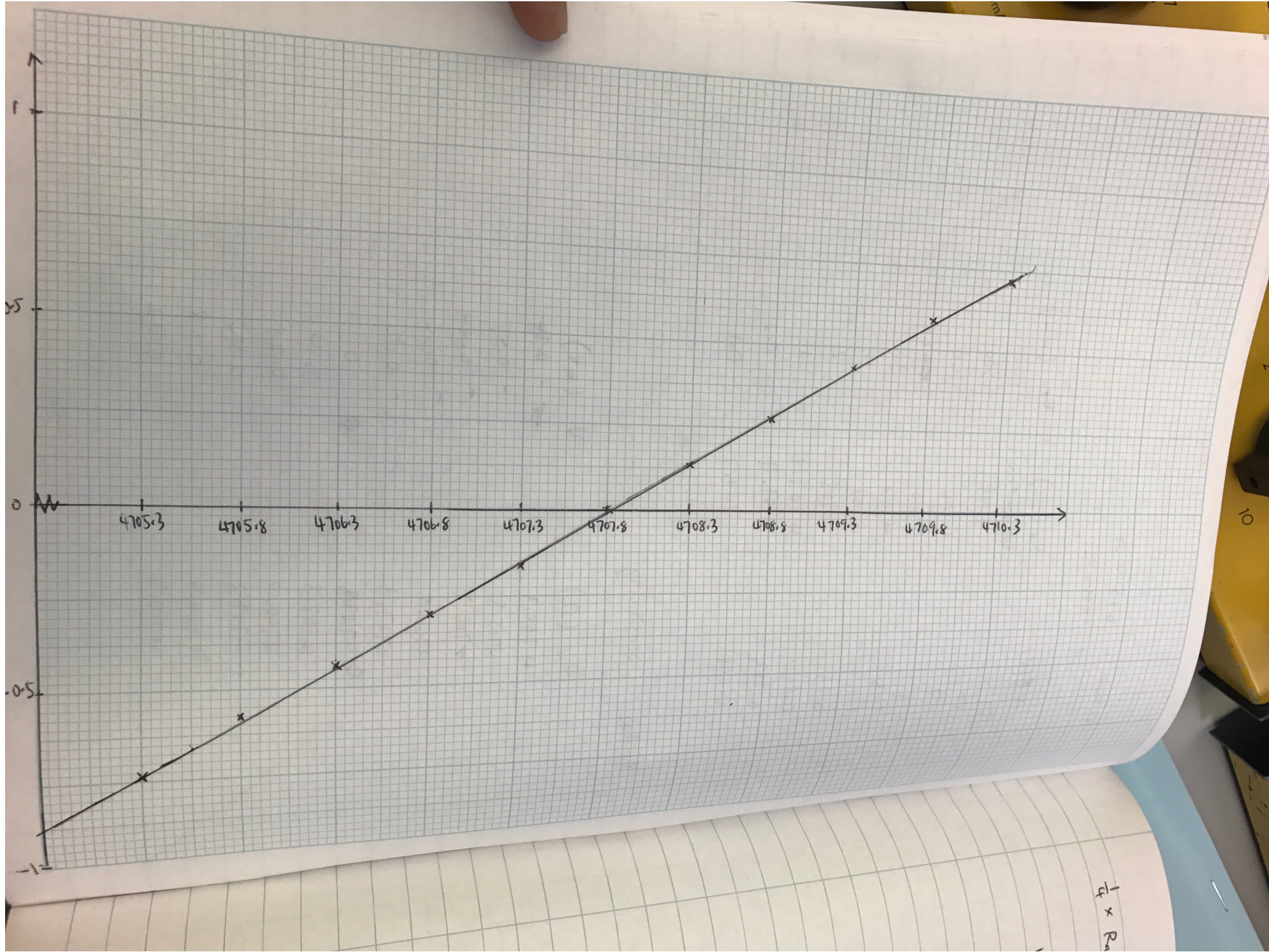

$f \times R_n$