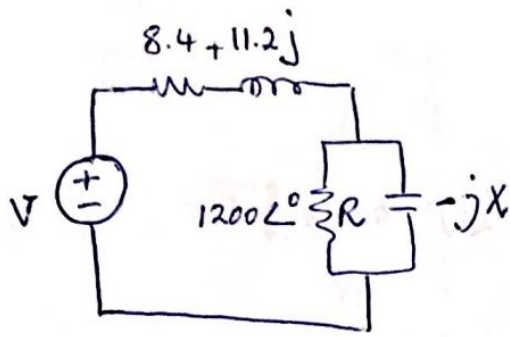


Tut. 1 / 3 phase - Power factor

Q1



$$P_R = VI \Rightarrow 30 \text{ kVA} = 1200 \angle 0^\circ \times I$$

$$\Rightarrow I = \frac{30 \times 1000}{1200 \angle 0^\circ} = 25$$

$$\cos \theta = 0.8 \Rightarrow \theta = \tan^{-1}(0.8) = 36.8^\circ$$

$$\text{Distribution line impedance} = Z_d = 8.4 + 11.2j = 14 \angle 53.1301^\circ$$

$$\Rightarrow \text{voltage drop: } V_d = Z_d \times I = 14 \angle 53.1301^\circ \times 25 \angle 36.8^\circ = 350 \angle 90^\circ$$

$$\boxed{V_d = j350}$$


$$\text{Now, } V_s = V_d + V_L = 350 \angle 90^\circ + 1200 \angle 0^\circ = 1200 + j350$$

$$\boxed{V_s = 1250 \angle 16.26^\circ}$$

$$Z_L = \frac{V_L}{I_L} = \frac{1200 \angle 0^\circ}{25 \angle 36.8^\circ} = 48 \angle -36.8^\circ = 29.87 + j37.57$$

$$Z_L = R + jX$$

Q2/

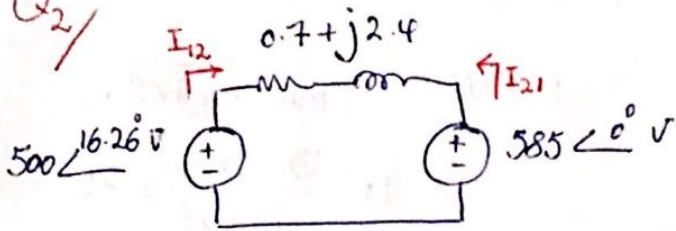

$$V_1 = 500 \cos(16.26) + j 500 \sin(16.26) = 480 + j 140$$

$$V_2 = 585 + j0$$

$$Z = 0.7 + j 2.4 = 2.5 \angle 73.74^\circ$$

$$\text{now, } I_{12} = \frac{V_1 - V_2}{Z} = \frac{480 + j140 - 585}{2.5 \angle 73.74^\circ} = \frac{-105 + j140}{2.5 \angle 73.74^\circ} = \frac{175 \angle 126.8}{2.5 \angle 73.74}$$

$$\Rightarrow I_{12} = 70 \angle -53.06^\circ$$

$$S_1 = V_1 \cdot I_{12}^* = 500 \angle 16.26 \times 70 \angle -53.06 = 35000 \angle -36.8$$

$$\Rightarrow S_1 = \boxed{28 - j 21}$$

↑ ↑
KW KVAR

$$I_{21} = -I_{12} = 70 \angle -126.88$$

$$S_2 = V_2 \cdot I_{21}^* = 585 \angle 0 \times 70 \angle +126.88 = 40950 \angle +126.88$$


$$S_2 = \boxed{-24.5 + j 32.7}$$

↑ ↑
KW KVAR

$$\text{Line losse} = R I^2 = 0.7 \times (70)^2 = 3430 \text{ W} = 3.4 \text{ kW}$$

Conclusion: Mach 2 + line losses = Mach 1 output

Q3/

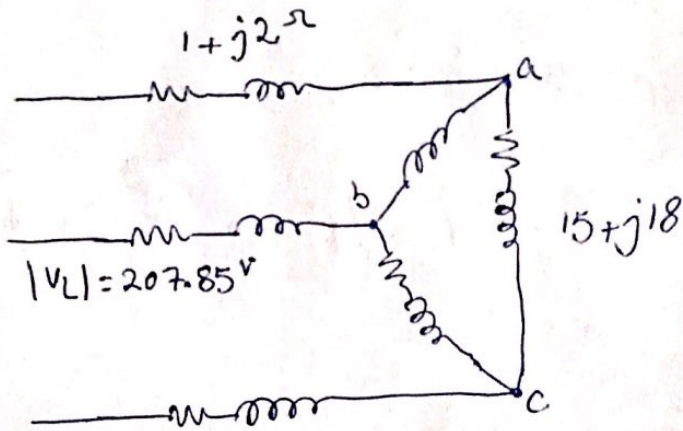

Step 1: Convert to single phase

Step 2: Convert delta to star load

Star equivalent for star load = $\frac{1}{3}$ (delta load)

$$= \frac{1}{3} (15 + j18) = 5 + j6$$

Step 3: Single-phase eq. ckt.

$$Z_{ph} = 1 + j2 + 5 + j6 = 6 + j8 = 10 \angle 53.13^\circ$$

$$V_{L-L} = 207.85 \rightarrow V_{ph} = \frac{V_{L-L}}{\sqrt{3}} = \frac{207.85}{\sqrt{3}} \approx 120 \text{ V}$$

$$\rightarrow \text{Line current: } I_L = \frac{V_{ph}}{Z_{ph}} = \frac{120}{10 \angle 53.13} = 12 \angle -53.13^\circ$$

$$S_{3-ph} = 3 V_{ph} \cdot I_{ph}^* = 3 \times 120 \times 12 \angle 53.13 = 2592 + j3456$$

phase voltage at load = Supply - line drop

$$\text{Line drop} = (1 + j2) (12 \angle -53.13) = 2.24 \angle 63.435^\circ \times 12 \angle -53.13$$

$$\text{Line drop} = 26.88 \angle 10.3$$

now, phase voltage at load = $120 - 26.88 \angle 10.3$

$$\Rightarrow 93.55 - j4.8$$

$$\text{line voltage at load} = \sqrt{3} \times V_{ph} = \sqrt{3} \times \sqrt{(93.55)^2 + (4.8)^2} = \underline{\underline{162.24^V}}$$