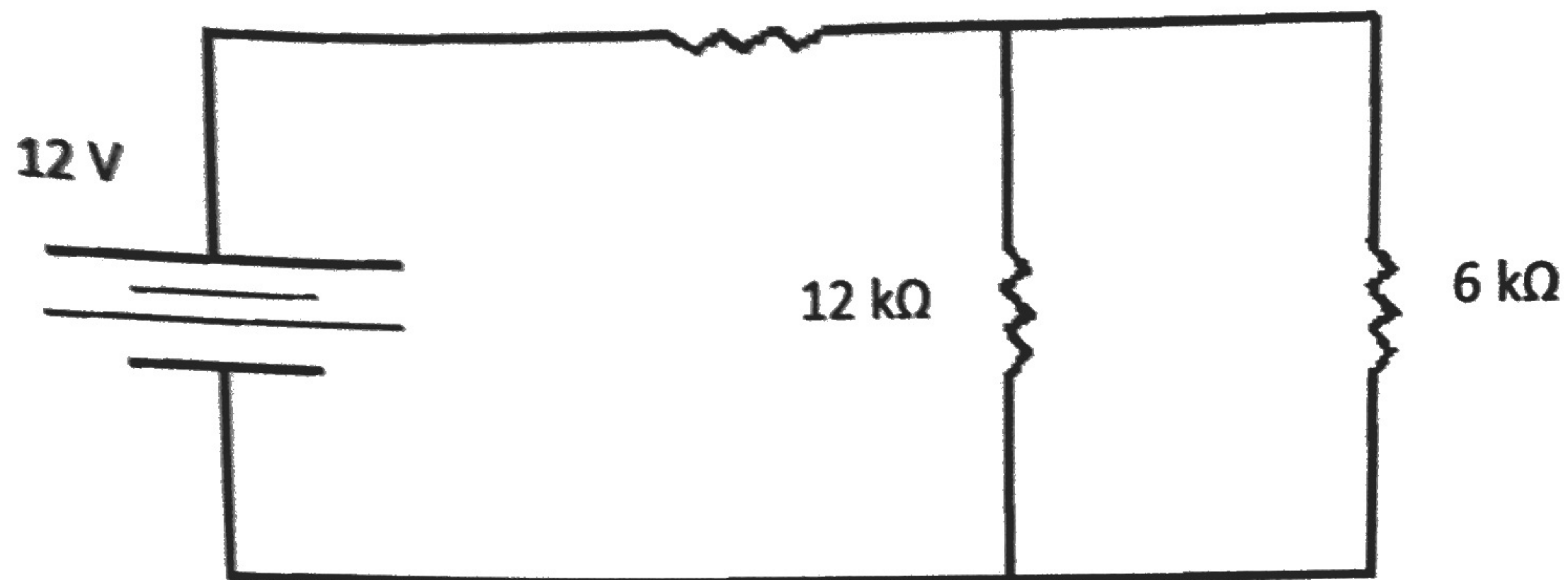




7. What theoretical current would you measure in an open circuit? In a short circuit?