

Answers to Self-Reviews

- 6-1 a. $1\text{ k}\Omega$
 b. $0.5\text{ k}\Omega$
 c. $1.5\text{ k}\Omega$

- 6-2 a. 12 V
 b. 6 A
 c. 18 V

- 6-3 a. 40 V
 b. 8 A
 c. 4 V

- 6-4 a. R_1
 b. R_4
 c. R_6

- 6-5 a. R_3
 b. R_1
 c. 4 A
 d. 60 V

- 6-6 a. A and B are input; C and D are output.
 b. Zero
 c. $71.35\ \Omega$
 d. $99.99\ \Omega$
 e. $500\ \Omega$

- 6-7 a. 10 A
 b. 1.1 A
 c. 12 V
 d. 0 V

Laboratory Application Assignment

In this lab application assignment you will examine the characteristics of a simple series-parallel circuit. You will also troubleshoot a series-parallel circuit containing both shorts and opens.

Equipment: Obtain the following items from your instructor.

- Variable dc power supply
- Assortment of carbon-film resistors
- DMM

Series-Parallel Circuit Characteristics

Examine the series-parallel circuit in Fig. 6-50. Calculate and record the following values:

$$R_T = \underline{\hspace{2cm}}, I_T = \underline{\hspace{2cm}}, V_1 = \underline{\hspace{2cm}}, V_2 = \underline{\hspace{2cm}},$$

$$V_3 = \underline{\hspace{2cm}}, V_4 = \underline{\hspace{2cm}},$$

$$V_{AB} = \underline{\hspace{2cm}}, I_2 = \underline{\hspace{2cm}}, I_3 = \underline{\hspace{2cm}}$$

Construct the series-parallel circuit in Fig. 6-50. Measure and record the following values. (Note that the power supply connections must be removed to measure R_T .)

$$R_T = \underline{\hspace{2cm}}, I_T = \underline{\hspace{2cm}}, V_1 = \underline{\hspace{2cm}}, V_2 = \underline{\hspace{2cm}},$$

$$V_3 = \underline{\hspace{2cm}}, V_4 = \underline{\hspace{2cm}},$$

$$V_{AB} = \underline{\hspace{2cm}}, I_2 = \underline{\hspace{2cm}}, I_3 = \underline{\hspace{2cm}}$$

In Fig. 6-50, identify which components are in series and which components are in parallel. _____

Do your measured values of voltage and current support your answers? _____

Does the current entering point B equal the current leaving point A? _____

Figure 6-50

