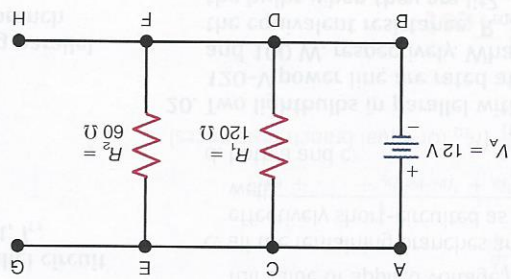


SECTION 5-1 THE APPLIED VOLTAGE V_A IS THE SAME ACROSS PARALLEL BRANCHES

5-1 **Multisim** In Fig. 5-19, how much voltage is across points

- a. A and B?
- b. C and D?
- c. E and F?
- d. G and H?

Figure 5-19



5-2 In Fig. 5-19, how much voltage is across

- a. the terminals of the voltage source?

- b. R_1 ?
- c. R_2 ?

5-3 In Fig. 5-19, how much voltage will be measured across points C and D if R_1 is removed from the circuit?

SECTION 5-2 EACH BRANCH / EQUALS V_A/R

5-4 In Fig. 5-19, solve for the branch currents, I_1 and I_2 .


5-5 In Fig. 5-19, explain why I_2 is double the value of I_1 .

5-6 In Fig. 5-19, assume a $10\text{-}\Omega$ resistor, R_3 , is added across

- a. Calculate the branch current, I_3 .
- b. Explain how the branch currents, I_1 and I_2 are affected by the addition of R_3 .

5-7 In Fig. 5-20, solve for the branch currents I_1 , I_2 , and I_3 .

Figure 5-20

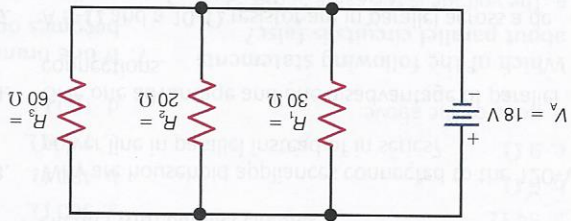

5-8 In Fig. 5-20, do the branch currents I_1 and I_3 remain the same if R_2 is removed from the circuit? Explain your answer.

- a. A and B?
- b. B and C?
- c. C and D?
- d. E and F?
- e. F and G?
- f. G and H?

5-18 In Fig. 5-22, how much is the current in the wire between

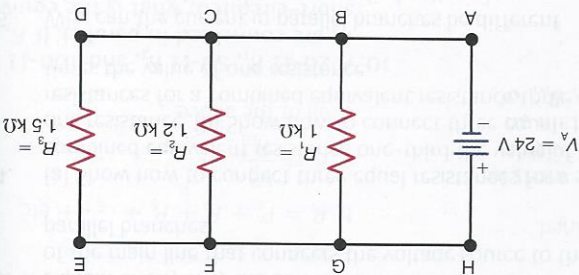


Figure 5-22

5-17 In Fig. 5-22, solve for I_1 , I_2 , I_3 , and I_T .

5-16 In Fig. 5-21, re-solve for the total current, I_T , if V_A is reduced to 51 V.

5-15 In Fig. 5-21, solve for the total current, I_T .

5-14 In Fig. 5-20, re-solve for the total current, I_T , if R_2 is removed from the circuit.

5-13 In Fig. 5-20, solve for the total current, I_T .

5-12 **Multisim** In Fig. 5-19 re-solve for the total current, I_T , if a $10\text{-}\Omega$ resistor, R_3 , is added across points G and H.

5-11 **Multisim** In Fig. 5-19, solve for the total current, I_T .

SECTION 5-3 KIRCHHOFF'S CURRENT LAW (KCL)

5-10 Recalculate the values for I_1 , I_2 , I_3 , and I_4 in Fig. 5-21 if the applied voltage, V_A , is reduced to 51V.

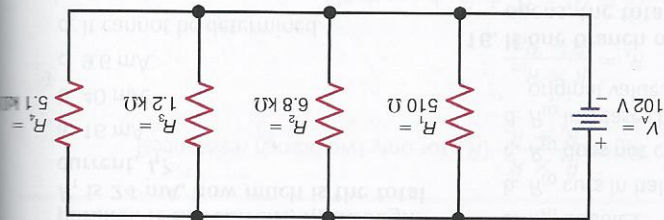


Figure 5-21

5-9 In Fig. 5-21, solve for the branch currents I_1 , I_2 , I_3 , and I_4 .