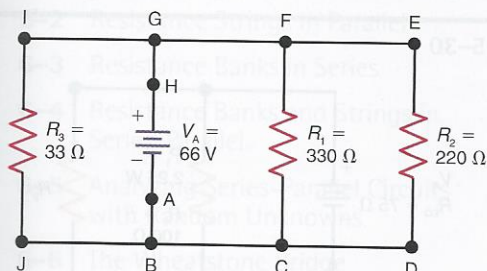


- 5-19 In Fig. 5-22 assume that a $100\text{-}\Omega$ resistor, R_4 , is added to the right of resistor, R_3 . How much is the current in the wire between points
- A and B?
 - B and C?
 - C and D?
 - E and F?
 - F and G?
 - G and H?

5-20 In Fig. 5-23, solve for I_1 , I_2 , I_3 , and I_T .


Figure 5-23



- 5-21 In Fig. 5-23, how much is the current in the wire between points
- A and B?
 - B and C?
 - C and D?
 - E and F?
 - F and G?
 - G and H?
 - G and I?
 - B and J?

5-22 In Fig. 5-24, apply Kirchoff's current law to solve for the unknown current, I_3 .

Figure 5-24

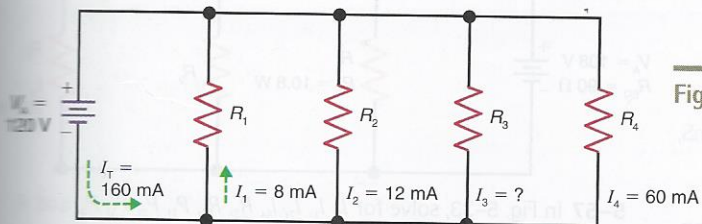

- 5-23 Two resistors R_1 and R_2 are in parallel with each other and a dc voltage source. How much is I_2 through R_2 if $I_T = 150\text{ mA}$ and I_1 through R_1 is 60 mA ?

SECTION 5-4 RESISTANCES IN PARALLEL

5-24 In Fig. 5-19, solve for R_{EQ} .

5-25 In Fig. 5-19, re-solve for R_{EQ} if a $10\text{-}\Omega$ resistor, R_3 is added across points G and H.

5-26 In Fig. 5-20, solve for R_{EQ} .

5-27 In Fig. 5-20, re-solve for R_{EQ} if R_2 is removed from the circuit.

5-28 In Fig. 5-21, solve for R_{EQ} .

5-29 In Fig. 5-21, re-solve for R_{EQ} if V_A is reduced to 51 V .


5-30 In Fig. 5-22, solve for R_{EQ} .

5-31 In Fig. 5-23, solve for R_{EQ} .

5-32 In Fig. 5-24, solve for R_{EQ} .

5-33 **MultiSim** In Fig. 5-25, how much is R_{EQ} if $R_1 = 100\text{ }\Omega$ and $R_2 = 25\text{ }\Omega$?

Figure 5-25

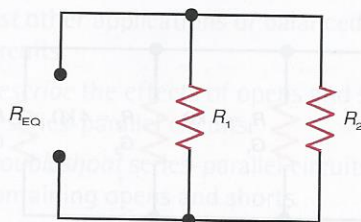

5-34 **MultiSim** In Fig. 5-25, how much is R_{EQ} if $R_1 = 1.5\text{ M}\Omega$ and $R_2 = 1\text{ M}\Omega$?

5-35 **MultiSim** In Fig. 5-25, how much is R_{EQ} if $R_1 = 2.2\text{ k}\Omega$ and $R_2 = 220\text{ }\Omega$?


5-36 In Fig. 5-25, how much is R_{EQ} if $R_1 = R_2 = 10\text{ k}\Omega$?

5-37 In Fig. 5-25, how much resistance, R_2 , must be connected in parallel with a $750\text{ }\Omega$ R_1 to obtain an R_{EQ} of $500\text{ }\Omega$?

5-38 In Fig. 5-25, how much resistance, R_1 , must be connected in parallel with a $6.8\text{ k}\Omega$ R_2 to obtain an R_{EQ} of $1.02\text{ k}\Omega$?

5-39 How much is R_{EQ} in Fig. 5-26 if $R_1 = 1\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$, $R_3 = 200\text{ }\Omega$, and $R_4 = 240\text{ }\Omega$?

Figure 5-26

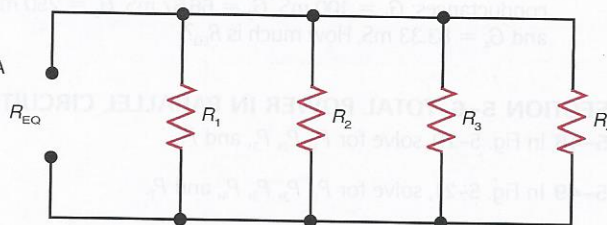

5-40 How much is R_{EQ} in Fig. 5-26 if $R_1 = 5.6\text{ k}\Omega$, $R_2 = 4.7\text{ k}\Omega$, $R_3 = 8.2\text{ k}\Omega$, and $R_4 = 2.7\text{ k}\Omega$?

5-41 **MultiSim** How much is R_{EQ} in Fig. 5-26 if $R_1 = 1.5\text{ k}\Omega$, $R_2 = 1\text{ k}\Omega$, $R_3 = 1.8\text{ k}\Omega$, and $R_4 = 150\text{ }\Omega$?