

Figure 5-33

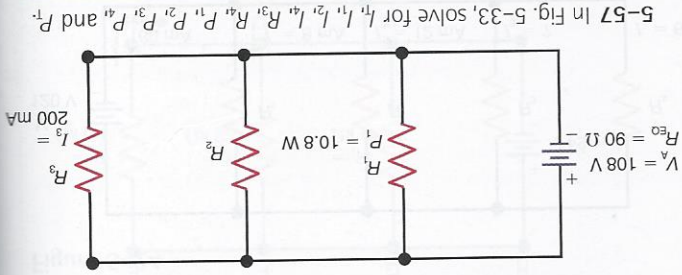


Figure 5-32

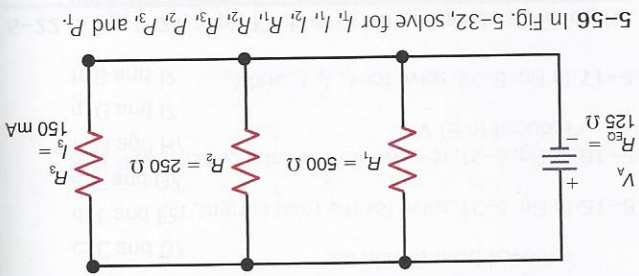


Figure 5-31

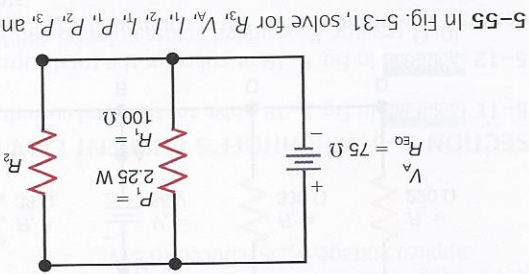


Figure 5-30

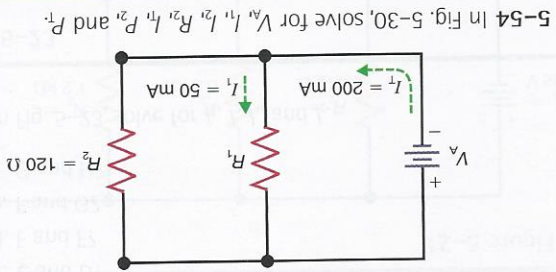


Figure 5-29

**SECTION 5-7 ANALYZING PARALLEL CIRCUITS WITH RANDOM UNKNOWN**

5-53 In Fig. 5-29, solve for  $V_A$ ,  $R_1$ ,  $I_2$ ,  $R_{eq}$ ,  $P_1$ ,  $P_2$ , and  $P_T$ .

5-54 In Fig. 5-30, solve for  $V_A$ ,  $I_1$ ,  $I_2$ ,  $R_2$ ,  $I_3$ ,  $P_1$ ,  $P_2$ , and  $P_T$ .

5-55 In Fig. 5-31, solve for  $R_3$ ,  $V_A$ ,  $I_1$ ,  $I_2$ ,  $I_3$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .

5-56 In Fig. 5-32, solve for  $I_1$ ,  $I_2$ ,  $I_3$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .

5-57 In Fig. 5-33, solve for  $I_1$ ,  $I_2$ ,  $I_3$ ,  $I_4$ ,  $R_4$ ,  $R_3$ ,  $R_2$ ,  $R_1$ ,  $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_4$ , and  $P_T$ .

**SECTION 5-5 CONDUCTANCES IN PARALLEL**

5-44 In Fig. 5-27, solve for  $G_1$ ,  $G_2$ ,  $G_3$ ,  $G_4$ ,  $G_T$ , and  $R_{eq}$ .

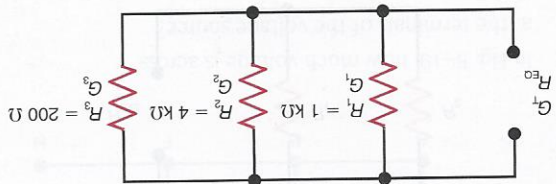


Figure 5-27

5-45 In Fig. 5-28, solve for  $G_1$ ,  $G_2$ ,  $G_3$ ,  $G_4$ ,  $G_T$ , and  $R_{eq}$ .

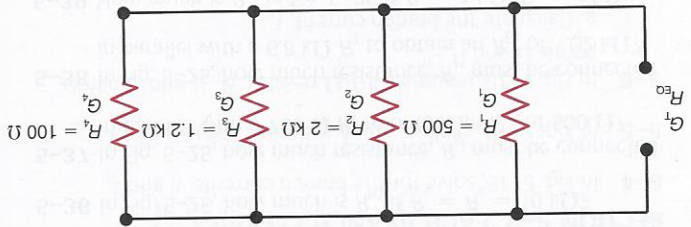


Figure 5-28

5-46 Find the total conductance,  $G_T$  for the following branch conductances;  $G_1 = 1 \text{ mS}$ ,  $G_2 = 200 \text{ } \mu\text{S}$ , and  $G_3 = 1.8 \text{ mS}$ . How much is  $R_{eq}$ ?

5-47 Find the total conductance,  $G_T$  for the following branch conductances;  $G_1 = 100 \text{ mS}$ ,  $G_2 = 66.67 \text{ mS}$ ,  $G_3 = 250 \text{ mS}$ , and  $G_4 = 83.33 \text{ mS}$ . How much is  $R_{eq}$ ?

**SECTION 5-6 TOTAL POWER IN PARALLEL CIRCUITS**

5-48 In Fig. 5-20, solve for  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .

5-49 In Fig. 5-21, solve for  $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_4$ , and  $P_T$ .

5-50 In Fig. 5-22, solve for  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .

5-51 In Fig. 5-23, solve for  $P_1$ ,  $P_2$ ,  $P_3$ , and  $P_T$ .

5-52 In Fig. 5-24, solve for  $P_1$ ,  $P_2$ ,  $P_3$ ,  $P_4$ , and  $P_T$ .

5-42 How much is  $R_{eq}$  in Fig. 5-26 if  $R_1 = R_2 = R_3 = R_4 = 2.2 \text{ k}\Omega$ ?

5-43 A technician is using an ohmmeter to measure a variety of different resistor values. Assume the technician has a body resistance of  $750 \text{ k}\Omega$ . How much resistance will the ohmmeter read if the fingers of the technician touch the leads of the ohmmeter when measuring the following resistors:

- a.  $270 \text{ }\Omega$
- b.  $390 \text{ k}\Omega$
- c.  $2.2 \text{ M}\Omega$
- d.  $1.5 \text{ k}\Omega$
- e.  $10 \text{ k}\Omega$