

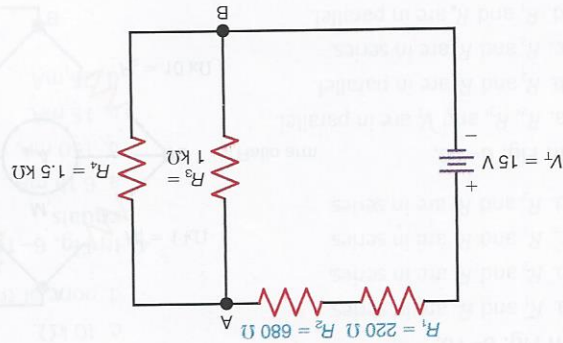


Figure 6-18

SECTION 6-1 FINDING R_T FOR SERIES-PARALLEL

RESISTANCES

6-1 In Fig. 6-18, identify which components are in series and which ones are in parallel.

6-2 In Fig. 6-18,

- 6-3 **Must-do** In Fig. 6-18, solve for the following: I_T , I_1 , V_1 , V_2 , V_3 , V_4 , I_3 , and I_4 .
- 6-4 In Fig. 6-19, identify which components are in series and which ones are in parallel.
- 6-5 In Fig. 6-19,
- What is the equivalent resistance of R_2 and R_3 across points A and B?
 - How much is the total resistance, R_T of the entire circuit?
 - How much is the total current, I_T in the circuit?
 - How much current flows into point B?
 - How much current flows away from point A?

Problems

- In a series-parallel circuit, how can you tell which resistances are in series and which are in parallel?
 - Draw a schematic diagram showing two resistances in a parallel bank that is in series with one resistance.
 - Draw a diagram showing how to connect three resistances of equal value so that the combined resistance will be $1\frac{1}{2}$ times the resistance of one unit.
 - Draw a diagram showing two strings in parallel across a voltage source, where each string has three series resistances.
 - Explain why components are connected in series-parallel, showing a circuit as an example of your explanation.
 - Give two differences between a short circuit and an open circuit.
7. Explain the difference between voltage division and current division.
8. In Fig. 6-12, assume that the thermistor has a positive temperature coefficient (PTC). Explain what happens to the voltage V_{CD} (a) if the ambient temperature decreases; (b) if the ambient temperature increases.
9. Draw a circuit with nine 40-V, 100-W bulbs connected to a 120-V source.
10. (a) Two 10- Ω resistors are in series with a 100-V source. If a third 10- Ω R is added in series, explain why I will decrease. (b) The same two 10- Ω resistors are in parallel with the 100-V source. If a third 10- Ω R is added in parallel, explain why I_T will increase.

Essay Questions

18. In Fig. 6-17, assume that the standard resistor, R_3 , has been adjusted so that the current in M_1 is exactly 0 μ A. How much voltage exists at terminal C with respect to terminal B?
19. In Fig. 6-17, assume that the ratio arm resistors, R_1 and R_2 , are
- 1.1 V.
 - 0 V.
 - 10.9 V.
 - none of the above.

20. In Fig. 6-17, assume that the standard resistor, R_3 , cannot be adjusted high enough to provide a balanced condition. What
- is balanced?
- equals 33,950 Ω when the bridge the unknown resistor, R_x , if R_3
- 339.5 k Ω .
 - 3.395 k Ω .
 - 33,950 Ω .
 - none of the above.

- modification must be made to the circuit?
- Change the ratio arm fraction R_1/R_2 from $1/10$ to $1/100$ or something less.
 - Change the ratio arm fraction, R_1/R_2 from $1/10$ to $1/10$ or something greater.
 - Reverse the polarity of the applied voltage, V_T .
 - None of the above.