

Figure 6-28


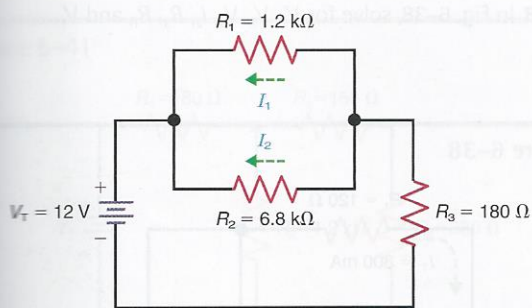



Figure 6-29

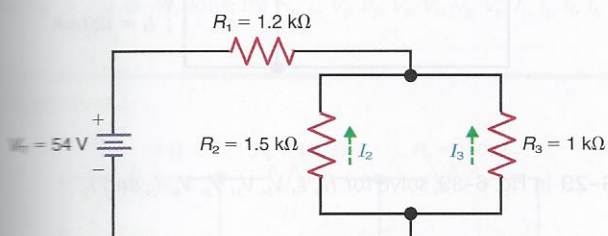

SECTION 6-4 RESISTANCE BANKS AND STRINGS IN SERIES-PARALLEL


6-20 In Fig. 6-30, solve for R_T , I_T , V_1 , V_2 , V_3 , V_4 , I_1 , I_2 , I_3 , and I_4 .

Figure 6-30

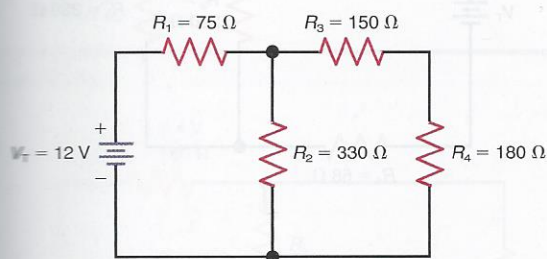


6-21 In Fig. 6-31, solve for R_T , I_T , V_1 , V_2 , V_3 , V_4 , V_5 , I_1 , I_2 , I_3 , I_4 , and I_5 .

Figure 6-31

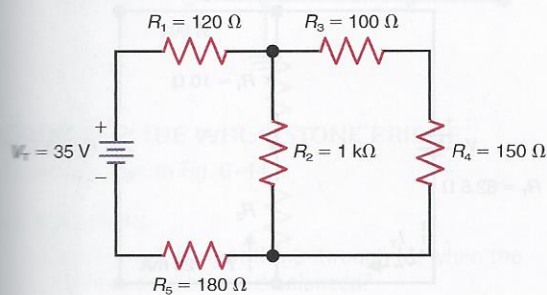


6-22 In Fig. 6-32, solve for R_T , I_T , V_1 , V_2 , V_3 , V_4 , V_5 , V_6 , I_1 , I_2 , I_3 , I_4 , I_5 , and I_6 .

Figure 6-32

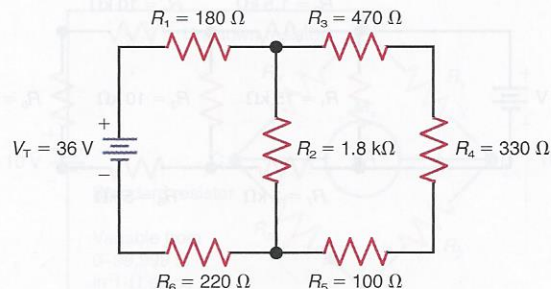

6-23 In Fig. 6-33, solve for R_T , I_T , V_1 , V_2 , V_3 , V_4 , V_5 , I_1 , I_2 , I_3 , I_4 , and I_5 .

Figure 6-33

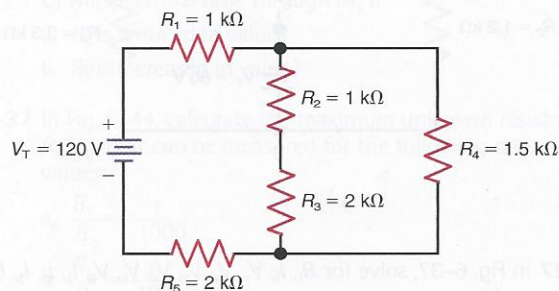

6-24 In Fig. 6-34, solve for R_T , I_T , V_1 , V_2 , V_3 , V_4 , V_5 , V_6 , I_1 , I_2 , I_3 , I_4 , I_5 , and I_6 .

Figure 6-34

