

Problem 1-1: For a resistor circuit element shown in Figure 1-1, and with constitutive relation of Equation 1-1, where V_{n1} and V_{n2} are the node voltages at the ends of the resistor element. i_R is the current through the resistor element, and the resistance has a value of 5 ohms.

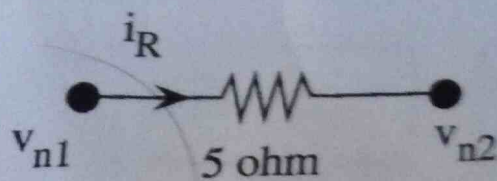


Figure 1-1


$$(V_{n1} - V_{n2}) - 5 i_R = 0$$

Equation 1-1

$$\frac{V_{n1} - V_{n2}}{5} = i_R$$

$$\frac{V_{n1} - V_{n2}}{5} = \frac{5 i_R}{5}$$

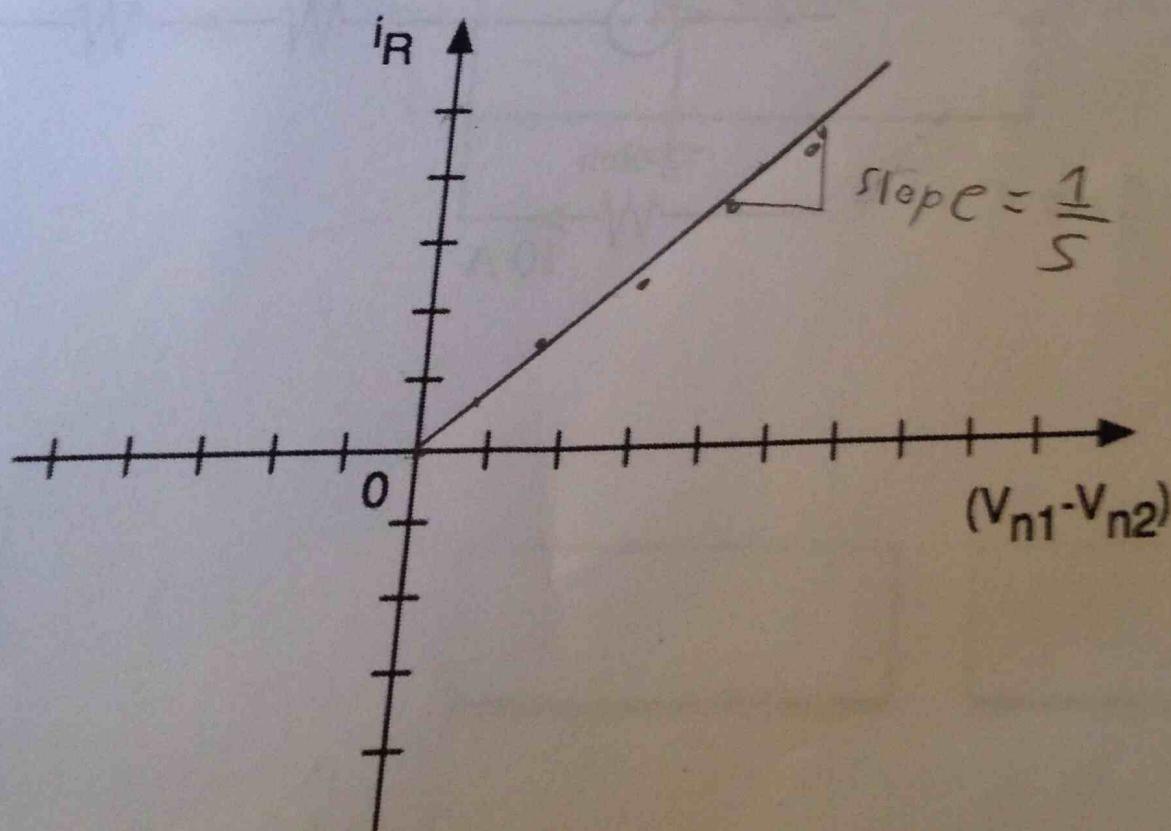at least 3 points that satisfy the constitutive relation and draw a connecting line through your points on the graph below of i_R versus the quantity $(V_{n1} - V_{n2})$. Show units on your graph.



Problem 1-2B: The node region in Figure 1-2B has 6 elements. Calculate the numerical value for the branch current i_b , give units. Only the local node region is shown NOT the entire circuit. [Four branch currents are given; use Conservation Laws.]

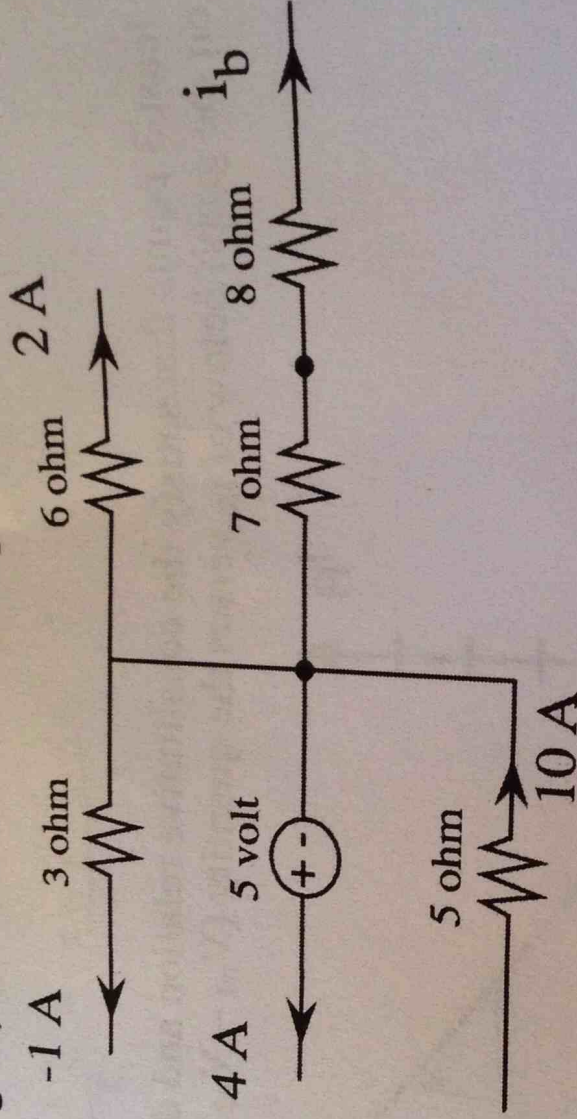


Figure 1-2B

$$i_b = 6 \text{ amps}$$

$$6 + 4 - 10 = 0$$

$$= 6$$

Problem 1-2A: The node in Figure 1-2A has 5 branches. Calculate the numerical value for the branch current, i_a , give units. Only the local node region is shown NOT the entire circuit. [Use Conservation Laws]

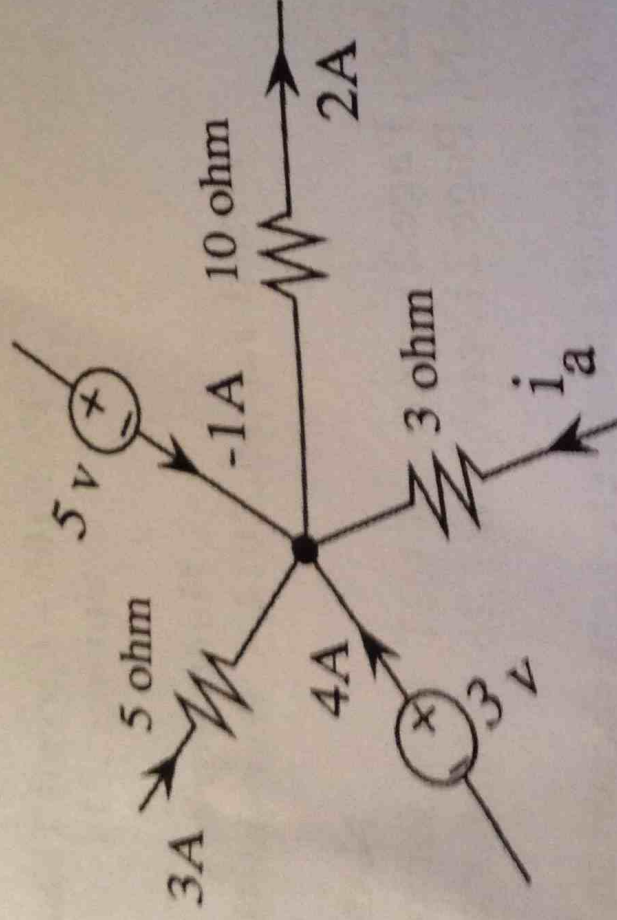


Figure 1-2A

$$i_a = -4 \text{ amp}$$

$$2 - i_a - 4 - 3 = 0$$

Problem 1-3A: The circuit in Figure 1-3A has 3 elements. Calculate the numerical value for the current, i_A , and the power dissipated in the 3 ohm resistor, give units. [Use Constitutive Laws with nodes, note: 'ground' is zero volts.]

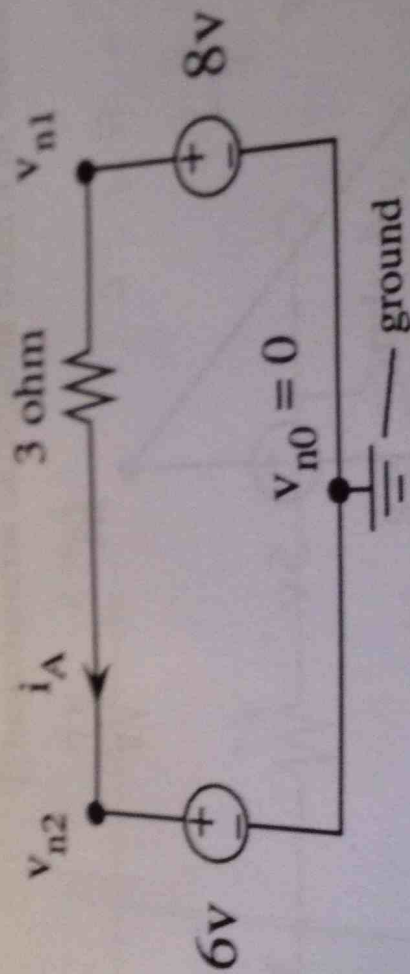


Figure 1-3A

$$i_A = \frac{V}{R} = \frac{8-6}{3} \text{ amps}$$

power dissipated = volts (i_A) = $2 \left(\frac{2}{3} \right) \text{ amps} =$

$$i_A = \frac{2}{3} \text{ amps}$$

$$P_d = 2 \left(\frac{2}{3} \right) \text{ watts} = \frac{4}{3} \text{ watts}$$