

✓

Sample problems

Q1. Determine if each of the following statements is true or false. (20 points)

(True / False)

a) $(1024)_{10} = (1000)_8$

b) $(11111111)_2 = (001001010101)_{BCD}$

c) $x + xy + xyz = x$

d) $(x \oplus y)' = (x' \oplus y') \oplus 1$

e) $((x y z)' \cdot (w s)')' = xyz + (w' + s')'$



f) The minimal size of a ROM that implements 4 functions in the same 6 variables is 24 bits.

g) The sum of minterms for the function $(x \oplus y \oplus z)'$ is $xyz' + xy'z + x'yz$.

h) If $x \oplus y = z$, then $x = y \oplus z$.

i) If $x+y = z$, then $x = z+y'$.

j) In the following circuits, $F1 = F2$.

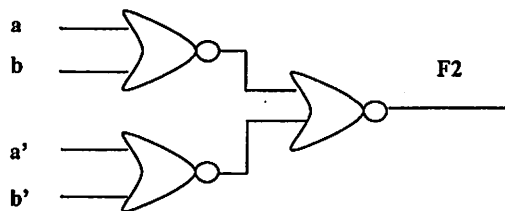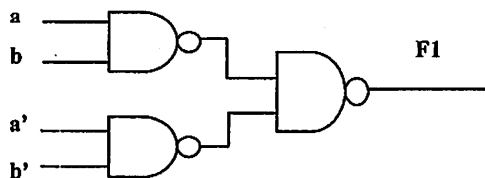

Q2. Express the following function

(12 points)





$$F(w,x,y,z) = \Sigma(0,1,2,5,10,11,13,14,15)$$

in the following forms

- a. Minimal sum of products**
- b. Minimal product of sums**

Q3. Complete the truth table for the outputs of the following circuits.

(20 points)

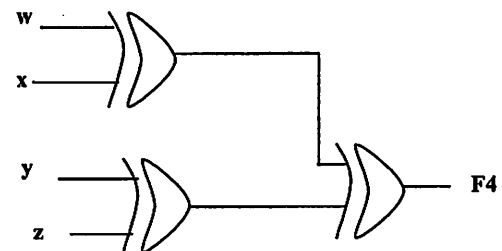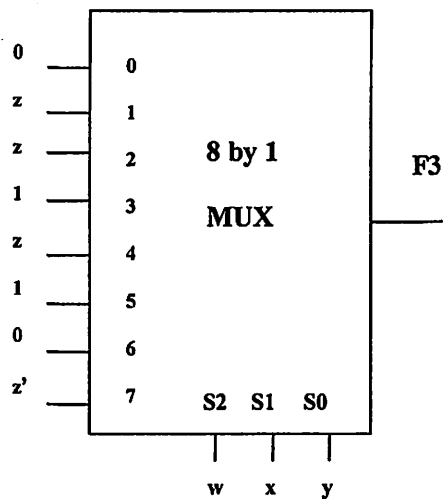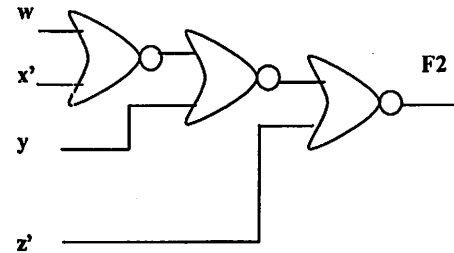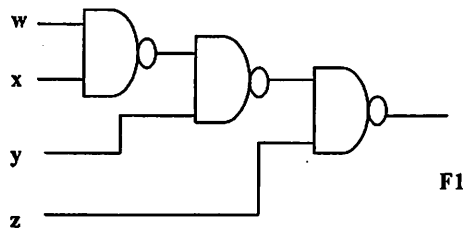

w	x	y	z	F1	F2	F3	F4
0	0	0	0				
0	0	0	1				
0	0	1	0				
0	0	1	1				
0	1	0	0				
0	1	0	1				
0	1	1	0				
0	1	1	1				
1	0	0	0				
1	0	0	1				
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

Q4. Design a circuit with three inputs x, y, z , that represent a binary integer M and six outputs A, B, C, D, E, F that represent a binary integer $N = M^2$. For example,

$x, y, z = 0, 0, 1$ implies $A, B, C, D, E, F = 0, 0, 0, 0, 0, 1$;


$x, y, z = 0, 1, 1$ implies $A, B, C, D, E, F = 0, 0, 1, 0, 0, 1$;

$x, y, z = 1, 1, 0$ implies $A, B, C, D, E, F = 1, 0, 0, 1, 0, 0$;

i) Assume one 3×8 binary decoder and exactly six OR gates are available. (8 points)


ii). If the above circuit is to be implemented as a ROM, determine the size of the ROM. (4 points)

(12 points)

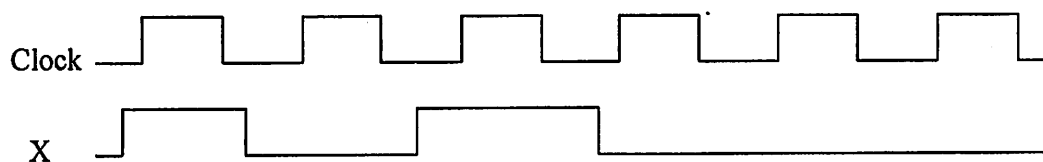

Z?

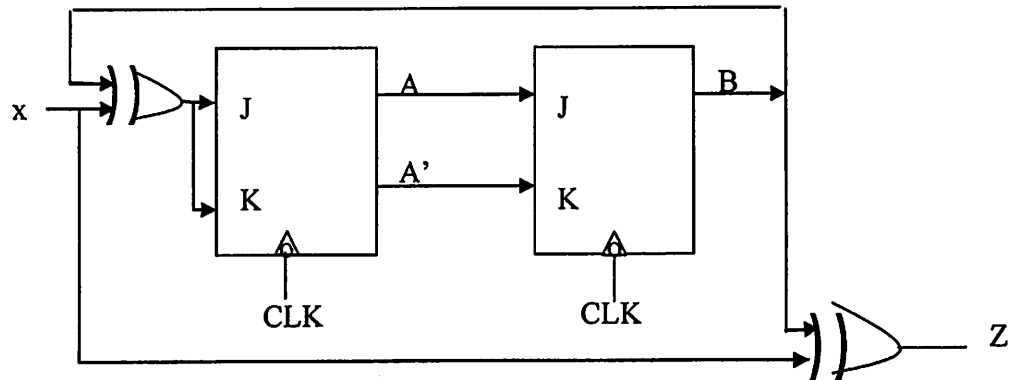- Q6.** For the following circuit, setup
- The state table and the state diagram
 - If the starting state is (0,0) and the input sequence is 1000000 determine the output sequence and the corresponding final state.
- (12 points)



Q7. Design a sequential circuit to implement the following state diagram using D flip-flops.

(12 points)

