

Name _____

- 1) If the *effective* voltage of an ac receptacle is 120V, what is the *peak-to-peak* voltage?
 A) 240 V
 B) 339 V
 C) 170 V
 D) 84.8 V

- 2) Which of the following will be necessary to increase the frequency of a sinusoidal waveform?
 A) Decrease the time period between successive repetitions
 B) Increase the amplitude
 C) Reverse polarity
 D) Increase the time period between successive repetitions

- 3) What are the period and frequency of a periodic wave that has 12 cycles in 46 milliseconds?

- 4) What is the inductive reactance at 800 Hz of a 1 mH inductor with an internal resistance of 20 Ω ?
 A) 20 Ω
 B) 12 Ω
 C) 5.0 Ω
 D) 0.2 Ω


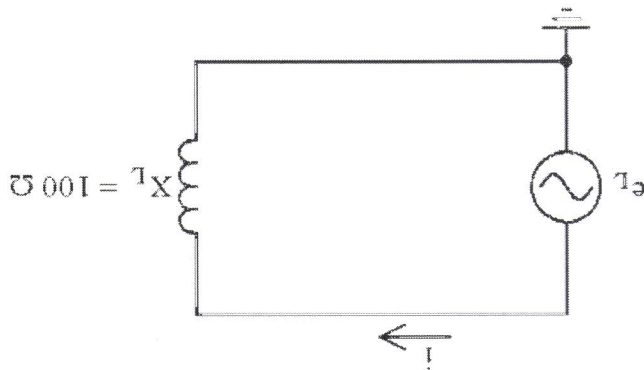


Figure 14.1


- 5) See Figure 14.1. What is the coil current if e_L is $500 \sin(50t + 20^\circ)$?
 A) $5 \sin(50t + 110^\circ)$
 B) $5 \sin 50t$
 C) $5 \sin(50t - 70^\circ)$
 D) $5 \sin(50t + 20^\circ)$

- 6) What is the susceptance of a 100 μF capacitor at 1000 Hz?
 A) 104 S
 B) 0.63 S
 C) 1.59 S
 D) 10^{-4} S

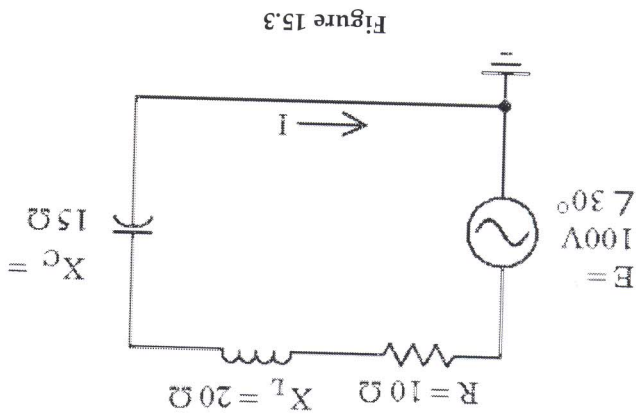- 10) See Figure 15.3. Calculate the current I.
 11) See Figure 15.3. Use the voltage divider rule to calculate the voltage across the coil.




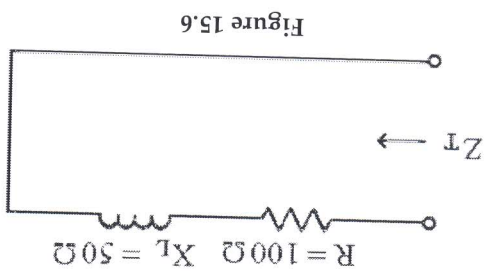- 7) See Figure 15.6. Which one of the following combinations is equivalent to the given series circuit?
 A) $R = 40 \Omega$ in parallel with $X_L = 20 \Omega$.
 B) $R = 250 \Omega$ in parallel with $X_L = 125 \Omega$.
 C) $R = 125 \Omega$ in parallel with $X_L = 250 \Omega$.
 D) $R = 20 \Omega$ in parallel with $X_L = 40 \Omega$.
- 8) Ignoring any effects of dc resistance, what is the total reactance of a 250 mH coil in series with a 4.7 microfarad capacitor at a signal frequency of 1000 Hz?
 A) 1570 ohms
 B) 35 ohms
 C) 1540 ohms
 D) 1600 ohms
- 9) If you need an LC circuit to be resonant at 2500 Hz, and use a 150 mH coil, what should the capacitance value be?
 A) 0.015 microfarads
 B) 0.027 microfarads
 C) 27 microfarads
 D) 0.15 microfarads




- 14) See Figure 17.1. The current source (a) includes a current $I = 10 \text{ A} \angle 20^\circ$ and an impedance consisting of a 10Ω resistor in series with a 20Ω inductive reactance. If this current source is converted to a voltage source as shown in (b), what is the value of the series impedance element Z?
- A) $20 \Omega \angle 90^\circ$
 B) $22.4 \Omega \angle 63.4^\circ$
 C) $10 \Omega \angle 70^\circ$
 D) $22.4 \Omega \angle 26.6^\circ$

Figure 17.1

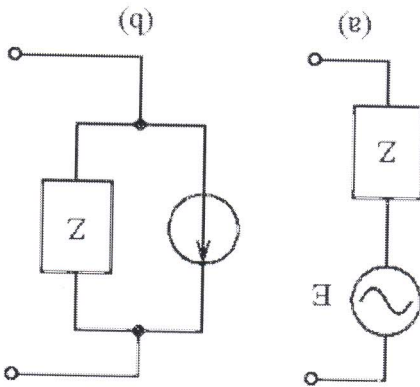

- 12) See Figure 16.1. If $I_S = 1 \text{ A} \angle 80^\circ$, what is the current through the coil?
- A) $2 \text{ A} \angle 100^\circ$
 B) $2 \text{ A} \angle -100^\circ$
 C) $0.5 \text{ A} \angle -100^\circ$
 D) $0.5 \text{ A} \angle 100^\circ$
- 13) A 1 kHz signal E is applied in the circuit shown in Figure 16.1. What is the value of inductor L?
- A) $1910 \mu\text{H}$
 B) $955 \mu\text{H}$
 C) $26.5 \mu\text{H}$
 D) $1047 \mu\text{H}$

Figure 16.1

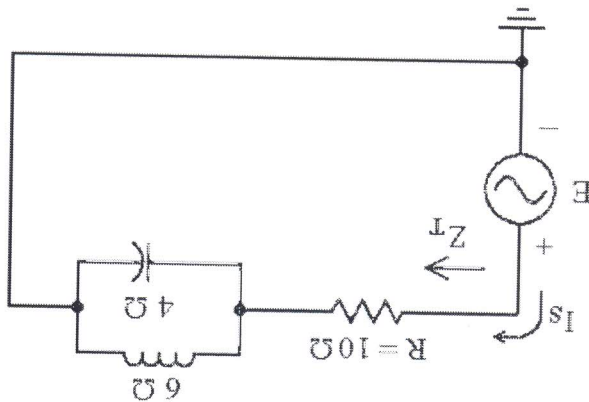

- 17) See Figure 17.4. In a general bridge circuit such as this, what condition will result in a balanced bridge?
 A) $Z_1Z_3 = Z_2Z_4$
 B) $Z_3 = Z_4$
 C) $Z_1Z_4 = Z_2Z_3$
 D) $Z_1Z_2 = Z_3Z_4$

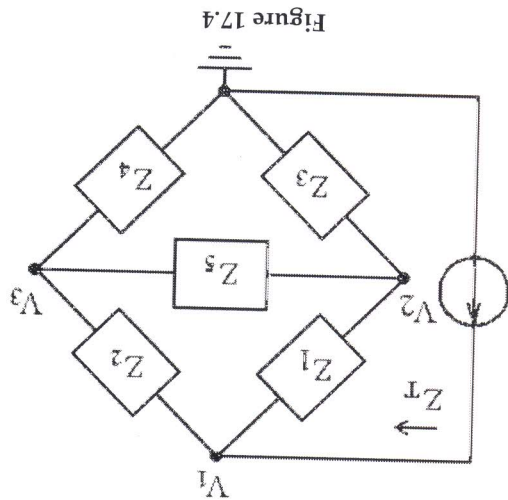


Figure 17.4

- 16) See Figure 17.3. Which one equation describes current I_2 ?
 A) $I_2 = I_4 + I_A$
 B) $I_2 = (V_1 + V_2)/Z_2$
 C) $I_2 = (V_1 - V_2)/Z_2$
 D) $I_2 = -I_A$
- 15) See Figure 17.3. When setting up this circuit for nodal analysis solution, which one equation describes node 1?
 A) $I_4 = I_A + I_2$
 B) $I_A = I_4$
 C) $I_2 = I_4 - I_3$
 D) $I_3 = I_A + I_4$


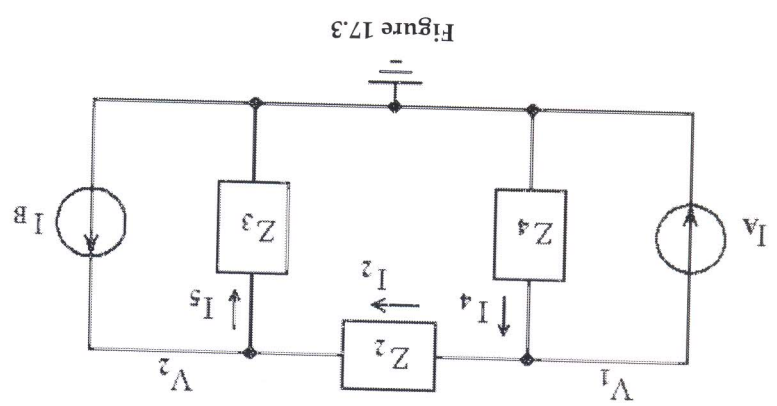


Figure 17.3


- 19) See Figure 20.2. What is the source current at resonance?
 A) $0.25\text{ A} \angle 0^\circ$ B) $66.7\text{ mA} \angle +90^\circ$ C) $4\text{ A} \angle 0^\circ$ D) $66.7\text{ mA} \angle -90^\circ$
- 20) See Figure 20.2. What is the voltage across the resistor in this resonant circuit?
 A) 1200 V B) 1180 V C) 20 V D) 80 V
- 21) See Figure 20.2. If the resonant frequency is 10 kHz , what is the bandwidth?
 A) 167 Hz B) $10,000\text{ Hz}$ C) 7071 Hz D) 5000 Hz

Figure 20.2

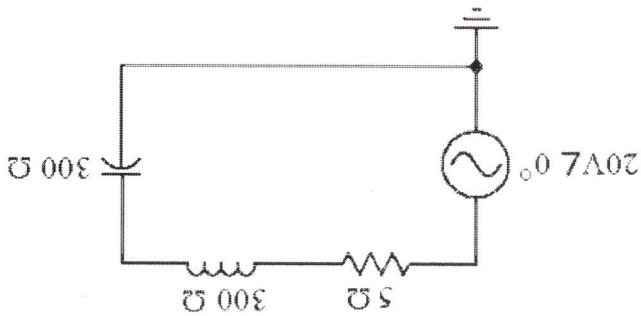


- 18) Referring to the circuit shown in Figure 17.8, determine the current through the $2\text{ }\Omega$ inductor, by using Mesh Analysis.
 A) $20.0\text{ A} \angle -143^\circ$ B) $3.61\text{ A} \angle 124^\circ$ C) $4.47\text{ A} \angle 153^\circ$


Figure 17.8

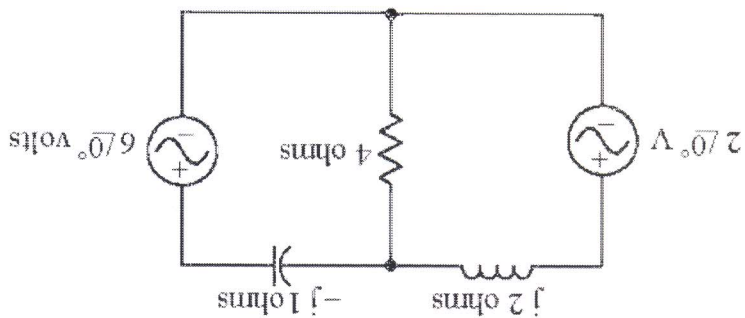

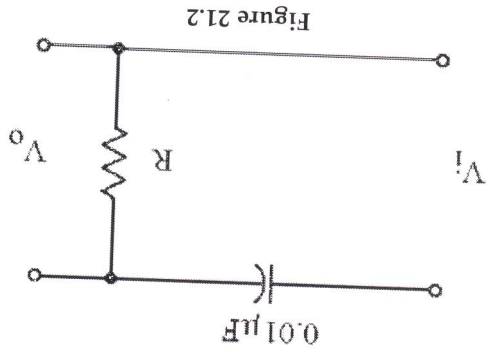- 24) See Figure 21.2. At the cutoff frequency f_c
- A) V_o leads V_i by 45°
 - C) V_o leads V_i by 90°
 - B) V_o lags V_i by 45°
 - D) V_o lags V_i by 90°
- 25) See Figure 21.2. V_i has a peak amplitude of 10 V. In reality, what is the peak amplitude of V_o at the cutoff frequency f_c ?
- A) 10 V
 - B) 5 V
 - C) 20 V
 - D) 7.07 V



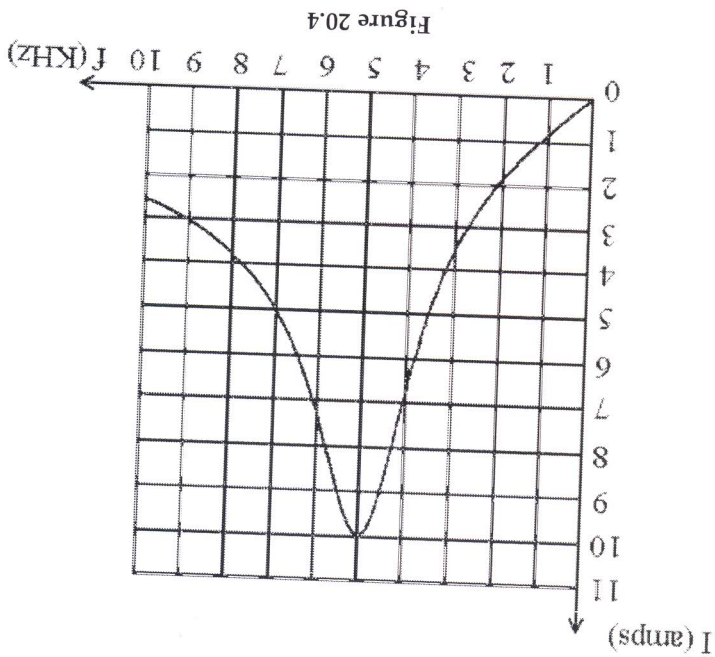- 22) See Figure 20.4. This curve describes a series resonant circuit. What is the approximate bandwidth of this circuit?
- A) 3.45 KHz
 - B) 1.9 KHz
 - C) 5.0 KHz
 - D) 2.5 KHz
- 23) What power level is 3 dB above 10 W?
- A) 10 W
 - B) 13 W
 - C) 14.1 W
 - D) 20 W




22) _____

23) _____


- 28) See Figure 22.3. What is the transformation ratio for this transformer?
 A) 0.667 B) 30 C) 1.5 D) 20
- 29) See Figure 22.3. What is the voltage E_s across the load?
 A) 66.7 V B) 100 V C) 150 V D) 120 V

Figure 22.3

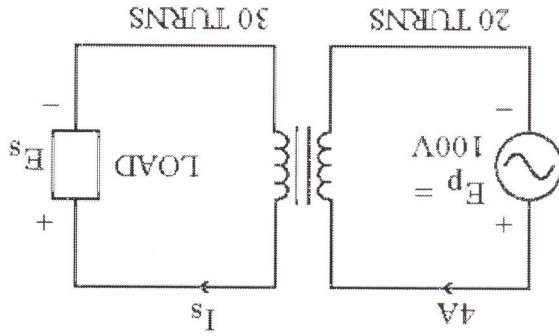


- 27) See Figure 22.6. Determine the voltage E_2 across Z_2 .
 A) 200 V B) 50 V C) 3200 V D) 150 V

Figure 22.6

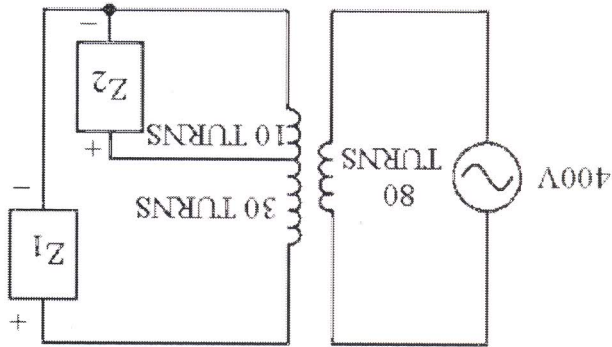

- 26) See Figure 22.1. What is the induced voltage e_p in the primary if the primary flux changes at 300 mWb/s?
 A) 15 V B) 3000 V C) 6 V D) 1.2 V

Figure 22.1

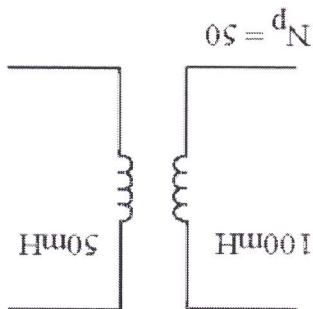

- 30) See Figure 22.3. What is the current I_S through the load?
 A) 6 A B) 2.67 A C) 4 A D) 1.5 A
- 31) Five watts are dissipated in a primary (input) circuit that includes a perfectly matched, ideal transformer with a primary to secondary turns ratio of 15:1. If the input resistance is $2000\ \Omega$, what is the load resistance?
 A) $79\ \Omega$ B) $6243\ \Omega$ C) $30,000\ \Omega$ D) $133\ \Omega$ E) $8.9\ \Omega$
- 32) NOTE: The following questions are all part of the same Research and Development (R&D) problem
 An Electrocardiogram (ECG) is the electrical recording of a patient's heart activity. Normal range for a ECG signal is 1 mV-p-p at 0.6 - 2 Hz. Outside electrical noise from other equipment being used in patient treatment must be removed for a clean ECG signal. This noise includes frequencies ranging from 60 Hz and up. A circuit to process the signal needs to be designed.
 What type of filter should be used?
 A) Stop-band B) Low-pass C) Pass-band D) High-pass
- 33) Due to a time crunch, you must use the parts on-hand in the shop inventory. You can find a $0.047\ \mu\text{farad}$ capacitor and a $500\ \text{k}\Omega$ potentiometer. What should the potentiometer be set to for $f_c=10\ \text{Hz}$?
- 34) The input to the processing portion of the ECG machine needs a 5 Vp-p signal. What is the needed gain from the amplifier in dB?
- 35) This circuit will have a second filter in parallel, allowing a 500 kHz signal used for respiration monitoring to pass through. Using another $0.047\ \mu\text{farad}$ capacitor from the bin and a variable inductor, what will the inductor need to be set to for the pass-band portion of the filter so $f_s=500\ \text{kHz}$?
 A) $3.5\ \mu\text{H}$ B) $8.5\ \mu\text{H}$ C) $2.16\ \mu\text{H}$ D) $26\ \mu\text{H}$