

Figure 9-18

9-15 In Fig. 9-18, write a KVL equation for the loop ACEFDBA going clockwise from point A.

9-14 In Fig. 9-18, write a KVL equation for the loop EFDCE going clockwise from point E.

9-13 In Fig. 9-18, write a KVL equation for the loop ABDCA going counterclockwise from point A.

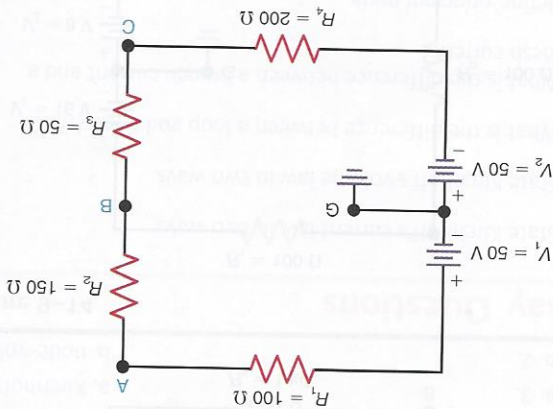


Figure 9-17

9-12 In Fig. 9-17, solve for the voltages V_{AG} , V_{BG} , and V_{CG} . Indicate the proper polarity for each voltage.

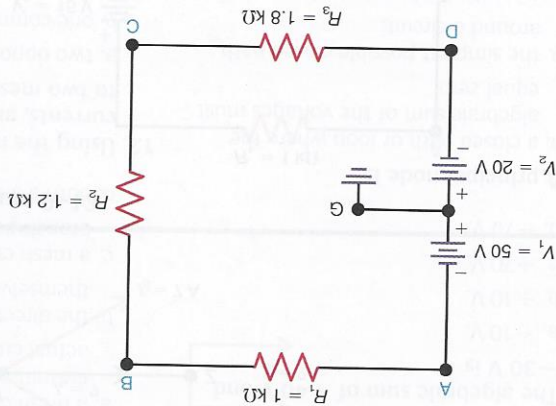


Figure 9-16

9-11 In Fig. 9-16, solve for the voltages V_{AG} , V_{BG} , V_{CG} , and V_{DG} . Indicate the proper polarity for each voltage.

9-17 Repeat Prob. 9-16 for Fig. 9-20.

- Using Kirchhoff's current law, write an equation for the currents I_1 , I_2 , and I_3 at point C.
- Specify the current I_3 in terms of I_1 and I_2 .
- Write a KVL equation for the loop ABDCA, going counterclockwise from point A, using the terms V_{R1} and V_{R2} . This loop will be called Loop 1.
- Write a KVL equation for the loop FECD, going counterclockwise from point F, using the terms V_{R2} and V_{R3} . This loop will be called Loop 2.
- Specify each resistor voltage drop as an I/R product using actual resistor values for R_1 , R_2 , and R_3 .
- Rewrite the KVL equation for Loop 1 in step c using the I/R voltage values for V_{R1} and V_{R2} specified in step e.
- Rewrite the KVL equation for Loop 2 in step d using the I/R voltage values for V_{R2} and V_{R3} specified in step e.
- Reduce the Loop 1 and Loop 2 equations in steps f and g to their simplest possible form.
- Solve for currents I_1 and I_2 using any of the methods for the solution of simultaneous equations. Next, solve for I_3 .
- In Fig. 9-19, were the assumed directions of all currents correct? How do you know?
- Using the actual values of I_1 , I_2 , and I_3 , calculate the individual resistor voltage drops.
- Rewrite the KVL equations for both Loops 1 and 2 using actual voltage values. Go counterclockwise around both loops when adding voltages. (Be sure that the resistor voltage drops all have the correct polarity based on the actual directions for I_1 , I_2 , and I_3 .)
- Based on the actual directions for I_1 , I_2 , and I_3 , write a KCL equation for the currents at point C.

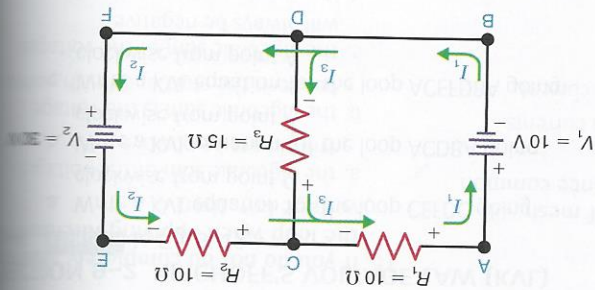


Figure 9-19

SECTION 9-3 METHOD OF BRANCH CURRENTS

9-16 Using the method of branch currents, solve for the unknown values of voltage and current in Fig. 9-19. This, complete steps a through m. The assumed directions of all currents is shown in the figure.