

Figure 17-14



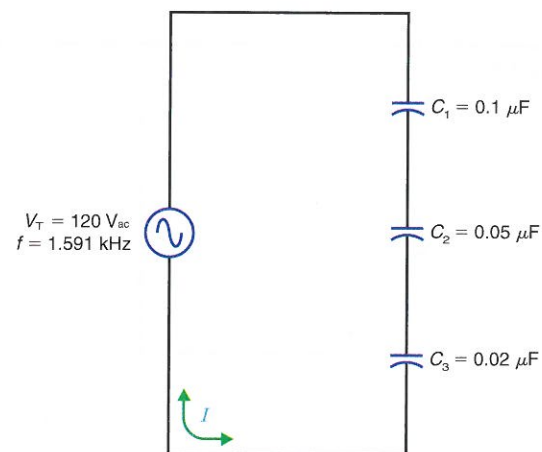


Figure 17-15

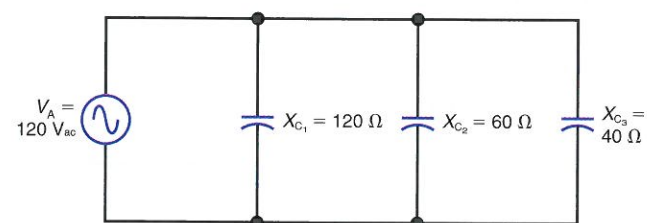

- 17-25 In Fig. 17-16, solve for
- X_{C_1} , X_{C_2} , and X_{C_3} .
 - I_{C_1} , I_{C_2} , and I_{C_3} .
 - I_T .
 - $X_{C_{eq}}$.
 - C_T .

Figure 17-16

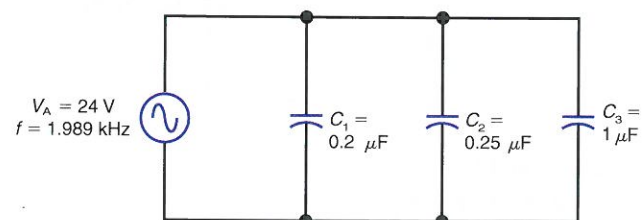

Critical Thinking

- 17-34 Explain an experimental procedure for determining the value of an unmarked capacitor. (Assume that a capacitance meter is not available.)

- 17-26 In Fig. 17-15, solve for C_1 , C_2 , C_3 , and C_T if the frequency of the applied voltage is 6.366 kHz.

SECTION 17-5 APPLICATIONS OF CAPACITIVE REACTANCE

- 17-27 Calculate the value of capacitance, C , required to produce an X_C value of 500Ω at the following frequencies:
- $f = 100 \text{ Hz}$.
 - $f = 2 \text{ kHz}$.
 - $f = 50 \text{ kHz}$.
 - $f = 10 \text{ MHz}$.


SECTION 17-6 SINE-WAVE CHARGE AND DISCHARGE CURRENT

- 17-28 Calculate the instantaneous charging current, i_C , for a $0.33\text{-}\mu\text{F}$ capacitor if the voltage across the capacitor plates changes at the rate of 10 V/1 ms .
- 17-29 Calculate the instantaneous charging current, i_C , for a $0.01\text{-}\mu\text{F}$ capacitor if the voltage across the capacitor plates changes at the rate of
- 100 V/s .
 - 100 V/ms .
 - $50 \text{ V}/\mu\text{s}$.
- 17-30 What is the instantaneous discharge current, i_C , for a $100\text{-}\mu\text{F}$ capacitor if the voltage across the capacitor plates decreases at the rate of
- 10 V/s .
 - 1 V/ms .
 - 50 V/ms .

- 17-31 For a capacitor, what is the phase relationship between the charge and discharge current, i_C , and the capacitor voltage, v_C ? Explain your answer.
- 17-32 A capacitor has a discharge current, i_C , of 15 mA when the voltage across its plates decreases at the rate of $150 \text{ V}/\mu\text{s}$. Calculate C .
- 17-33 What rate of voltage change, $\frac{dv}{dt}$, will produce a charging current of 25 mA in a $0.01\text{-}\mu\text{F}$ capacitor? Express your answer in volts per second.

- 17-35 In Fig. 17-17, calculate X_{C_1} , X_{C_2} , C_1 , C_3 , V_{C_1} , V_{C_2} , V_{C_3} , I_{C_2} , and I_{C_3} .

Figure 17-17 Circuit for Critical Thinking Prob. 17-35.

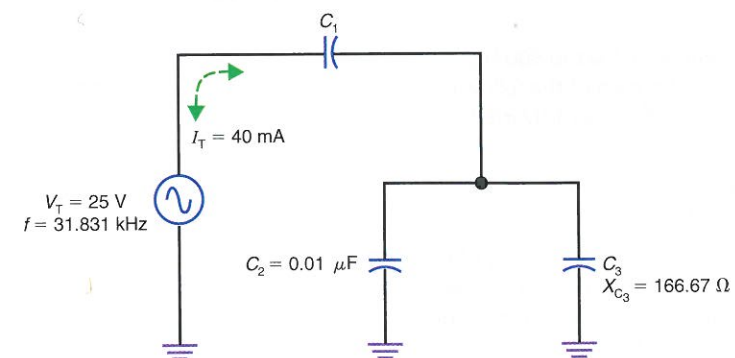

Answers to Self-Reviews

- 17-1 a. $0.1 \mu\text{F}$
b. $0.5 \mu\text{F}$
- 17-2 a. 200Ω
b. 800Ω
c. larger
- 17-3 a. 500Ω
b. 120Ω

- 17-4 a. 300Ω
b. 66.7Ω
- 17-5 a. 50Ω
b. 1000Ω
- 17-6 a. 90°
b. 0 or 360°
c. 90°

Laboratory Application Assignment

In this lab application assignment you will examine how the capacitive reactance, X_C , of a capacitor decreases when the frequency, f , increases. You will also see that more capacitance, C , at a given frequency results in less capacitive reactance, X_C . Finally, you will observe how X_C values combine in series and in parallel.

Equipment: Obtain the following items from your instructor.

- Function generator
- Assortment of capacitors
- DMM

Capacitive Reactance, X_C

Refer to Fig. 17-18a. Calculate and record the value of X_C for each of the following frequencies listed below. Calculate X_C as $1/(2\pi fC)$.

- $X_C = \underline{\hspace{2cm}} @ f = 100 \text{ Hz}$
 $X_C = \underline{\hspace{2cm}} @ f = 200 \text{ Hz}$
 $X_C = \underline{\hspace{2cm}} @ f = 400 \text{ Hz}$

Connect the circuit in Fig. 17-18a. Set the voltage source to exactly 5 V_{rms} . For each of the following frequencies listed below, measure and record the current, I . (Use a DMM to measure I .) Next, calculate X_C as V/I .

- $I = \underline{\hspace{2cm}} @ f = 100 \text{ Hz}; X_C = \underline{\hspace{2cm}}$
 $I = \underline{\hspace{2cm}} @ f = 200 \text{ Hz}; X_C = \underline{\hspace{2cm}}$
 $I = \underline{\hspace{2cm}} @ f = 400 \text{ Hz}; X_C = \underline{\hspace{2cm}}$

How do the experimental values of X_C compare to those initially calculated? _____
 Based on your experimental values, what happens to the value of X_C each time the frequency, f , is doubled? _____

Figure 17-18

