

- 16-11 Determine the capacitance of each chip capacitor in Fig. 16-34. Use the coding scheme in Fig. 16-17.

Figure 16-34




- 16-12 Determine the capacitance of each chip capacitor in Fig. 16-35. Use the coding scheme in Fig. 16-18.

Figure 16-35




- 16-13 Determine the capacitance of each chip capacitor in Fig. 16-36.

Figure 16-36

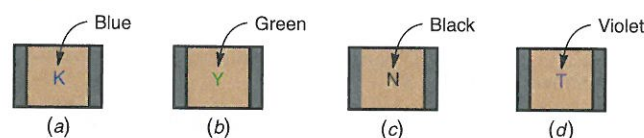

- 16-14 Determine the capacitance and tolerance of each capacitor in Fig. 16-37.

Figure 16-37

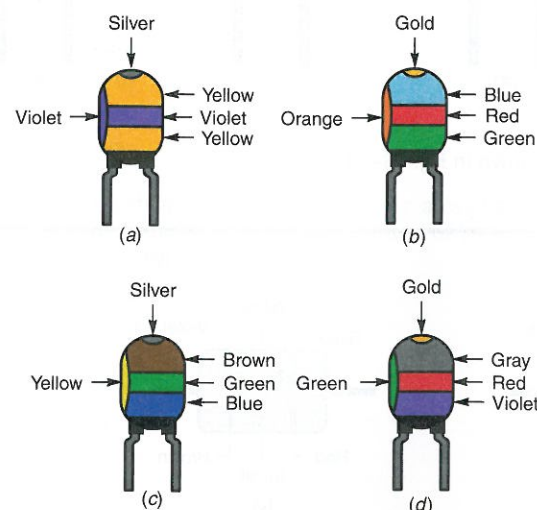

- 16-15 Determine the permissible capacitance range of the capacitors in
a. Fig. 16-31a.
b. Fig. 16-31d.
c. Fig. 16-31f.
d. Fig. 16-32c.
e. Fig. 16-32d.

- 16-16 Explain the alphanumeric code, Z5U, for the capacitor in Fig. 16-32b.

SECTION 16-7 PARALLEL CAPACITANCES


- 16-17 A $5\text{-}\mu\text{F}$ and $15\text{-}\mu\text{F}$ capacitor are in parallel. How much is C_T ?

- 16-18 A $0.1\text{-}\mu\text{F}$, $0.27\text{-}\mu\text{F}$, and $0.01\text{-}\mu\text{F}$ capacitor are in parallel. How much is C_T ?

- 16-19 A 150-pF , 330-pF , and $0.001\text{-}\mu\text{F}$ capacitor are in parallel. How much is C_T ?

- 16-20 In Fig. 16-38,
a. how much voltage is across each individual capacitor?
b. how much charge is stored by C_1 ?
c. how much charge is stored by C_2 ?
d. how much charge is stored by C_3 ?
e. what is the total charge stored by all capacitors?
f. how much is C_T ?

Figure 16-38

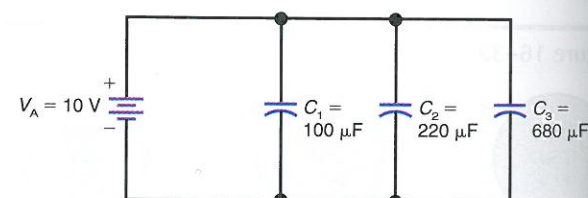

SECTION 16-8 SERIES CAPACITANCES


- 16-21 A $0.1\text{-}\mu\text{F}$ and $0.4\text{-}\mu\text{F}$ capacitor are in series. How much is the equivalent capacitance, C_{EQ} ?

- 16-22 A 1500-pF and $0.001\text{-}\mu\text{F}$ capacitor are in series. How much is the equivalent capacitance, C_{EQ} ?

- 16-23 A $0.082\text{-}\mu\text{F}$, $0.047\text{-}\mu\text{F}$, and $0.012\text{-}\mu\text{F}$ capacitor are in series. How much is the equivalent capacitance, C_{EQ} ?


- 16-24 In Fig. 16-39, assume a charging current of $180\text{-}\mu\text{A}$ flows for 1 s. Solve for
a. C_{EQ} .
b. the charge stored by C_1 , C_2 , and C_3 .
c. the voltage across C_1 , C_2 , and C_3 .
d. the total charge stored by all capacitors.

Figure 16-39

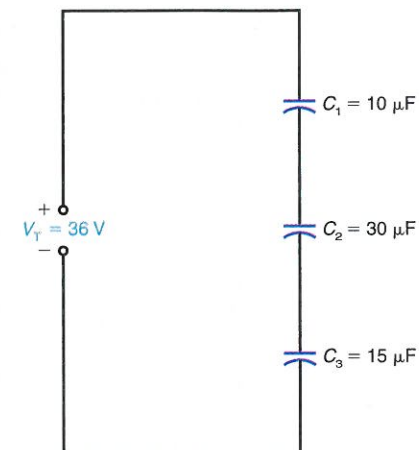

- 16-25 In Fig. 16-40, assume a charging current of 2.4-mA flows for 1 ms. Solve for
a. C_{EQ} .
b. the charge stored by C_1 , C_2 , and C_3 .
c. the voltage across C_1 , C_2 , and C_3 .
d. the total charge stored by all capacitors.

Figure 16-40

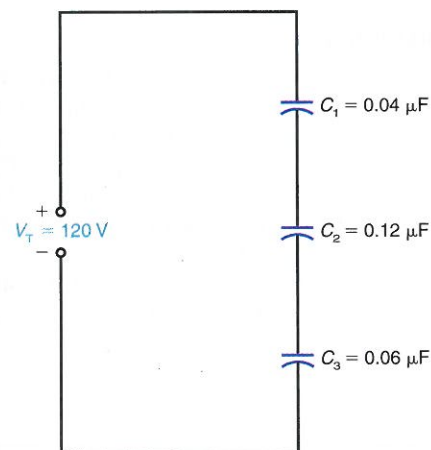

- 16-26 How much capacitance must be connected in series with a 120-pF capacitor to obtain an equivalent capacitance, C_{EQ} , of 100-pF .

Critical Thinking

- 16-37 Three capacitors in series have a combined equivalent capacitance C_{EQ} of 1.6-nF . If $C_1 = 4C_2$ and $C_3 = 20C_1$, calculate the values for C_1 , C_2 , and C_3 .

SECTION 16-9 ENERGY STORED IN ELECTROSTATIC FIELD OF CAPACITANCE

- 16-27 How much energy is stored by a $100\text{-}\mu\text{F}$ capacitor which is charged to

- a. 5-V ?
b. 10-V ?
c. 50-V ?

- 16-28 How much energy is stored by a $0.027\text{-}\mu\text{F}$ capacitor which is charged to

- a. 20-V ?
b. 100-V ?
c. 500-V ?

- 16-29 Calculate the energy stored by each capacitor in Fig. 16-39.

SECTION 16-10 MEASURING AND TESTING CAPACITORS

- 16-30 Make the following conversions:

- a. $0.047\text{-}\mu\text{F}$ to pF.
b. $0.0015\text{-}\mu\text{F}$ to pF.
c. $390,000\text{-pF}$ to μF .
d. 1000-pF to μF .

- 16-31 Make the following conversions:

- a. 15-nF to pF.
b. 1-nF to pF.
c. 680-nF to pF.
d. $33,000\text{-pF}$ to nF.
e. $1,000,000\text{-pF}$ to nF.
f. $560,000\text{-pF}$ to nF.

- 16-32 A plastic-film capacitor has a coded value of 154K. If the measured value of capacitance is $0.160\text{-}\mu\text{F}$, is the capacitance value within tolerance?

- 16-33 A ceramic disk capacitor is coded 102Z. If the measured value of capacitance is 680-pF , is the capacitance within tolerance?

- 16-34 A plastic-film capacitor has a coded value of 229B. If the measured value of capacitance is 2.05-pF , is the capacitance within tolerance?

SECTION 16-11 TROUBLES IN CAPACITORS

- 16-35 What is the ohmmeter reading for a(n)

- a. shorted capacitor.
b. open capacitor.
c. leaky capacitor.

- 16-36 Describe the effect of connecting a $0.47\text{-}\mu\text{F}$ capacitor to the leads of an analog ohmmeter set to the $R \times 10\text{K}$ range.

- 16-38 A 100-pF ceramic capacitor has a temperature coefficient T_C of N500. Calculate its capacitance at (a) 75°C ; (b) 125°C ; (c) -25°C .