


8. Referring to Fig. 17-8, draw three similar curves but for a sine wave of voltage with a period $T = 12 \mu\text{s}$ for the full cycle. Use the same C of 240 pF . Compare the value of X_C obtained as $1/(2\pi fC)$ and V_C/I_C .

Problems

SECTION 17-1 ALTERNATING CURRENT IN A CAPACITIVE CIRCUIT


- 17-1 With the switch, S_1 , closed in Fig. 17-9, how much is
a. the current, I , in the circuit?
b. the dc voltage across the 12-V lamp?
c. the dc voltage across the capacitor?

Figure 17-9

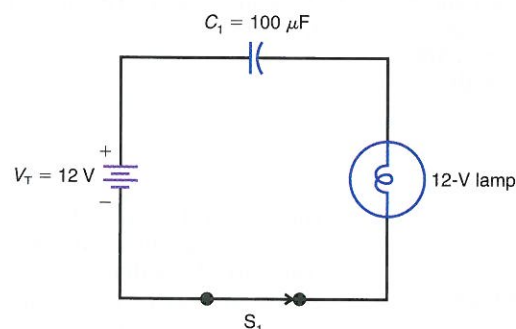

- 17-2 In Fig. 17-9 explain why the bulb will light for just an instant when S_1 is initially closed.
- 17-3 In Fig. 17-10, the capacitor and the lightbulb draw 400 mA from the 120-Vac source. How much current flows
a. to and from the terminals of the 120-Vac source?
b. through the lightbulb?
c. to and from the plates of the capacitor?
d. through the connecting wires?
e. through the dielectric of the capacitor?

Figure 17-10

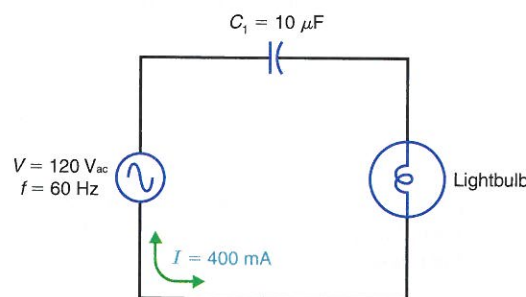


- 17-4 In Fig. 17-11, calculate the capacitive reactance, X_C , for the following values of V_{ac} and I ?
a. $V_{ac} = 10 \text{ V}$ and $I = 20 \text{ mA}$.
b. $V_{ac} = 24 \text{ V}$ and $I = 8 \text{ mA}$.

9. (a) What is the relationship between charge q and current i ? (b) How is this comparison similar to the relation between the two formulas $Q = CV$ and $i_C = C(dv/dt)$?

- c. $V_{ac} = 15 \text{ V}$ and $I = 300 \mu\text{A}$.
d. $V_{ac} = 100 \text{ V}$ and $I = 50 \mu\text{A}$.

Figure 17-11

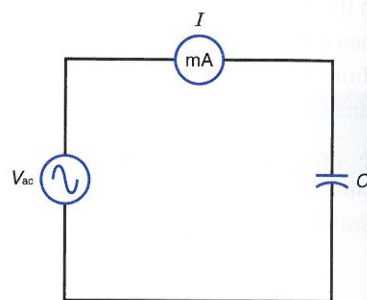

- 17-5 In Fig. 17-11, list three factors that can affect the amount of charge and discharge current flowing in the circuit.

SECTION 17-2 THE AMOUNT OF X_C EQUALS $\frac{1}{2\pi fC}$

- 17-6 Calculate the capacitive reactance, X_C , of a $0.1\text{-}\mu\text{F}$ capacitor at the following frequencies:
a. $f = 10 \text{ Hz}$.
b. $f = 50 \text{ Hz}$.
c. $f = 200 \text{ Hz}$.
d. $f = 10 \text{ kHz}$.
- 17-7 Calculate the capacitive reactance, X_C , of a $10\text{-}\mu\text{F}$ capacitor at the following frequencies:
a. $f = 60 \text{ Hz}$.
b. $f = 120 \text{ Hz}$.
c. $f = 500 \text{ Hz}$.
d. $f = 1 \text{ kHz}$.
- 17-8 What value of capacitance will provide an X_C of $1 \text{ k}\Omega$ at the following frequencies?
a. $f = 318.3 \text{ Hz}$.
b. $f = 1.591 \text{ kHz}$.
c. $f = 3.183 \text{ kHz}$.
d. $f = 6.366 \text{ kHz}$.
- 17-9 At what frequency will a $0.047\text{-}\mu\text{F}$ capacitor provide an X_C value of
a. $100 \text{ k}\Omega$?
b. $5 \text{ k}\Omega$?
c. $1.5 \text{ k}\Omega$?
d. 50Ω ?

- 17-10 How much is the capacitance of a capacitor that draws 2 mA of current from a 10-V ac generator whose frequency is 3.183 kHz ?

- 17-11 At what frequency will a 820-pF capacitance have an X_C value of 250Ω ?

- 17-12 A $0.01\text{-}\mu\text{F}$ capacitor draws 50 mA of current when connected directly across a 50-V ac source. What is the value of current drawn by the capacitor when
a. the frequency is doubled?
b. the frequency is decreased by one-half?
c. the capacitance is doubled to $0.02 \mu\text{F}$?
d. the capacitance is reduced by one-half to $0.005 \mu\text{F}$?

- 17-13 A capacitor has an X_C value of $10 \text{ k}\Omega$ at a given frequency. What is the new value of X_C when the frequency is
a. cut in half?
b. doubled?
c. quadrupled?
d. increased by a factor of 10?

- 17-14 Calculate the capacitive reactance, X_C , for the following capacitance and frequency values:
a. $C = 0.47 \mu\text{F}$, $f = 1 \text{ kHz}$.
b. $C = 100 \mu\text{F}$, $f = 120 \text{ Hz}$.
c. $C = 250 \text{ pF}$, $f = 1 \text{ MHz}$.
d. $C = 0.0022 \mu\text{F}$, $f = 50 \text{ kHz}$.

- 17-15 Determine the capacitance value for the following frequency and X_C values:
a. $X_C = 1 \text{ k}\Omega$, $f = 3.183 \text{ kHz}$.
b. $X_C = 200 \Omega$, $f = 63.66 \text{ kHz}$.
c. $X_C = 25 \text{ k}\Omega$, $f = 1.592 \text{ kHz}$.
d. $X_C = 1 \text{ M}\Omega$, $f = 100 \text{ Hz}$.

- 17-16 Determine the frequency for the following capacitance and X_C values:
a. $C = 0.05 \mu\text{F}$, $X_C = 4 \text{ k}\Omega$.
b. $C = 0.1 \mu\text{F}$, $X_C = 1.591 \text{ k}\Omega$.
c. $C = 0.0082 \mu\text{F}$, $X_C = 6.366 \text{ k}\Omega$.
d. $C = 50 \mu\text{F}$, $X_C = 100 \Omega$.


SECTION 17-3 SERIES OR PARALLEL CAPACITIVE REACTANCES

- 17-17 How much is the total capacitive reactance, X_{C_T} , for the following series capacitive reactances:
a. $X_{C_1} = 1 \text{ k}\Omega$, $X_{C_2} = 1.5 \text{ k}\Omega$, $X_{C_3} = 2.5 \text{ k}\Omega$.
b. $X_{C_1} = 500 \Omega$, $X_{C_2} = 1 \text{ k}\Omega$, $X_{C_3} = 1.5 \text{ k}\Omega$.
c. $X_{C_1} = 20 \text{ k}\Omega$, $X_{C_2} = 10 \text{ k}\Omega$, $X_{C_3} = 120 \text{ k}\Omega$.
d. $X_{C_1} = 340 \Omega$, $X_{C_2} = 570 \Omega$, $X_{C_3} = 2.09 \text{ k}\Omega$.
- 17-18 What is the equivalent capacitive reactance, $X_{C_{EQ}}$, for the following parallel capacitive reactances:
a. $X_{C_1} = 100 \Omega$ and $X_{C_2} = 400 \Omega$.
b. $X_{C_1} = 1.2 \text{ k}\Omega$ and $X_{C_2} = 1.8 \text{ k}\Omega$.
c. $X_{C_1} = 15 \Omega$, $X_{C_2} = 6 \Omega$, $X_{C_3} = 10 \Omega$.
d. $X_{C_1} = 2.5 \text{ k}\Omega$, $X_{C_2} = 10 \text{ k}\Omega$, $X_{C_3} = 2 \text{ k}\Omega$, $X_{C_4} = 1 \text{ k}\Omega$.

SECTION 17-4 OHM'S LAW APPLIED TO X_C

- 17-19 In Fig. 17-12, calculate the current, I .


Figure 17-12

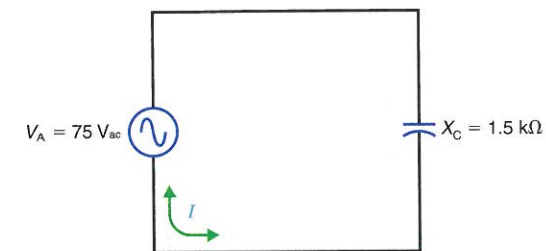

- 17-20 In Fig. 17-12, what happens to the current, I , when the frequency of the applied voltage
a. decrease?
b. increase?

- 17-21 In Fig. 17-13, solve for
a. X_{C_T} .
b. I .
c. V_{C_1} , V_{C_2} , and V_{C_3} .

Figure 17-13

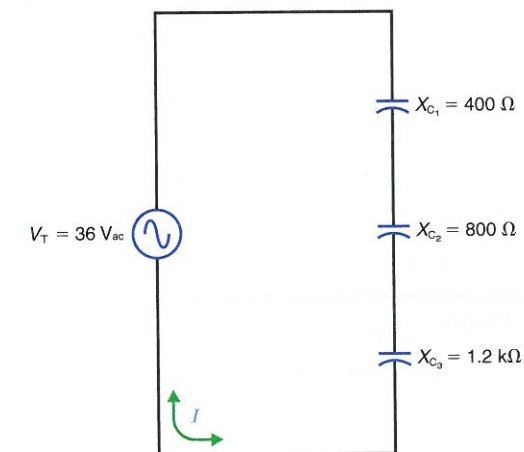

- 17-22 In Fig. 17-14, solve for
a. X_{C_1} , X_{C_2} , and X_{C_3} .
b. X_{C_T} .
c. I .
d. V_{C_1} , V_{C_2} , and V_{C_3} .
e. C_{EQ} .

- 17-23 In Fig. 17-13, solve for C_1 , C_2 , C_3 , and C_{EQ} if the applied voltage has a frequency of 318.3 Hz .

- 17-24 In Fig. 17-15, solve for
a. I_{C_1} , I_{C_2} , and I_{C_3} .
b. I_T .
c. $X_{C_{EQ}}$.