


- 18-23 With R set at $1\text{ k}\Omega$ in Fig. 18-21, solve for
 a. Z_T , I , V_R , V_C , and θ_Z .
 b. the phase relationship between V_T and V_R .
 c. the phase relationship between V_T and V_C .

- 18-24 With R set at $100\text{ k}\Omega$ in Fig. 18-21, solve for
 a. Z_T , I , V_R , V_C , and θ_Z .
 b. the phase relationship between V_T and V_R .
 c. the phase relationship between V_T and V_C .

SECTION 18-5 X_C AND R IN PARALLEL

- 18-25 In Fig. 18-22, how much voltage is across
 a. the $40\text{-}\Omega$ resistor, R ?
 b. the $30\text{-}\Omega$ capacitive reactance, X_C ?

Figure 18-22

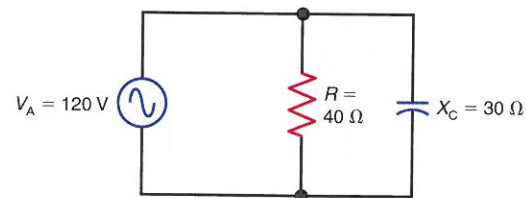


- 18-26 In Fig. 18-22, what is the phase relationship between
 a. V_A and I_R ?
 b. V_A and I_C ?
 c. I_C and I_R ?

- 18-27 In Fig. 18-22, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T .

- 18-28 Draw the phasor current triangle for the circuit in Fig. 18-22. (Use I_R as the reference phasor.)


- 18-29 In Fig. 18-23, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T .

Figure 18-23

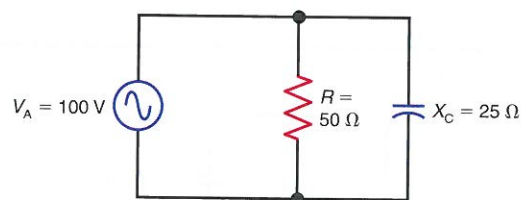


- 18-30 In Fig. 18-24, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T .

Figure 18-24

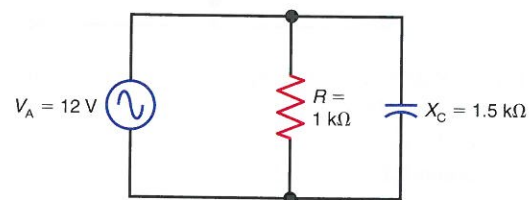


- 18-31 In Fig. 18-25, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T .

Figure 18-25

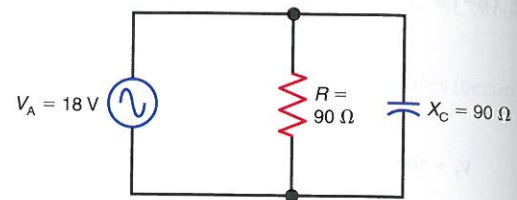

- 18-32 In Fig. 18-26, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T .


Figure 18-26

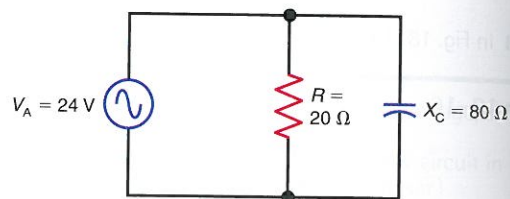

- 18-33 In Fig. 18-27, solve for I_R , I_C , I_T , Z_{EQ} , and θ_T for the following circuit values:

- a. $R = 50\text{ }\Omega$, $X_C = 50\text{ }\Omega$, and $V_A = 50\text{ V}$.
 b. $R = 10\text{ }\Omega$, $X_C = 100\text{ }\Omega$, and $V_A = 20\text{ V}$.
 c. $R = 100\text{ }\Omega$, $X_C = 10\text{ }\Omega$, and $V_A = 20\text{ V}$.


Figure 18-27

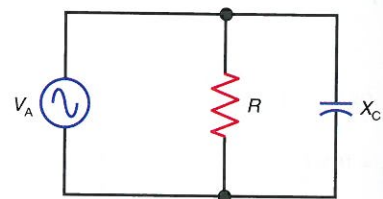

- 18-34 In Fig. 18-27, how much is Z_{EQ} if $R = 60\text{ }\Omega$ and $X_C = 80\text{ }\Omega$?

- 18-35 In Fig. 18-28, solve for X_C , I_R , I_C , I_T , Z_{EQ} , and θ_T .

Figure 18-28

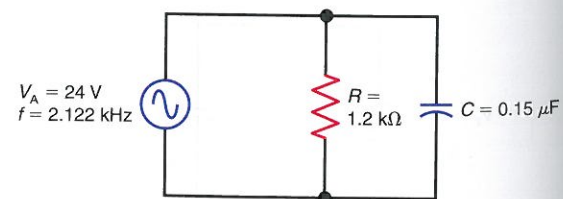

- 18-36 In Fig. 18-28, what happens to each of the following quantities if the frequency of the applied voltage increases?

- a. I_R .
 b. I_C .

- c. I_T .
 d. Z_{EQ} .
 e. θ_T .


- 18-37 Repeat Prob. 18-36 if the frequency of the applied voltage decreases.

SECTION 18-6 RF AND AF COUPLING CAPACITORS

- 18-38 In Fig. 18-29, calculate the minimum coupling capacitance, C_C , in series with the $1\text{-k}\Omega$ resistance, R , if the frequency of the applied voltage is

- a. 159.1 Hz .
 b. 1591 Hz .
 c. 15.91 kHz .

Figure 18-29

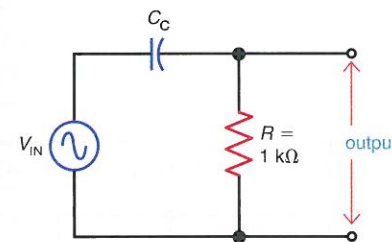


- 18-39 In Fig. 18-29, assume that $C_C = 0.047\text{ }\mu\text{F}$ and $R = 1\text{ k}\Omega$, as shown. For these values, what is the lowest frequency of the applied voltage that will provide an X_C of $100\text{ }\Omega$? At this frequency, what is the phase angle, θ_Z ?

SECTION 18-7 CAPACITIVE VOLTAGE DIVIDERS

- 18-40 In Fig. 18-30, calculate the following:


- a. X_{C1} , X_{C2} , X_{C3} , X_{C4} , and X_{C_T} .
 b. I .
 c. V_{C1} , V_{C2} , V_{C3} , and V_{C4} .

Figure 18-30

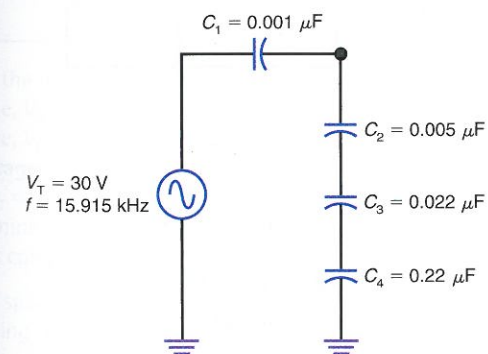

- 18-41 In Fig. 18-31, calculate V_{C1} , V_{C2} , and V_{C3} .


Figure 18-31

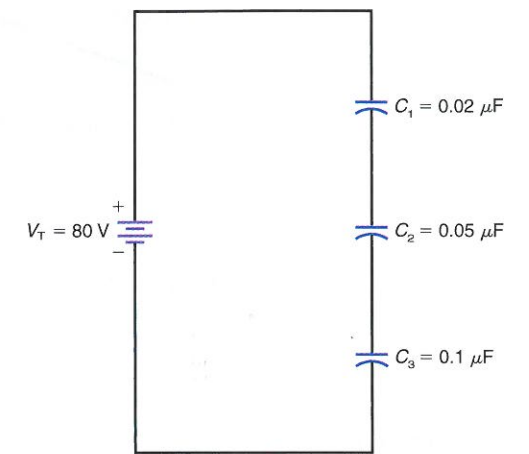

SECTION 18-8 THE GENERAL CASE OF CAPACITIVE CURRENT, i_C

- 18-42 For the waveshape of capacitor voltage, V_C , in Fig. 18-32, show the corresponding charge and discharge current, i_C , with values for a 200-pF capacitance.

Figure 18-32

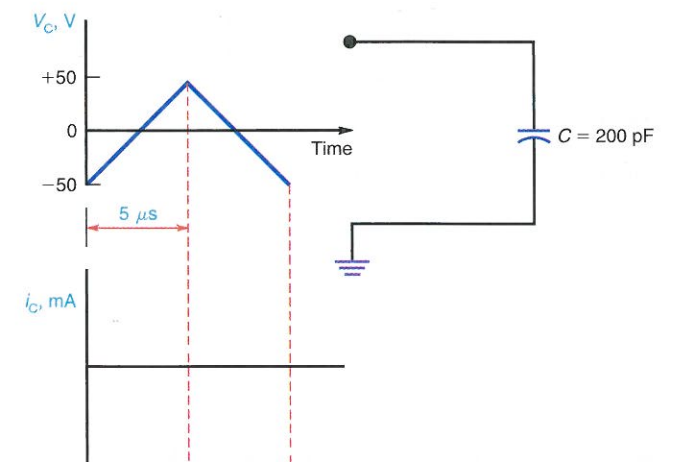

- 18-43 In Fig. 18-33, show the corresponding charge and discharge current for the waveshape of capacitor voltage shown.