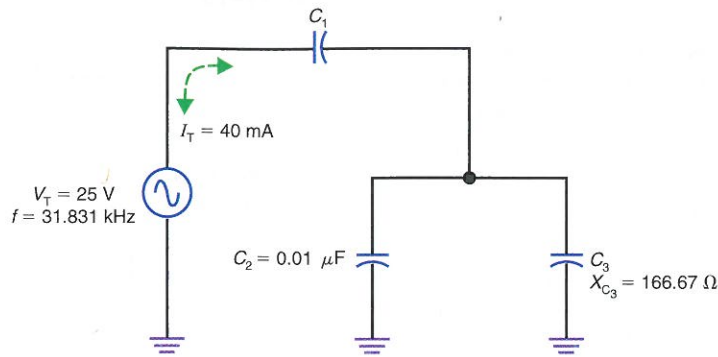


Figure 17-17 Circuit for Critical Thinking Prob. 17-35.



## Answers to Self-Reviews

17-1 a.  $0.1 \mu\text{F}$   
b.  $0.5 \mu\text{F}$

17-2 a.  $200 \Omega$   
b.  $800 \Omega$   
c. larger

17-3 a.  $500 \Omega$   
b.  $120 \Omega$

17-4 a.  $300 \Omega$   
b.  $66.7 \Omega$

17-5 a.  $50 \Omega$   
b.  $1000 \Omega$

17-6 a.  $90^\circ$   
b.  $0$  or  $360^\circ$   
c.  $90^\circ$

## Laboratory Application Assignment

In this lab application assignment you will examine how the capacitive reactance,  $X_C$ , of a capacitor decreases when the frequency,  $f$ , increases. You will also see that more capacitance,  $C$  at a given frequency results in less capacitive reactance,  $X_C$ . Finally, you will observe how  $X_C$  values combine in series and in parallel.

**Equipment:** Obtain the following items from your instructor.

- Function generator
- Assortment of capacitors
- DMM

### Capacitive Reactance, $X_C$

Refer to Fig. 17-18a. Calculate and record the value of  $X_C$  for each of the following frequencies listed below. Calculate  $X_C$  as  $1/(2\pi fC)$ .

$X_C = \underline{\hspace{2cm}}$  @  $f = 100 \text{ Hz}$   
 $X_C = \underline{\hspace{2cm}}$  @  $f = 200 \text{ Hz}$   
 $X_C = \underline{\hspace{2cm}}$  @  $f = 400 \text{ Hz}$

Connect the circuit in Fig. 17-18a. Set the voltage source to exactly  $5 \text{ V}_{\text{rms}}$ . For each of the following frequencies listed below, measure and record the current,  $I$ . (Use a DMM to measure  $I$ .)

Next, calculate  $X_C$  as  $V/I$ .

$I = \underline{\hspace{2cm}}$  @  $f = 100 \text{ Hz}$ ;  $X_C = \underline{\hspace{2cm}}$   
 $I = \underline{\hspace{2cm}}$  @  $f = 200 \text{ Hz}$ ;  $X_C = \underline{\hspace{2cm}}$   
 $I = \underline{\hspace{2cm}}$  @  $f = 400 \text{ Hz}$ ;  $X_C = \underline{\hspace{2cm}}$

How do the experimental values of  $X_C$  compare to those initially calculated? \_\_\_\_\_  
 Based on your experimental values, what happens to the value of  $X_C$  each time the frequency,  $f$ , is doubled? \_\_\_\_\_

Figure 17-18

