

11. The measured voltage across an unloaded secondary of a transformer is usually

- the same as the rated secondary voltage.
- 5 to 10% higher than the rated secondary voltage.
- 50% higher than the rated secondary voltage.
- 5 to 10% lower than the rated secondary voltage.

12. A laminated iron-core transformer has reduced eddy-current losses because

- the laminations are stacked vertically.
- more wire can be used with less dc resistance.
- the magnetic flux is in the air gap of the core.
- the laminations are insulated from each other.

13. How much is the inductance of a coil that induces 50 V when its current changes at the rate of 500 A/s?

- 100 mH.
- 1 H.
- 100  $\mu$ H.
- 10  $\mu$ H.

14. A 100-mH inductor is in parallel with a 150-mH and a 120-mH inductor. Assuming no mutual

inductance between coils, how much is  $L_{eq}$ ?

- 400 mH.
- 370 mH.
- 40 mH.
- 80 mH.

15. A 400- $\mu$ H coil is in series with a 1.2-mH coil without mutual inductance. How much is  $L_T$ ?

- 401.2  $\mu$ H.
- 300  $\mu$ H.
- 160  $\mu$ H.
- 1.6 mH.

16. A step-down transformer has a turns ratio,  $\frac{N_p}{N_s}$ , of 4:1. If the primary voltage,  $V_p$ , is 120 Vac, how much is the secondary voltage,  $V_s$ ?

- 480 Vac.
- 120 Vac.
- 30 Vac.
- It cannot be determined.

17. If an iron-core transformer has a turns ratio,  $\frac{N_p}{N_s}$ , of 3:1 and  $Z_s = 16 \Omega$ , how much is  $Z_p$ ?

- 48  $\Omega$ .
- 144  $\Omega$ .

- 1.78  $\Omega$ .
- 288  $\Omega$ .

18. How much is the induced voltage,  $V_L$ , across a 5-H inductor carrying a steady dc current of 200 mA?

- 0 V.
- 1 V.
- 100 kV.
- 120 Vac.

19. The secondary current,  $I_s$ , in an iron-core transformer equals 1.8 A.

If the turns ratio,  $\frac{N_p}{N_s}$ , equals 3:1,

how much is the primary current,  $I_p$ ?

- $I_p = 1.8$  A.
- $I_p = 600$  mA.
- $I_p = 5.4$  A.
- none of the above.

20. For a coil, the dc resistance,  $r_i$ , and inductance,  $L$ , are

- in parallel.
- infinite.
- the same thing.
- in series.

## Problems

### SECTION 19-1 INDUCTION BY ALTERNATING CURRENT

19-1 Which can induce more voltage in a conductor, a steady dc current of 10 A or a small current change of 1 to 2 mA?

19-2 Examine the sine wave of alternating current in Fig. 19-1. Identify the points on the waveform (using the letters A-I) where the rate of current change,  $\frac{di}{dt}$ , is

- greatest.
- zero.

19-3 Which will induce more voltage across a conductor, a low-frequency alternating current or a high-frequency alternating current?

### SECTION 19-2 SELF-INDUCTANCE L

19-4 Convert the following current changes,  $\frac{di}{dt}$ , to amperes per second:

- 0 to 3 A in 2 s.
- 0 to 50 mA in 5  $\mu$ s.
- 100 to 150 mA in 5 ms.
- 150 to 100 mA in 20  $\mu$ s.
- 30 to 35 mA in 1  $\mu$ s.
- 80 to 96 mA in 0.4  $\mu$ s.
- 10 to 11 A in 1 s.

19-5 How much inductance,  $L$ , will be required to produce an induced voltage,  $V_L$ , of 15 V for each of the  $\frac{di}{dt}$  values listed in Prob. 19-4?

19-6 How much is the inductance,  $L$ , of a coil that induces 75 V when the current changes at the rate of 2500 A/s?

19-7 How much is the inductance,  $L$ , of a coil that induces 20 V when the current changes at the rate of 400 A/s?

19-8 Calculate the inductance,  $L$ , for the following long coils: (Note: 1 m = 100 cm and 1 m<sup>2</sup> = 10,000 cm<sup>2</sup>.)

- air core, 20 turns, area 3.14 cm<sup>2</sup>, length 25 cm.
- same coil as step a with ferrite core having a  $\mu_r$  of 5000.
- air core, 200 turns, area 3.14 cm<sup>2</sup>, length 25 cm.
- air core, 20 turns, area 3.14 cm<sup>2</sup>, length 50 cm.
- iron core with  $\mu_r$  of 2000, 100 turns, area 5 cm<sup>2</sup>, length 10 cm.

19-9 Recalculate the inductance,  $L$ , in Prob. 19-8a if the number of turns is doubled to 40.

19-10 What is another name for an rf inductor?

### SECTION 19-3 SELF-INDUCED VOLTAGE $V_L$

19-11 How much is the self-induced voltage across a 5-H inductance produced by a current change of 100 to 200 mA in 1 ms?

19-12 How much is the self-induced voltage across a 33-mH inductance when the current changes at the rate of 1500 A/s?

19-13 Calculate the self-induced voltage across a 100-mH inductor for the following values of  $\frac{di}{dt}$ :

- 100 A/s.
- 200 A/s.
- 50 A/s.
- 1000 A/s.

### SECTION 19-5 MUTUAL INDUCTANCE $L_M$

19-14 A coil,  $L_1$ , produces 200  $\mu$ Wb of magnetic flux. A nearby coil,  $L_2$ , is linked with  $L_1$  by 50  $\mu$ Wb of magnetic flux. What is the coefficient of coupling,  $k$ , between  $L_1$  and  $L_2$ ?

19-15 A coil,  $L_1$ , produces 40  $\mu$ Wb of magnetic flux. A coil,  $L_2$ , nearby, is linked with  $L_1$  by 30  $\mu$ Wb of magnetic flux. What is the value of  $k$ ?

19-16 Two 50-mH coils,  $L_1$  and  $L_2$ , have a coefficient of coupling,  $k$ , equal to 0.6. Calculate  $L_M$ .

19-17 Two inductors,  $L_1$  and  $L_2$ , have a coefficient of coupling,  $k$ , equal to 0.5.  $L_1 = 100$  mH and  $L_2 = 150$  mH. Calculate  $L_M$ .


19-18 What is the assumed value of  $k$  for an iron-core transformer?

### SECTION 19-6 TRANSFORMERS

19-19 In Fig. 19-35, solve for

- the secondary voltage,  $V_s$ .
- the secondary current,  $I_s$ .
- the secondary power,  $P_{sec}$ .
- the primary power,  $P_{pri}$ .
- the primary current,  $I_p$ .

Figure 19-35

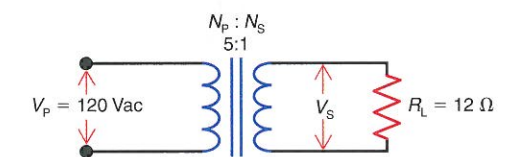

19-20 Repeat Prob. 19-19 if  $N_p:N_s = 10:1$ .

19-21 In Fig. 19-36, solve for

- $V_{s1}$  (secondary 1 voltage).
- $V_{s2}$  (secondary 2 voltage).
- $I_{s1}$  (secondary 1 current).
- $I_{s2}$  (secondary 2 current).
- $P_{sec1}$ .
- $P_{sec2}$ .
- $P_{pri}$ .
- $I_p$ .

## Essay Questions

- Define 1 H of self-inductance and 1 H of mutual inductance.
- State Lenz's law in terms of induced voltage produced by varying current.
- Refer to Fig. 19-5. Explain why the polarity of  $v_L$  is the same for the examples in Fig. 19-5a and d.
- Make a schematic diagram showing the primary and secondary of an iron-core transformer with a 1:6 voltage step-up ratio (a) using an autotransformer; (b) using a transformer with isolated secondary winding. Then (c) with 100 turns in the primary, how many turns are in the secondary for both cases?
- Define the following: coefficient of coupling, transformer efficiency, stray inductance, and eddy-current losses.
- Why are eddy-current losses reduced with the following cores: (a) laminated; (b) powdered iron; (c) ferrite?
- Why is a good conductor used for an rf shield?
- Show two methods of providing a variable inductance.
- (a) Why will the primary of a power transformer have excessive current if the secondary is short-circuited? (b) Why is there no voltage across the secondary if the primary is open?
- (a) Describe briefly how to check a coil for an open winding with an ohmmeter. Which ohmmeter range should be used? (b) Which leads will be checked on an autotransformer with one secondary and a transformer with two isolated secondary windings?
- Derive the formula  $L_M = (L_s - L_T)/4$  from the fact that  $L_T = L_1 + L_2 + 2L_M$  and  $L_s = L_1 + L_2 - 2L_M$ .
- Explain how a transformer with a 1:1 turns ratio and an isolated secondary can be used to reduce the chance of electric shock from the 120-Vac power line.
- Explain the terms *stray inductance* and *stray capacitance* and give an example of each.