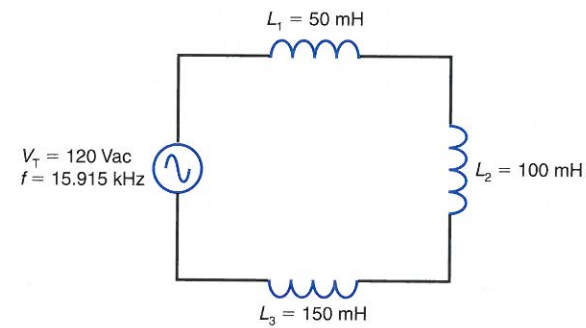



Figure 20-13



20-25 In Fig. 20-14, solve for

- I_{L_1} , I_{L_2} , and I_{L_3} .
- I_T .
- $X_{L_{EQ}}$.

Figure 20-14

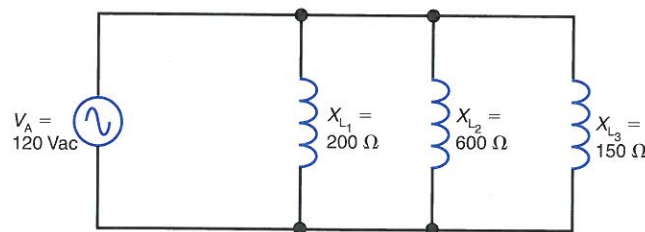


20-26 In Fig. 20-14, solve for L_1 , L_2 , L_3 , and L_T if the frequency of the applied voltage is 6.366 kHz.

20-27 In Fig. 20-15, solve for

- X_{L_1} , X_{L_2} , and X_{L_3} .
- I_{L_1} , I_{L_2} , and I_{L_3} .

- I_T .
- $X_{L_{EQ}}$.
- L_{EQ} .

Figure 20-15

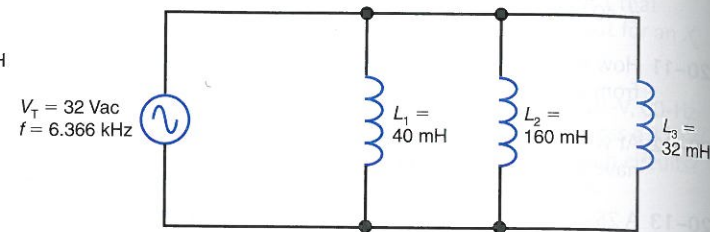

SECTION 20-5 APPLICATIONS OF X_L FOR DIFFERENT FREQUENCIES

20-28 Calculate the value of inductance, L , required to produce an X_L value of 500Ω at the following frequencies:

- $f = 250 \text{ Hz}$.
- $f = 636.6 \text{ Hz}$.
- $f = 3.183 \text{ kHz}$.
- $f = 7.957 \text{ kHz}$.

SECTION 20-6 WAVESHAPES OF V_L INDUCED BY SINE-WAVE CURRENT

20-29 For an inductor, what is the phase relationship between the induced voltage, V_L , and the inductor current, I_L ? Explain your answer.

20-30 For a sine wave of alternating current flowing through an inductor, at what angles in the cycle will the induced voltage be

- maximum?
- zero?


Critical Thinking

20-31 In Fig. 20-16, calculate L_1 , L_2 , L_3 , I_T , X_{L_1} , X_{L_2} , X_{L_3} , V_{L_1} , V_{L_2} , V_{L_3} , I_{L_1} , and I_{L_3} .

20-32 Two inductors in series without L_M have a total inductance L_T of $120 \mu\text{H}$. If $L_1/L_2 = 1/20$, what are the values for L_1 and L_2 ?

20-33 Three inductors in parallel have an equivalent inductance L_{EQ} of 7.5 mH . If $L_2 = 3 L_3$ and $L_3 = 4 L_1$, calculate L_1 , L_2 , and L_3 .

Figure 20-16 Circuit for Critical Thinking Prob. 20-31.

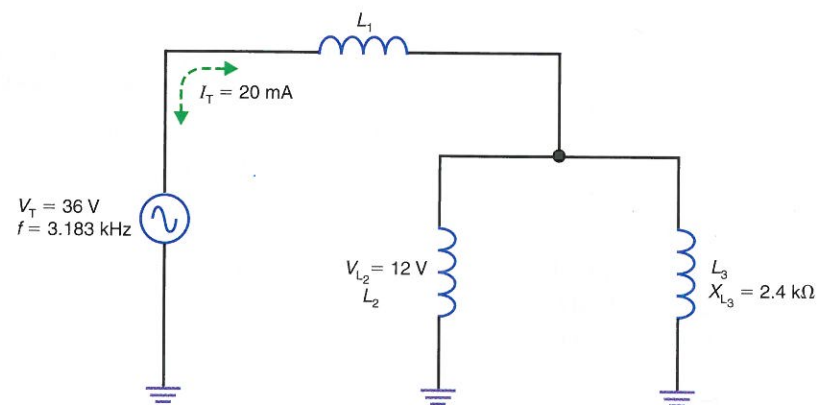

Answers to Self-Reviews

- 20-1 a. 0Ω
b. 1000Ω
- 20-2 a. 628Ω
b. 314Ω
c. 6280Ω
- 20-3 a. 500Ω
b. 120Ω

- 20-4 a. 0.5 A
b. 100 V
- 20-5 a. 100 MHz
b. 2000Ω
- 20-6 a. 90°
b. 0° or 360°
c. 90°

Laboratory Application Assignment

In this lab application assignment you will examine how the inductive reactance, X_L , of an inductor increases when the frequency, f , increases. You will also see that more inductance, L , at a given frequency results in more inductive reactance, X_L . Finally, you will observe how X_L values combine in series and in parallel.

Equipment: Obtain the following items from your instructor.

- Function generator
- 33-mH and 100-mH inductors
- DMM

DC Resistance, r_i , of a Coil

With a DMM, measure and record the dc resistance of each inductor. Set the DMM to the lowest resistance range when measuring r_i .

$$r_i = \text{_____} (33 \text{ mH})$$

$$r_i = \text{_____} (100 \text{ mH})$$

Inductive Reactance, X_L

Refer to Fig. 20-17a. Calculate and record the value of X_L for each of the following frequencies listed below. Calculate X_L as $2\pi fL$.

$$X_L = \text{_____} @ f = 500 \text{ Hz}$$

$$X_L = \text{_____} @ f = 1 \text{ kHz}$$

$$X_L = \text{_____} @ f = 2 \text{ kHz}$$

Connect the circuit in Fig. 20-17a. Set the voltage source to exactly 5 Vrms. For each of the following frequencies listed below, measure and record the current, I . (Use a DMM to measure I) Next, calculate X_L as V/I .


$$I = \text{_____} @ f = 500 \text{ Hz}; X_L = \text{_____}$$

$$I = \text{_____} @ f = 1 \text{ kHz}; X_L = \text{_____}$$

$$I = \text{_____} @ f = 2 \text{ kHz}; X_L = \text{_____}$$

How do the experimental values of X_L compare to the calculated values? _____
Based on your experimental values, what happens to the value of X_L every time the frequency, f , doubles? _____
Is X_L proportional or inversely proportional to the frequency, f ? _____

Figure 20-17

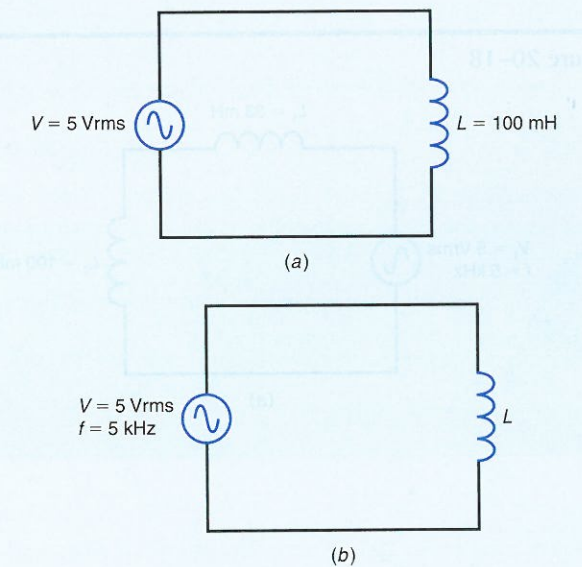

Refer to Fig. 20-17b. With the frequency, f , set to 5 kHz, calculate and record the value of X_L for each of the following inductance values listed below. Calculate X_L as $2\pi fL$.

$$X_L = \text{_____} \text{ when } L = 33 \text{ mH}$$

$$X_L = \text{_____} \text{ when } L = 100 \text{ mH}$$

Connect the circuit in Fig. 20-17b. Adjust the frequency, f , of the function generator to exactly 5 kHz. For each inductance value listed below, measure and record the current, I . (Use a DMM to measure I) Next, calculate X_L as V/I .

$$I = \text{_____} \text{ when } L = 33 \text{ mH}; X_L = \text{_____}$$

$$I = \text{_____} \text{ when } L = 100 \text{ mH}; X_L = \text{_____}$$

Is X_L proportional or inversely proportional to the value of inductance? _____

Did the dc resistance, r_i , of the inductors affect any of your measurements? _____
If so, explain. _____