

13. The dividing line for calculating the value of a choke inductance is to make

- X_L 10 or more times larger than the series R .
- X_L one-tenth or less than the series R .
- X_L equal to R .
- R 10 or more times larger than the series X_L .

14. The Q of a coil is affected by

- frequency.
- the resistance of the coil.

- skin effect.
- all of the above.

15. If the current through a 300-mH coil increases at the linear rate of 50 mA per 10 μ s, how much is the induced voltage, V_L ?

- 1.5 V.
- 1.5 kV.

- This is impossible to determine because X_L is unknown.
- This is impossible to determine because V_L also increases at a linear rate.

Essay Questions

- What characteristic of the current in an inductance determines the amount of induced voltage? State briefly why.
- Draw a schematic diagram showing an inductance connected across a sine-wave voltage source, and indicate the current and voltage that are 90° out of phase with one another.
- Why is the voltage across a resistance in phase with the current through the resistance?
- (a) Draw the sine waveforms for two voltages 90° out of phase, each with a peak value of 100 V. (b) Why does their phasor sum equal 141 V and not 200 V? (c) When will the sum of two 100-V drops in series equal 200 V?
- (a) Define the phase angle of a sine-wave ac circuit. (b) State the formula for the phase angle in a circuit with X_L and R in series.
- Define the following: (a) Q of a coil; (b) ac effective resistance; (c) rf choke; (d) sawtooth current.
- Why do all waveshapes in Fig. 21-2b have the same frequency?
- Describe how to check the trouble of an open choke with an ohmmeter.
- Redraw the circuit and graph in Fig. 21-11 for a sawtooth current with a peak of 30 mA.
- Why is the R_e of a coil considered resistance rather than reactance?
- Why are rf chokes usually smaller than af chokes?
- What is the waveshape of v_L for a sine wave i_L ?


Problems

SECTION 21-1 SINE WAVE i_L LAGS v_L BY 90°

21-1 In Fig. 21-12, what is the

- peak value of the inductor voltage, V_L ?
- peak value of the inductor current, i_L ?
- frequency of the inductor current, i_L ?
- phase relationship between V_L and i_L ?

Figure 21-12

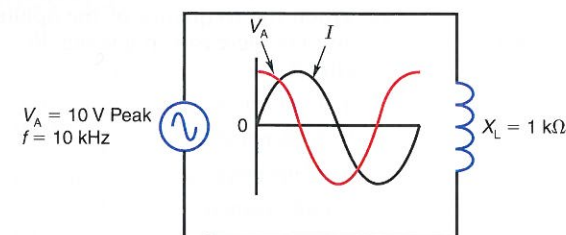

21-2 In Fig. 21-12, what is the value of the induced voltage, V_L , when i_L is at

- 0 mA?
- its positive peak of 10 mA?
- its negative peak of 10 mA?

21-3 In Fig. 21-12, draw the phasors representing V_L and i_L using


- i_L as the reference phasor.
- V_L as the reference phasor.

SECTION 21-2 X_L AND R IN SERIES

21-4 In Fig. 21-13, how much current, I , is flowing

- through the 15- Ω resistor, R ?
- through the 20- Ω inductive reactance, X_L ?
- to and from the terminals of the applied voltage, V_T ?

Figure 21-13

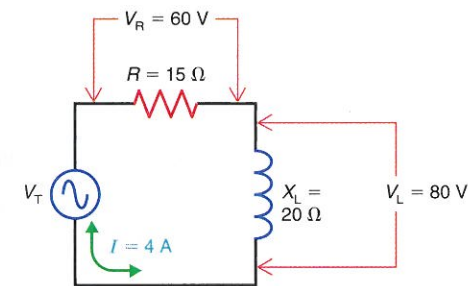

21-5 In Fig. 21-13, what is the phase relationship between

- I and V_R ?
- I and V_L ?
- V_L and V_R ?


21-6 In Fig. 21-13, how much is the applied voltage, V_T ?

21-7 Draw the phasor voltage triangle for the circuit in Fig. 21-13. (Use V_R as the reference phasor.)

21-8 In Fig. 21-14, solve for

- the resistor voltage, V_R .
- the inductor voltage, V_L .
- the total voltage, V_T .


Figure 21-14

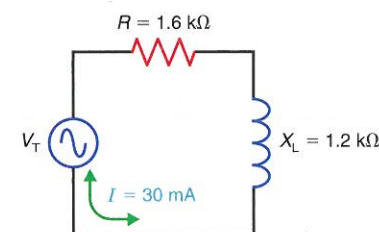

21-9 In Fig. 21-15, solve for

- the resistor voltage, V_R .
- the inductor voltage, V_L .
- the total voltage, V_T .

Figure 21-15

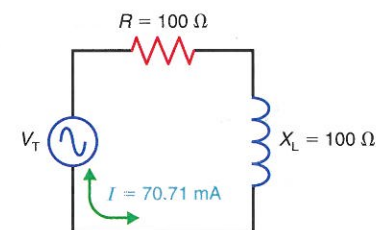


21-10 In a series RL circuit, solve for the applied voltage, V_T , if

- $V_R = 12$ V and $V_L = 6$ V.
- $V_R = 25$ V and $V_L = 40$ V.
- $V_R = 9$ V and $V_L = 16$ V.
- $V_R = 40$ V and $V_L = 40$ V.

SECTION 21-3 IMPEDANCE Z TRIANGLE

21-11 In Fig. 21-16, solve for Z_T , I , V_L , V_R , and θ_Z .


Figure 21-16

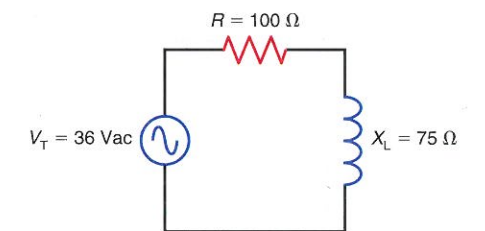

21-12 Draw the impedance triangle for the circuit in Fig. 21-16. (Use R as the reference phasor.)


21-13 In Fig. 21-17, solve for Z_T , I , V_L , V_R , and θ_Z .

Figure 21-17

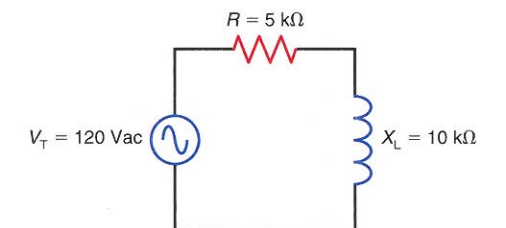

21-14 In Fig. 21-18, solve for Z_T , I , V_L , V_R , and θ_Z .

Figure 21-18

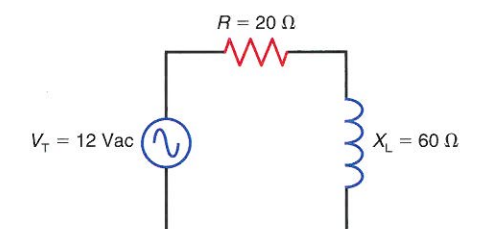

21-15 In Fig. 21-19, solve for Z_T , I , V_L , V_R , and θ_Z .

Figure 21-19

