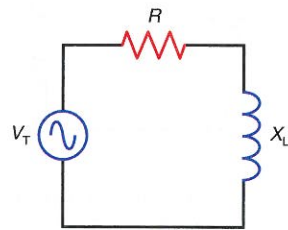


21-16 In Fig. 21-20, solve for Z_T , I , V_L , V_R , and θ_Z for the following circuit values:


- $X_L = 30 \Omega$, $R = 40 \Omega$, and $V_T = 50 \text{ V}$.
- $X_L = 50 \Omega$, $R = 50 \Omega$, and $V_T = 141.4 \text{ V}$.
- $X_L = 10 \Omega$, $R = 100 \Omega$, and $V_T = 10 \text{ V}$.
- $X_L = 100 \Omega$, $R = 10 \Omega$, and $V_T = 10 \text{ V}$.

Figure 21-20



21-17 In Fig. 21-21, solve for X_L , Z_T , I , V_R , V_L , and θ_Z .

Figure 21-21

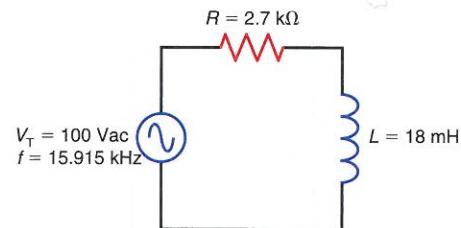

21-18 In Fig. 21-21, what happens to each of the following quantities if the frequency of the applied voltage increases?

- X_L .
- Z_T .
- I .
- V_R .
- V_L .
- θ_Z .


21-19 Repeat Prob. 21-18 if the frequency of the applied voltage decreases.

SECTION 21-4 X_L AND R IN PARALLEL

21-20 In Fig. 21-22, how much voltage is across

- the $30\text{-}\Omega$ resistor, R ?
- the $40\text{-}\Omega$ inductive reactance, X_L ?

Figure 21-22

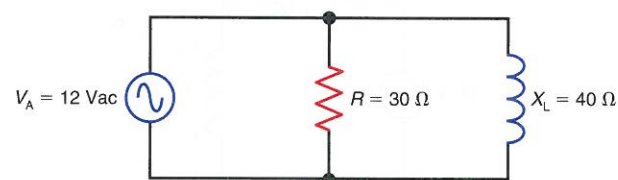

21-21 In Fig. 21-22, what is the phase relationship between


- V_A and I_R ?
- V_A and I_L ?
- I_L and I_R ?

21-22 In Fig. 21-22, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T .

21-23 Draw the phasor current triangle for the circuit in Fig. 21-22. (Use I_R as the reference phasor.)


21-24 In Fig. 21-23, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T .

Figure 21-23

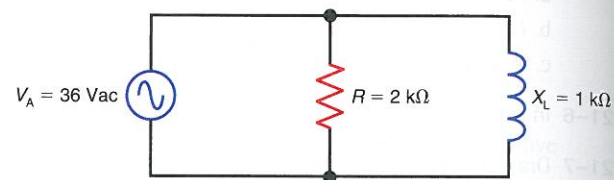


21-25 In Fig. 21-24, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T .

Figure 21-24

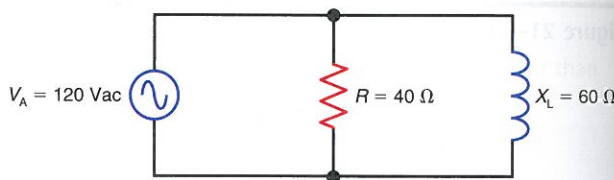


21-26 In Fig. 21-25, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T .

Figure 21-25

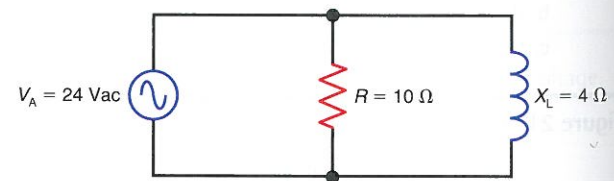

21-27 In Fig. 21-26, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T .


Figure 21-26

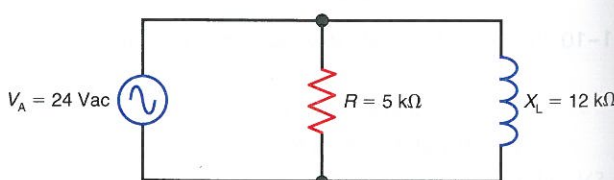

21-28 In Fig. 21-27, solve for I_R , I_L , I_T , Z_{EQ} , and θ_T for the following circuit values?

- $R = 50 \Omega$, $X_L = 50 \Omega$, and $V_A = 50 \text{ V}$.
- $R = 10 \Omega$, $X_L = 100 \Omega$, and $V_A = 20 \text{ V}$.
- $R = 100 \Omega$, $X_L = 10 \Omega$, and $V_A = 20 \text{ V}$.


Figure 21-27

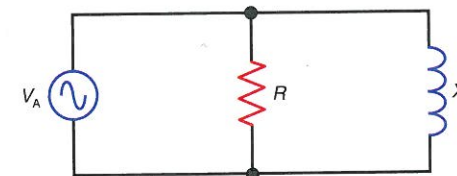

21-29 In Fig. 21-27, how much is Z_{EQ} if $R = 320 \Omega$ and $X_L = 240 \Omega$?

21-30 In Fig. 21-28, solve for X_L , I_R , I_L , I_T , Z_{EQ} , and θ_T .

Figure 21-28

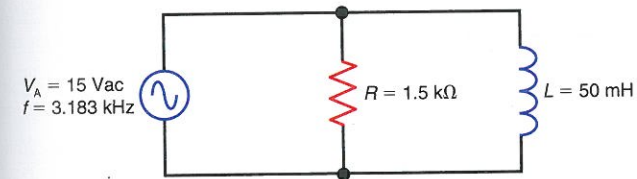

21-31 In Fig. 21-28, what happens to each of the following quantities if the frequency of the applied voltage increases?

- I_R .
- I_L .
- I_T .
- Z_{EQ} .
- θ_T .


21-32 Repeat Prob. 21-31 if the frequency of the applied voltage decreases.

SECTION 21-5 Q OF A COIL

21-33 For the inductor shown in Fig. 21-29, calculate the Q for the following frequencies:

- $f = 500 \text{ Hz}$.
- $f = 1 \text{ kHz}$.
- $f = 1.592 \text{ kHz}$.
- $f = 10 \text{ kHz}$.

Figure 21-29

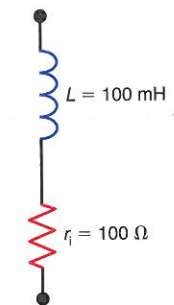

21-34 Why can't the Q of a coil increase without limit as the value of X_L increases for higher frequencies?

21-35 Calculate the ac effective resistance, R_e , of a $350\text{-}\mu\text{H}$ inductor whose Q equals 35 at 1.5 MHz.


21-36 Recalculate the value of R_e in Prob. 21-35 if the value of Q decreases to 25 at 5 MHz.

SECTION 21-6 AF AND RF CHOKES

21-37 In Fig. 21-30, calculate the required value of the choke inductance, L , at the following frequencies:

- $f = 500 \text{ Hz}$.
- $f = 2.5 \text{ kHz}$.
- $f = 200 \text{ kHz}$.
- $f = 1 \text{ MHz}$.

Figure 21-30

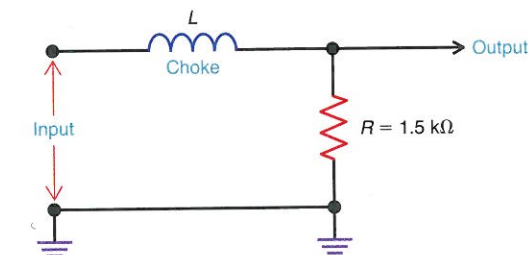

21-38 If $L = 50 \text{ mH}$ in Fig. 21-30, then what is the lowest frequency at which L will serve as a choke?

21-39 In Fig. 21-30 assume that the input voltage equals 10 V peak-to-peak for all frequencies. If $L = 150 \text{ mH}$, then calculate V_{out} for the following frequencies:

- 159.2 Hz.
- 1.592 kHz.
- 15.92 kHz.

SECTION 21-7 THE GENERAL CASE OF INDUCTIVE VOLTAGE

21-40 In Fig. 21-31, draw the waveform of induced voltage, V_L , across the 8-mH inductor for the triangular current waveform shown.

21-41 In Fig. 21-32, draw the waveform of induced voltage, V_L , across the 250-mH inductor for the sawtooth current waveform shown.