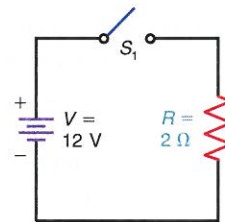


Problems

SECTION 22-1 RESPONSE OF RESISTANCE ALONE

22-1 In Fig. 22-13, how long does it take for the current, I , to reach its steady-state value after S_1 is closed?

Figure 22-13




22-2 In Fig. 22-13, what is the current with S_1 closed?

22-3 Explain how the resistor in Fig. 22-13 reacts to the closing or opening of S_1 .

SECTION 22-2 L/R TIME CONSTANT

- 22-4 In Fig. 22-14,
- what is the time constant of the circuit with S_1 closed?
 - what is the eventual steady-state current with S_1 closed?
 - what is the value of the circuit current at the first instant S_1 is closed? ($t = 0$ s)
 - what is the value of the circuit current exactly one time constant after S_1 is closed?
 - how long after S_1 is closed will it take before the circuit current reaches its steady-state value?

Figure 22-14

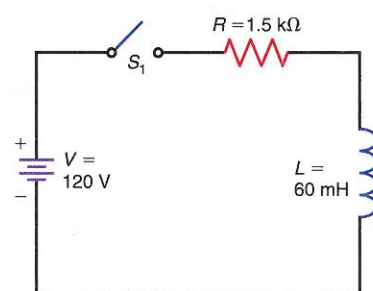

22-5 Repeat Prob. 22-4 if $L = 100$ mH and $R = 500$ Ω.

22-6 Calculate the time constant for an inductive circuit with the following values:

- $L = 10$ H, $R = 1$ kΩ.
- $L = 500$ mH, $R = 2$ kΩ.
- $L = 250$ μH, $R = 50$ Ω.
- $L = 15$ mH, $R = 7.5$ kΩ.

22-7 List two ways to

- increase the time constant of an inductive circuit.
- decrease the time constant of an inductive circuit.

SECTION 22-3 HIGH VOLTAGE PRODUCED BY OPENING AN RL CIRCUIT

22-8 Assume that the switch, S_1 , in Fig. 22-14 has been closed for more than five L/R time constants. If a 1-MΩ resistor is placed across the terminals of the switch, calculate

- the approximate time constant of the circuit with S_1 open.
- the peak inductor voltage, V_L , when S_1 is opened.
- the di/dt value at the instant S_1 is opened.
- how long it takes for the current to decay to zero after S_1 is opened (approximately).


22-9 Without a resistor across S_1 in Fig. 22-14, is it possible to calculate the time constant of the circuit with the switch open? Also, what effect will probably occur inside the switch when it is opened?

SECTION 22-4 RC TIME CONSTANT

22-10 In Fig. 22-15, what is the time constant of the circuit with the switch, S_1 , in Position

- 1?
- 2?

Figure 22-15

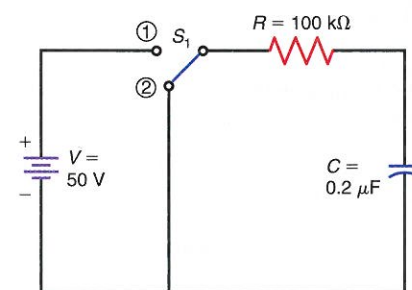

22-11 Assume that the capacitor in Fig. 22-15 is fully discharged with S_1 in Position 2. How much is the capacitor voltage, V_C ,

- exactly one time constant after S_1 is moved to Position 1?
- five time constants after S_1 is moved to Position 1?
- 1 week after S_1 is moved to Position 1?

22-12 Assume that the capacitor in Fig. 22-15 is fully charged with S_1 in Position 1. How much is the capacitor voltage, V_C ,

- exactly one time constant after S_1 is moved to Position 2?
- five time constants after S_1 is moved to Position 2?
- 1 week after S_1 is moved to Position 2?

22-13 Calculate the time constant of a capacitive circuit with the following values:

- $R = 1$ MΩ, $C = 1$ μF.
- $R = 150$ Ω, $C = 0.01$ μF.
- $R = 330$ kΩ, $C = 270$ pF.
- $R = 5$ kΩ, $C = 40$ μF.

22-14 List two ways to

- increase the time constant of a capacitive circuit.
- decrease the time constant of a capacitive circuit.

22-15 Assume that the capacitor in Fig. 22-15 is discharging from 50 V with S_1 in Position 2. At the instant the capacitor voltage reaches 25 V, S_1 is moved back to Position 1. What is

- the net charging voltage at the first instant S_1 is put back in Position 1?
- the value of the capacitor voltage exactly one time constant after S_1 is moved back to Position 1?
- the value of the capacitor voltage five time constants after S_1 is moved back to Position 1?

22-16 Assume that the capacitor in Fig. 22-15 is charging from 0 V with S_1 in Position 1. At the instant the capacitor voltage reaches 35 V, S_1 is moved back to Position 2. What is

- the value of the capacitor voltage exactly one time constant after S_1 is moved back to Position 2?
- the value of the capacitor voltage five time constants after S_1 is moved back to Position 2?

SECTION 22-5 RC CHARGE AND DISCHARGE CURVES

22-17 Assume that the capacitor in Fig. 22-15 is fully discharged with S_1 in Position 2. What is

- the value of the charging current at the first instant S_1 is moved to Position 1?
- the value of the charging current five time constants after S_1 is moved to Position 1?
- the value of the resistor voltage exactly one time constant after S_1 is moved to Position 1?
- the value of the charging current exactly one time constant after S_1 is moved to Position 1?

22-18 Assume that the capacitor in Fig. 22-15 is fully charged to 50 V with S_1 in Position 1. What is the value of the discharge current


- at the first instant S_1 is moved to Position 2?
- exactly one time constant after S_1 is moved to Position 2?
- five time constants after S_1 is moved to Position 2?

SECTION 22-6 HIGH CURRENT PRODUCED BY SHORT-CIRCUITING AN RC CIRCUIT

22-19 In Fig. 22-16, what is the RC time constant with S_1 in Position

- 1?
- 2?

Figure 22-16

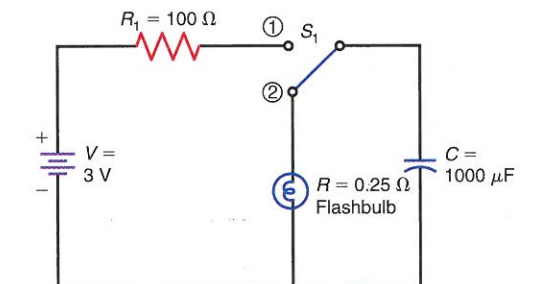

22-20 In Fig. 22-16, how long will it take the capacitor voltage to

- reach 3 V after S_1 is moved to Position 1?
- discharge to 0 V after S_1 is moved to Position 2?

22-21 Assume that the capacitor in Fig. 22-16 is fully discharged with S_1 in Position 2. At the first instant S_1 is moved to Position 1, how much is

- the voltage across the capacitor?
- the voltage across the resistor?
- the initial charging current?

22-22 Assume that the capacitor in Fig. 22-16 is fully charged with S_1 in Position 1. At the first instant S_1 is moved to Position 2, what is

- the dc voltage across the flashbulb?
- the initial value of the discharge current?
- the initial rate of voltage change, dv/dt ?

22-23 How much energy is stored by the capacitor in Fig. 22-16 if it is fully charged to 3 V?

SECTION 22-7 RC WAVESHAPES

22-24 For the circuit in Fig. 22-17,

- calculate the RC time constant.
- draw the capacitor voltage waveform and include voltage values at times t_0 , t_1 , t_2 , t_3 , and t_4 .
- draw the resistor voltage waveform and include voltage values at times t_0 , t_1 , t_2 , t_3 , and t_4 .
- draw the charge and discharge current waveform and include current values at times t_0 , t_1 , t_2 , t_3 , and t_4 .