

While measuring the total current, I_T , connect and disconnect the 0.22- μF capacitor several times. You should notice that I_T decreases when the capacitor is connected. Explain why this happens.

Using measured values, calculate the net reactive current, I_X , as $I_T - I_C$ or $I_C - I_T$ depending on which current is larger.

Using the experimental value of I_X and the measured value of I_T , calculate the circuit's phase angle, θ . $\theta =$

Using measured values, calculate the following:
apparent power = , real power = ,
PF =

In Figure 23-34a

a. Did the apparent power increase, decrease, or stay the same when the capacitor was added?

- b. Did the phase angle, θ , become more negative, less negative, or did it stay the same when the capacitor was added?
c. Did the real power increase, decrease, or stay the same when the capacitor was added?
d. Did the power factor, PF, increase, decrease, or stay the same when the capacitor was added?

Add a 10- Ω sensing resistor as shown in Fig. 23-34b. Next, connect the oscilloscope to measure the phase angle, θ , between V_A and I_T . Note the connections designated for channels 1 and 2 in the figure. While viewing the displayed waveforms on the oscilloscope, connect and disconnect the 0.22- μF capacitor several times. Explain what happens to the phase angle when the capacitor is connected.