

4. What is the power factor (PF) of a purely resistive ac circuit?

- 0.
- 1.
- 0.707.
- Without values, it cannot be determined.

5. The unit of apparent power is the

- volt-ampere (VA).
- watt (W).
- volt-ampere reactive (VAR).
- joule (J).

6. A $15\text{-}\Omega$ resistance is in series with $50\text{-}\Omega$ of X_L and $30\text{-}\Omega$ of X_C . If the applied voltage equals 50 V , how much real power is dissipated by the circuit?

- 60 W.
- 100 W.
- 100 VA.
- 4.16 W.

7. An ac circuit has a $100\text{-}\Omega$ R , a $300\text{-}\Omega$ X_L , and a $200\text{-}\Omega$ X_C all in series. What is the phase angle of the circuit?

- 78.7° .
- 45° .
- -90° .
- 56.3° .

8. A $10\text{-}\Omega$ resistor is in parallel with an X_L of $10\text{-}\Omega$. If the applied voltage is 120 V , what is the power factor of the circuit?

- 0.
- 0.5.
- 1.
- 0.707.

9. An ac circuit has an $80\text{-}\Omega$ R , $20\text{-}\Omega$ X_L , and a $40\text{-}\Omega$ X_C in parallel. If the applied voltage is 24 Vac , what is the phase angle of the circuit?

- -26.6° .
- 45° .
- -63.4° .
- -51.3° .

10. In an ac circuit with only series capacitors,

- V_T leads I by 90° .
- V_T lags I by 90° .
- each capacitor voltage drop leads I by 90° .
- both a and c.

11. A $10\text{-}\Omega$ R is in parallel with a $15\text{-}\Omega$ X_L . The applied voltage is 120 Vac . How much is the apparent power in the circuit?

- 2.4 kW.
- 1.44 kVA.

- 1.44 kW.
- 1.73 kVA.

12. The unit of real power is the

- watt (W).
- volt-ampere (VA).
- joule (J).
- volt-ampere reactive (VAR).

13. In a parallel ac circuit with X_L and X_C ,

- I_L and I_C are 90° out of phase.
- I_L and I_C are in phase.
- I_L and I_C are 180° out of phase.
- X_L and X_C are 90° out of phase.

14. In a series RLC circuit,

- X_L and X_C are 180° out of phase.
- I_L and I_C are 180° out of phase.
- X_L and X_C are 90° out of phase.
- X_L and X_C are in phase.

15. A parallel ac circuit with 120 Vac applied has a total current, I_T , of 5 A . If the phase angle of the circuit is -53.13° , how much real power is dissipated by the circuit?

- 600 VA.
- 480 W.
- 360 W.
- 3.6 kVA.

Essay Questions

- Why can series or parallel resistances be combined in ac circuits the same way as in dc circuits?
- (a) Why do X_L and X_C reactances in series offset each other? (b) With X_L and X_C reactances in parallel, why can their branch currents be subtracted?
- Give one difference in electrical characteristics comparing R and X_C , R and Z , X_C and C , X_L and L .
- Name three types of ac meters.
- Make a diagram showing a resistance R_1 in series with the load resistance R_L , with a wattmeter connected to measure the power in R_L .
- Make a phasor diagram for the circuit in Fig. 23-8a showing the phase of the voltage drops $I R$, $I X_C$, and $I X_L$ with respect to the reference phase of the common current I .
- Explain briefly why the two opposite phasors at $+90^\circ$ for X_L and -90° for I_L both follow the principle that any

self-induced voltage leads the current through the coil by 90° .


- Why is it that a reactance phasor is always at exactly 90° but an impedance phasor can be less than 90° ?
- Why must the impedance of a series circuit be more than either its X or its R ?
- Why must I_T in a parallel circuit be more than either I_R or I_X ?
- Compare real power and apparent power.
- Define *power factor*.
- Make a phasor diagram showing the opposite direction of positive and negative angles.
- In Fig. 23-15, which circuit has leading current with a positive phase angle θ where I from the source leads the V applied by the source?

Problems

SECTION 23-1 AC CIRCUITS WITH RESISTANCE BUT NO REACTANCE

23-1 In Fig. 23-17, solve for R_T , I , V_1 , and V_2 .

Figure 23-17

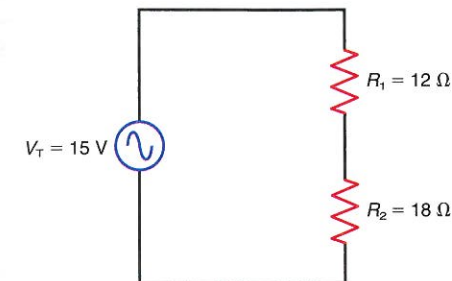

23-2 In Fig. 23-17, what is the phase relationship between


- V_T and I ?
- V_1 and I ?
- V_2 and I ?

23-3 In Fig. 23-18, solve for I_1 , I_2 , I_T , and R_{EQ} .

23-4 In Fig. 23-18, what is the phase relationship between

- V_A and I_1 ?
- V_A and I_2 ?
- V_A and I_T ?


Figure 23-18

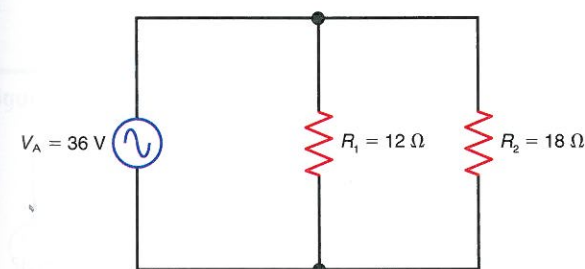

SECTION 23-2 CIRCUITS WITH X_L ALONE

23-5 In Fig. 23-19, solve for X_{L_T} , I , V_1 , and V_2 .

Figure 23-19

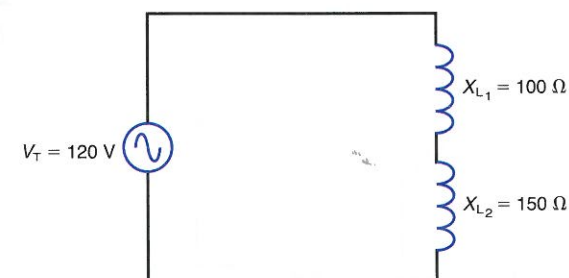


23-6 In Fig. 23-19, what is the phase relationship between

- V_T and I ?
- V_1 and I ?
- V_2 and I ?

23-7 In Fig. 23-20, solve for I_1 , I_2 , I_T , and $X_{L_{EQ}}$.

Figure 23-20

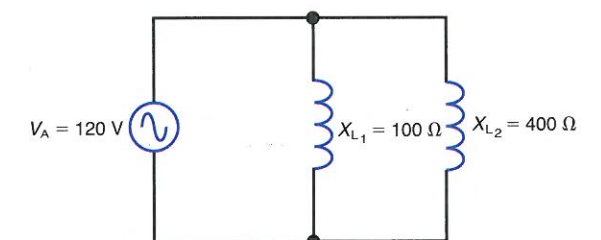


23-8 In Fig. 23-20, what is the phase relationship between

- V_A and I_1 ?
- V_A and I_2 ?
- V_A and I_T ?

SECTION 23-3 CIRCUITS WITH X_C ALONE

23-9 In Fig. 23-21, solve for X_{C_T} , I , V_1 , and V_2 .

Figure 23-21

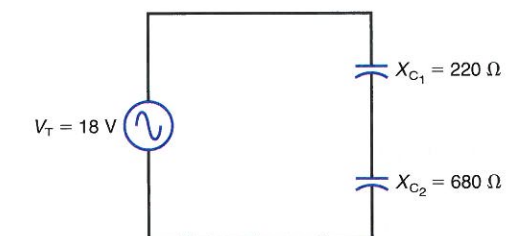

23-10 In Fig. 23-21, what is the phase relationship between

- V_T and I ?
- V_1 and I ?
- V_2 and I ?

23-11 In Fig. 23-22, solve for I_1 , I_2 , I_T , and $X_{C_{EQ}}$.

Figure 23-22

