


## Prob #2

A balanced three phase load of 3000 KW, power factor 0.8 lagging, is supplied at 22000 V (Line-to-Line) over a line having a resistance of  $3\Omega$  and an inductive reactance of  $10\Omega$  per conductor (or line to neutral)

Monitor the following variables.

- ~~(a)~~ Line Current
- ~~(b)~~ Line-to-neutral voltage at load.
- ~~(c)~~ Voltage drop in the transmission line.
- ~~(d)~~ Power loss in all three conductors.
- (e) Line-to-neutral voltage at the source
- (f) Line-to-Line voltage at the source.

## Problem # 3

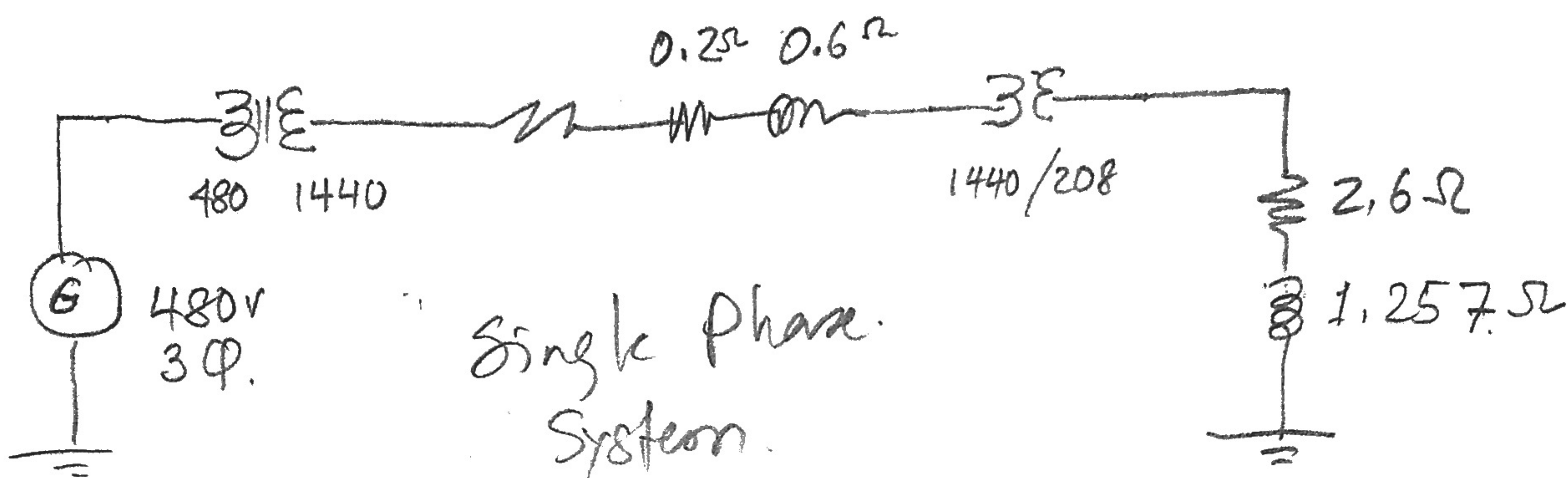

Monitor following variables:

- Voltage at the generator end
- Line Loss per phase and total for all three phase.
- Voltage at the load end
- Current at the load end.
- Current at the source end.
- Current in the transmission line, between the two transformer.

Prob# 4 Repeat Problem #3 with 3φ balanced Y-connected Load.