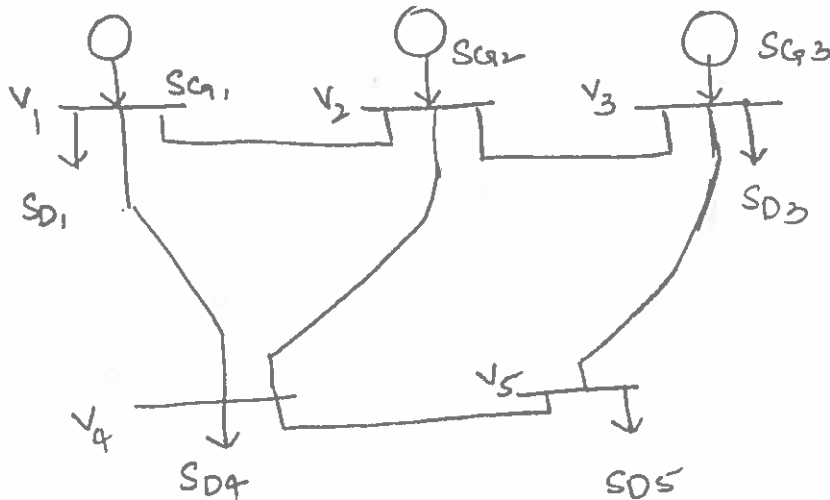


EENG 4310- HOME WORK# 3

POWER FLOW ANALYSIS

- Find Y_{bus} for figure below assuming that all the transmission links have identical π -equivalent circuits; series element impedance is $0.01+j0.1$ and each(of the two) shunt element admittances is $j0.8$




- We are given the system shown in fig below and the following equations for bus powers:

$$S_1 = j19.98 |V_1|^2 - jV_1 V_2^* - j10 V_1 V_3^*$$

$$S_2 = -j10 V_2 V_1^* + j19.98 |V_2|^2 - j10 V_2 V_3^*$$

$$S_3 = -j10 V_3 V_1 - j10 V_3 V_2^* + j19.98 |V_3|^2$$

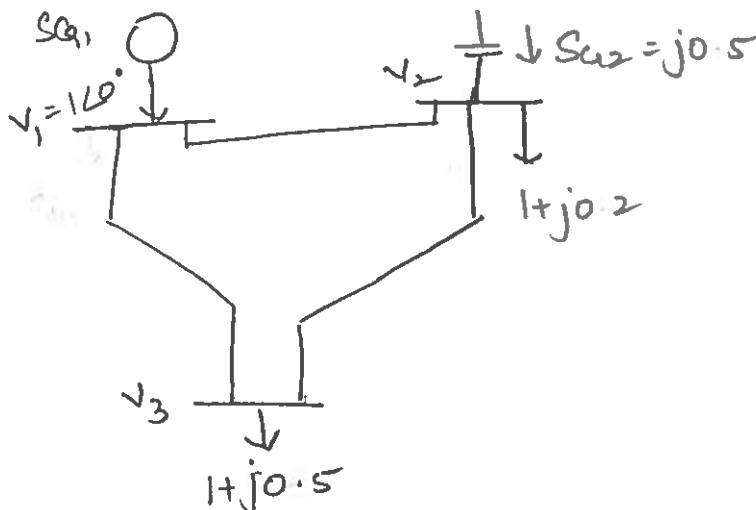Do one step of gauss iteration to find V_2^1 and V_3^1 . Start with $V_2^0 = V_3^0 = 1$



3. For the system below, assume $P_{G2}=0.3$, $|V_2|=0.95$, and $S_{D3}=0.5+j0.2$. Starting with $\theta_2^0=\theta_3^0=0$ and $|V_3|^0=1.0$, do one N-R iteration and find $|V_3|^1$, θ_2^1 and θ_3^1 . Evaluate the mismatch vector after this single iteration.

