

Department of Electrical Engineering

Transmission Line Models-Worked Problems

Student name:

- *Manually solve all problems!*
- *Write a MATLAB® code to solve the problems and verify your manual calculations!*
- *Turn in your manual solution along with the MATLAB® code plus the code results for 15 points added to your Exam1 grade. It must be attached to the Exam!*

1. A single-circuit 60-Hz high voltage power transmission line is 370 km (230 mi) long. The conductors are Rook with flat horizontal configuration and 7.25 m (23.8 ft.) conductor spacing. The load on the line is 125 MW at 100% power factor. Use attached Tables A3 to A5 to determine;
 - a. The sending end voltage V_s
 - b. The sending end current I_s
 - c. The sending end power P_s
 - d. The percentage voltage regulation
 - e. The transmission efficiency

Hint: All calculations are done at conductor temperature of 50°C

2. Given that D_s for the Rook conductor is 0.0327 ft., and its resistance is $0.1603\Omega/\text{mi}$, determine;
 - a. The phase inductance of the transmission line in mH/mi
 - b. The line series impedance z in Ω/mi
 - c. The line capacitance C_n
 - d. The line shunt admittance y in Ω^{-1}/mi
 - e. Compare the parameters obtained to the tabulated values
3. Repeat Problem (1) using the per-unit system. (Hint: Use 125 MVA and 215 kV as base values and then determine both the base current and base impedance)

4. A single-circuit 60-Hz high voltage power transmission line is 181 km (112.5 mi) long. The conductors are Dove with flat horizontal configuration and 7.25 m (23.8 ft.) conductor spacing. The load on the line is 70 MW at 100% power factor. Use attached Tables A3 to A5 to determine;
- The ABCD constants of the line
 - The sending end voltage V_s
 - The sending end current I_s
 - The sending end power P_s
 - The percentage voltage regulation
 - The transmission efficiency
5. Find the equivalent- π circuit (**equivalent to the long TL model**) for the power transmission line given in problem (1) and compare it with the nominal- π circuit model (Hint: calculate the % difference of the equivalent series impedance shunt reactance from the nominal- π circuit values. Please discuss your results!)
6. A short 3-phase, 34-kV power transmission line delivers a load of 10-MW at a power factor of 0.9 lagging and 34-kV. If the series impedance of the line is $10+j15 \Omega / \text{phase}$ calculate;
- The ABCD constants
 - The sending end voltage V_s
 - The sending end current I_s
 - The percentage voltage regulation
 - The transmission efficiency