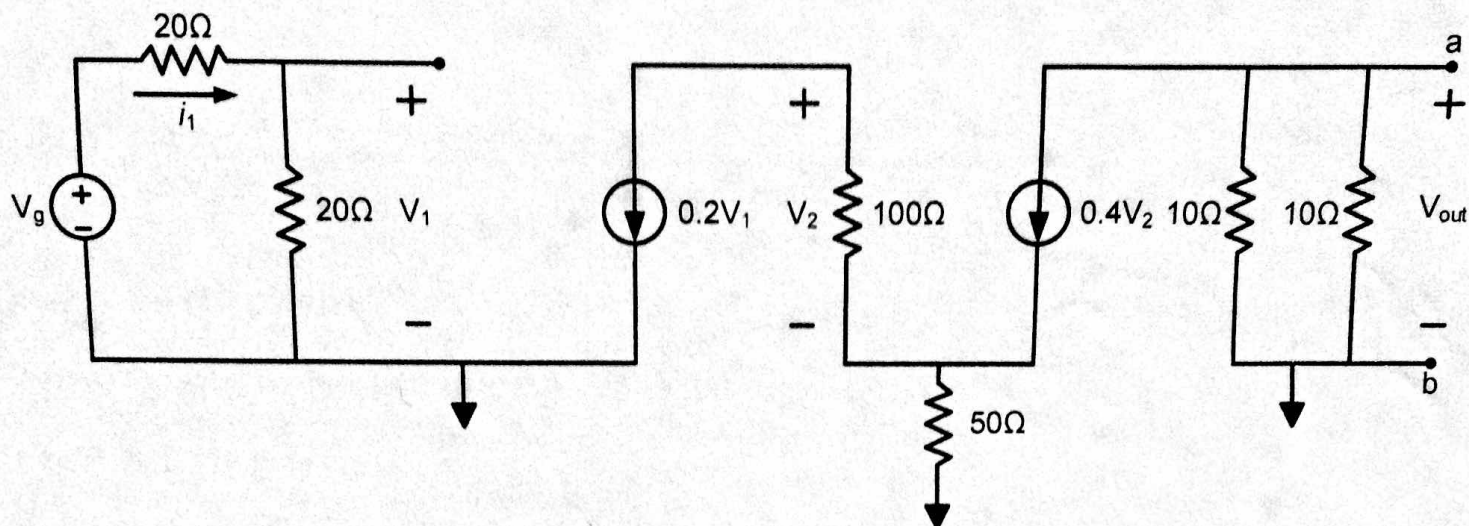


Problem 1 (30 points):

- (1) Find V_{out}/V_g .
- (2) Assuming V_g is the input signal, find the Thevenin equivalent circuit looking into the terminals a-b.



Problem 2 (20 points):

Use the solution from Problem 1,

- (a) If $V_g = 2\text{VDC}$, what is the voltage at V_{out} ?
- (b) If $V_g = 7\text{V DC}$, what is the voltage at V_{out} ?
- (c) If $V_g = 2\cos(10t)$, what is the output voltage at V_{out} ? Make a rough sketch of V_{out} and V_g .
- (d) Note that this is an amplifier, i.e. the output is linearly related to the input by a gain value. Mathematically, that is express as: $V_{out}/V_{in} = \text{gain}$.

For the circuit above, what is the variable for V_{out} and V_{in} ? What is the numerical gain value?


Problem 3 (10 points):

Sketch the following waveforms. Identify the DC component of the waveform and the AC component of the waveform.

(a) $V_s = 5V\cos(2\pi t)$

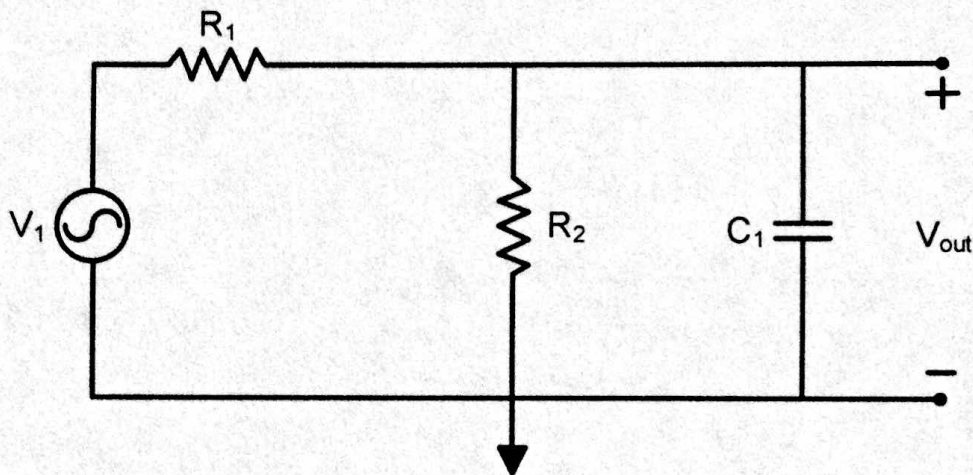(b) $V_s = 1V - 1V\sin(3t)$

Using the following circuit for Problems 4-7, assuming $R_1 = 20\Omega$, $R_2 = 100\Omega$, and $C_1 = 3\text{mF}$ (i.e. $3 \times 10^{-3}\text{F}$)



Problem 4 (10 points)

Derive the transfer function $H(s) = V_{out}(s)/V_1(s)$.

Problem 5 (10 points)

Use PSPICE to draw and print out the circuit schematic.

Problem 6 (10 points)

Simulate the circuit in PSPICE to obtain the Bode Plot of $H(s) = V_{out}(s)/V_1(s)$.

Problem 7 (10 points)

Use MATLAB and the results of the hand derivation to obtain the Bode Plot.

Note: PSPICE plots the results over frequency in Hz and derived transfer function uses ω in radians/sec.