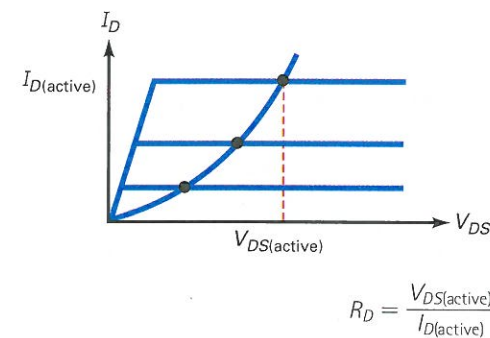


(14-6) Two-terminal resistance:




Derivations

(14-2) D-MOSFET zero-bias:

$$V_{DS} = V_{DD} - I_{DSS} R_D$$

(14-4) Saturation current:

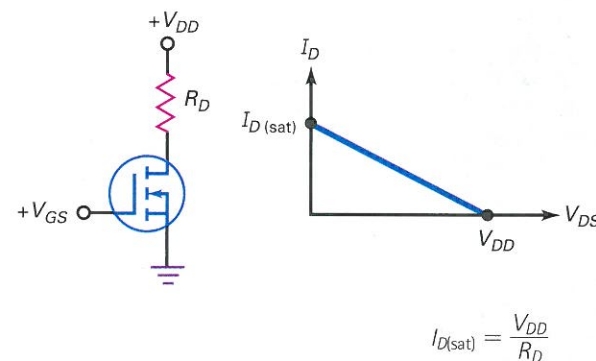


(14-8) E-MOSFET constant k :

$$k = \frac{I_{D(on)}}{[V_{GS(on)} - V_{GS(th)}]^2}$$

(14-10) E-MOSFET g_m :

$$g_m = 2k[V_{GS} - V_{GS(th)}]$$

(14-5) Ohmic region:

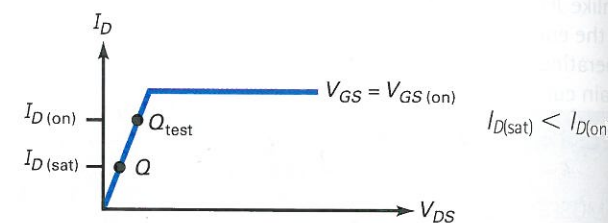

(14-7) E-MOSFET drain current:

$$I_D = k[V_{GS} - V_{GS(th)}]^2$$

(14-9) R_D for drain-feedback bias:

$$R_D = \frac{V_{DD} - V_{DS(on)}}{I_{D(on)}}$$

Student Assignments

- A D-MOSFET can operate in the
 - Depletion-mode only
 - Enhancement-mode only
 - Depletion-mode or enhancement-mode
 - Low-impedance mode
- When an n -channel D-MOSFET has $I_D > I_{DSS}$, it
 - Will be destroyed
 - Is operating in the depletion mode
 - Is forward biased
 - Is operating in the enhancement mode
- The voltage gain of a D-MOSFET amplifier is dependent on
 - R_D
 - R_L
 - g_m
 - All of the above
- Which of the following devices revolutionized the computer industry?
 - JFET
 - D-MOSFET
 - E-MOSFET
 - Power FET
- The voltage that turns on an EMOS device is the
 - Gate-source cutoff voltage
 - Pinchoff voltage
 - Threshold voltage
 - Knee voltage
- Which of these may appear on the data sheet of an enhancement-mode MOSFET?
 - $V_{GS(th)}$
 - $I_{D(on)}$
 - $V_{GS(on)}$
 - All the above
- The $V_{GS(on)}$ of an n -channel E-MOSFET is
 - Less than the threshold voltage
 - Equal to the gate-source cutoff voltage
 - Greater than $V_{DS(on)}$
 - Greater than $V_{GS(th)}$
- An ordinary resistor is an example of
 - A three-terminal device
 - An active load
 - A passive load
 - A switching device
- An E-MOSFET with its gate connected to its drain is an example of
 - A three-terminal device
 - An active load
 - A passive load
 - A switching device

10. An E-MOSFET that operates at cutoff or in the ohmic region is an example of

- A current source
- An active load
- A passive load
- A switching device

11. VMOS devices generally

- Switch off faster than BJTs
- Carry low values of current
- Have a negative temperature coefficient
- Are used as CMOS inverters

12. A D-MOSFET is considered to be a

- Normally off device
- Normally on device
- Current controlled device
- High-power switch

13. CMOS stands for

- Common MOS
- Active-load switching
- p -channel and n -channel devices
- Complementary MOS

14. $V_{GS(on)}$ is always

- Less than $V_{GS(th)}$
- Equal to $V_{DS(on)}$
- Greater than $V_{GS(th)}$
- Negative

15. With active-load switching, the upper E-MOSFET is a

- Two-terminal device
- Three-terminal device
- Switch
- Small resistance

16. CMOS devices use

- Bipolar transistors
- Complementary E-MOSFETs
- Class A operation
- DMOS devices

17. The main advantage of CMOS is its

- High power rating
- Small-signal operation
- Switching capability
- Low power consumption

18. Power FETs are

- Integrated circuits
- Small-signal devices
- Used mostly with analog signals
- Used to switch large currents

19. When the internal temperature increases in a power FET, the

- Threshold voltage increases
- Gate current decreases
- Drain current decreases
- Saturation current increases

20. Most small-signal E-MOSFETs are found in

- Heavy-current applications
- Discrete circuits
- Disk drives
- Integrated circuits

21. Most power FETs are

- Used in high-current applications
- Digital computers
- RF stages
- Integrated circuits

22. An n -channel E-MOSFET conducts when it has

- $V_{GS} > V_P$
- An n -type inversion layer
- $V_{DS} > 0$
- Depletion layers

23. With CMOS, the upper MOSFET is

- A passive load
- An active load
- Nonconducting
- Complementary

24. The high output of a CMOS inverter is

- $V_{DD}/2$
- V_{GS}
- V_{DS}
- V_{DD}

25. The $R_{DS(on)}$ of a power FET

- Is always large
- Has a negative temperature coefficient
- Has a positive temperature coefficient
- Is an active load

Problems

SEC. 14-2 D-MOSFET CURVES

- 14-1 An n -channel D-MOSFET has the specifications $V_{GS(off)} = -2$ V and $I_{DSS} = 4$ mA. Given V_{GS} values of -0.5 V, -1.0 V, -1.5 V, $+0.5$ V, $+1.0$ V, and $+1.5$ V, determine I_D in the depletion mode only.
- 14-2 Given the same values as in the previous problem, calculate I_D for the enhancement mode only.
- 14-3 A p -channel D-MOSFET has $V_{GS(off)} = +3$ V and $I_{DSS} = 12$ mA. Given V_{GS} values of -1.0 V, -2.0 V, 0 V, $+1.5$ V, and $+2.5$ V, determine I_D in the depletion mode only.

SEC. 14-3 DEPLETION-MODE MOSFET AMPLIFIERS

- 14-4 The D-MOSFET in Fig. 14-36 has $V_{GS(off)} = -3$ V and $I_{DSS} = 12$ mA. Determine the circuit's drain current and V_{DS} values.

14-5 In Fig. 14-36, what are the values of r_d , A_v , and V_{out} using a g_{mo} of $4000 \mu S$?

14-6 Using Fig. 14-36 find r_d , A_v , and V_{out} if $R_D = 680 \Omega$ and $R_L = 10 k\Omega$.

14-7 What is the approximate input impedance of Fig. 14-36?

SEC. 14-5 THE OHMIC REGION

14-8 Calculate $R_{DS(on)}$ for each of these E-MOSFET values:

- $V_{DS(on)} = 0.1$ V and $I_{D(on)} = 10$ mA
- $V_{DS(on)} = 0.25$ V and $I_{D(on)} = 45$ mA
- $V_{DS(on)} = 0.75$ V and $I_{D(on)} = 100$ mA
- $V_{DS(on)} = 0.15$ V and $I_{D(on)} = 200$ mA