
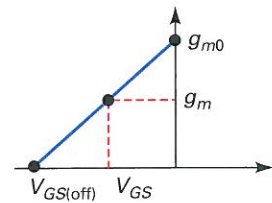


(13-16) Transconductance:

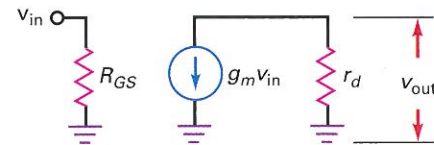


$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

(13-17) CS voltage gain:



$$A_v = g_m r_d$$

(13-18) Source follower:

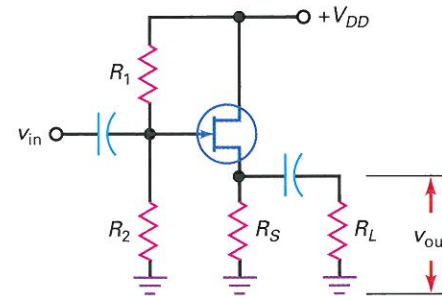

$$A_v = \frac{g_m r_s}{1 + g_m r_s}$$

Student Assignments

- A JFET
 - Is a voltage-controlled device
 - Is a current-controlled device
 - Has a low input resistance
 - Has a very large voltage gain
- A unipolar transistor uses
 - Both free electrons and holes
 - Only free electrons
 - Only holes
 - Either one or the other, but not both
- The input impedance of a JFET
 - Approaches zero
 - Approaches one
 - Approaches infinity
 - Is impossible to predict
- The gate controls
 - The width of the channel
 - The drain current
 - The gate voltage
 - All the above
- The gate-source diode of a JFET should be
 - Forward biased
 - Reverse biased
 - Either forward or reverse biased
 - None of the above
- Compared to a bipolar junction transistor, the JFET has a much higher
 - Voltage gain
 - Input resistance
 - Supply voltage
 - Current
- The pinchoff voltage has the same magnitude as the
 - Gate voltage
 - Drain-source voltage
 - Gate-source voltage
 - Gate-source cutoff voltage
- When the drain saturation current is less than I_{DSS} , a JFET acts like a
 - Bipolar junction transistor
 - Current source
 - Resistor
 - Battery
- R_{DS} equals pinchoff voltage divided by
 - Drain current
 - Gate current
 - Ideal drain current
 - Drain current for zero gate voltage
- The transconductance curve is
 - Linear
 - Similar to the graph of a resistor
 - Nonlinear
 - Like a single drain curve
- The transconductance increases when the drain current approaches
 - 0
 - $I_{D(sat)}$
 - I_{DSS}
 - I_S
- A CS amplifier has a voltage gain of
 - $g_m r_d$
 - $g_m r_s$
 - $g_m r_s / (1 + g_m r_s)$
 - $g_m r_d / (1 + g_m r_d)$
- A source follower has a voltage gain of
 - $g_m r_d$
 - $g_m r_s$
 - $g_m r_s / (1 + g_m r_s)$
 - $g_m r_d / (1 + g_m r_d)$
- When the input signal is large, a source follower has
 - A voltage gain of less than 1
 - Some distortion
 - A high input resistance
 - All of these
- The input signal used with a JFET analog switch should be
 - Small
 - Large
 - A square wave
 - Chopped
- A cascode amplifier has the advantage of
 - Large voltage gain
 - Low input capacitance
 - Low input impedance
 - Higher g_m
- VHF covers frequencies from
 - 300 kHz to 3 MHz
 - 3 to 30 MHz
 - 30 to 300 MHz
 - 300 MHz to 3 GHz

18. When a JFET is cut off, the depletion layers are

- Far apart
- Close together
- Touching
- Conducting

19. When the gate voltage becomes more negative in an *n*-channel JFET, the channel between the depletion layers

- Shrinks
- Expands
- Conducts
- Stops conducting

20. If a JFET has $I_{DSS} = 8$ mA and $V_P = 4$ V, then R_{DS} equals

- 200 Ω
- 320 Ω
- 500 Ω
- 5 k Ω

21. The easiest way to bias a JFET in the ohmic region is with

- Voltage-divider bias
- Self-bias
- Gate bias
- Source bias

22. Self-bias produces

- Positive feedback
- Negative feedback
- Forward feedback
- Reverse feedback

23. To get a negative gate-source voltage in a self-biased JFET circuit, you must have a

- Voltage divider
- Source resistor
- Ground
- Negative gate supply voltage

24. Transconductance is measured in

- Ohms
- Amperes
- Volts
- Mhos or siemens

25. Transconductance indicates how effectively the input voltage controls the

- Voltage gain
- Input resistance
- Supply voltage
- Output current

Problems

SEC. 13-1 BASIC IDEAS

13-1 A 2N5458 has a gate current of 1 nA when the reverse voltage is -15 V. What is the input resistance of the gate?

13-2 A 2N5640 has a gate current of 1 μ A when the reverse voltage is -20 V and the ambient temperature is 100°C . What is the input resistance of the gate?

SEC. 13-2 DRAIN CURVES

13-3 A JFET has $I_{DSS} = 20$ mA and $V_P = 4$ V. What is the maximum drain current? The gate-source cutoff voltage? The value of R_{DS} ?

13-4 A 2N5555 has $I_{DSS} = 16$ mA and $V_{GS(off)} = -2$ V. What is the pinchoff voltage for this JFET? What is the drain-source resistance R_{DS} ?

13-5 A 2N5457 has $I_{DSS} = 1$ to 5 mA and $V_{GS(off)} = -0.5$ to -6 V. What are the minimum and maximum values of R_{DS} ?

SEC. 13-3 THE TRANSCONDUCTANCE CURVE

13-6 A 2N5462 has $I_{DSS} = 16$ mA and $V_{GS(off)} = -6$ V. What are the gate voltage and drain current at the half cutoff point?

13-7 A 2N5670 has $I_{DSS} = 10$ mA and $V_{GS(off)} = -4$ V. What are the gate voltage and drain current at the half cutoff point?

13-8 If a 2N5486 has $I_{DSS} = 14$ mA and $V_{GS(off)} = -4$ V, what is the drain current when $V_{GS} = -1$ V? When $V_{GS} = -3$ V?

SEC. 13-4 BIASING IN THE OHMIC REGION

13-9 What is the drain saturation current in Fig. 13-43a? The drain voltage?

13-10 If the 10-k Ω resistor of Fig. 13-43a is increased to 20 k Ω , what is the drain voltage?

13-11 What is the drain voltage in Fig. 13-43b?

13-12 If the 20-k Ω resistor of Fig. 13-43b is decreased to 10 k Ω , what is the drain saturation current? The drain voltage?

SEC. 13-5 BIASING IN THE ACTIVE REGION

For Problems 13-13 through 13-20, use preliminary analysis.

13-13 What is the ideal drain voltage in Fig. 13-44a?

13-14 Draw the dc load line and Q point for Fig. 13-44a.

13-15 What is the ideal drain voltage in Fig. 13-44b?

13-16 If the 18 k Ω of Fig. 13-44b is changed to 30 k Ω , what is the drain voltage?

13-17 In Fig. 13-45a, what is the drain current? The drain voltage?