


7. The initial slope of a sine wave is directly proportional to
 - a. Slew rate
 - b. Frequency
 - c. Voltage gain
 - d. Capacitance
8. When the initial slope of a sine wave is greater than the slew rate,
 - a. Distortion occurs
 - b. Linear operation occurs
 - c. Voltage gain is maximum
 - d. The op amp works best
9. The power bandwidth increases when
 - a. Frequency decreases
 - b. Peak value decreases
 - c. Initial slope decreases
 - d. Voltage gain increases
10. A 741C contains
 - a. Discrete resistors
 - b. Inductors
 - c. Active-load resistors
 - d. A large coupling capacitor
11. A 741C cannot work without
 - a. Discrete resistors
 - b. Passive loading
 - c. DC return paths on the two bases
 - d. A small coupling capacitor
12. The input impedance of a BIFET op amp is
 - a. Low
 - b. Medium
 - c. High
 - d. Extremely high
13. An LF157A is a
 - a. Diff amp
 - b. Source follower
 - c. Bipolar op amp
 - d. BIFET op amp
14. If the two supply voltages are ± 12 V, the MPP value of an op amp is closest to
 - a. 0
 - b. $+12$ V
 - c. -12 V
 - d. 24 V
15. The open-loop cutoff frequency of a 741C is controlled by
 - a. A coupling capacitor
 - b. The output short circuit current
 - c. The power bandwidth
 - d. A compensating capacitor
16. The 741C has a unity-gain frequency of
 - a. 10 Hz
 - b. 20 kHz
 - c. 1 MHz
 - d. 15 MHz
17. The unity-gain frequency equals the product of closed-loop voltage gain and the
 - a. Compensating capacitance
 - b. Tail current
 - c. Closed-loop cutoff frequency
 - d. Load resistance
18. If f_{unity} is 10 MHz and midband open-loop voltage gain is 200,000, then the open-loop cutoff frequency of the op amp is
 - a. 10 Hz
 - b. 20 Hz
 - c. 50 Hz
 - d. 100 Hz
19. The initial slope of a sine wave increases when
 - a. Frequency decreases
 - b. Peak value increases
 - c. C_c increases
 - d. Slew rate decreases
20. If the frequency of the input signal is greater than the power bandwidth,
 - a. Slew-rate distortion occurs
 - b. A normal output signal occurs
 - c. Output offset voltage increases
 - d. Distortion may occur
21. An op amp has an open base resistor. The output voltage will be
 - a. Zero
 - b. Slightly different from zero
 - c. Maximum positive or negative
 - d. An amplified sine wave
22. An op amp has a voltage gain of 200,000. If the output voltage is 1 V, the input voltage is
 - a. $2 \mu\text{V}$
 - b. $5 \mu\text{V}$
 - c. 10 mV
 - d. 1 V
23. A 741C has supply voltages of ± 15 V. If the load resistance is large, the MPP value is approximately
 - a. 0
 - b. $+15$ V
 - c. 27 V
 - d. 30 V
24. Above the cutoff frequency, the voltage gain of a 741C decreases approximately
 - a. 10 dB per decade
 - b. 20 dB per octave
 - c. 10 dB per octave
 - d. 20 dB per decade
25. The voltage gain of an op amp is unity at the
 - a. Cutoff frequency
 - b. Unity-gain frequency
 - c. Generator frequency
 - d. Power bandwidth
26. When slew-rate distortion of a sine wave occurs, the output
 - a. Is larger
 - b. Appears triangular
 - c. Is normal
 - d. Has no offset
27. A 741C has
 - a. A voltage gain of 100,000
 - b. An input impedance of $2 \text{ M}\Omega$
 - c. An output impedance of 75Ω
 - d. All of the above
28. The closed-loop voltage gain of an inverting amplifier equals
 - a. The ratio of the input resistance to the feedback resistance
 - b. The open-loop voltage gain
 - c. The feedback resistance divided by the input resistance
 - d. The input resistance
29. The noninverting amplifier has a
 - a. Large closed-loop voltage gain
 - b. Small open-loop voltage gain
 - c. Large closed-loop input impedance
 - d. Large closed-loop output impedance
30. The voltage follower has a
 - a. Closed-loop voltage gain of unity
 - b. Small open-loop voltage gain
 - c. Closed-loop bandwidth of zero
 - d. Large closed-loop output impedance
31. A summing amplifier can have
 - a. No more than two input signals
 - b. Two or more input signals
 - c. A closed-loop input impedance of infinity
 - d. A small open-loop voltage gain

Problems

SEC. 18-2 THE 741 OP AMP

- 18-1 Assume that negative saturation occurs at 1 V less than the supply voltage with an 741C. How much inverting input voltage does it take to drive the op amp of Fig. 18-29 into negative saturation?

Figure 18-29

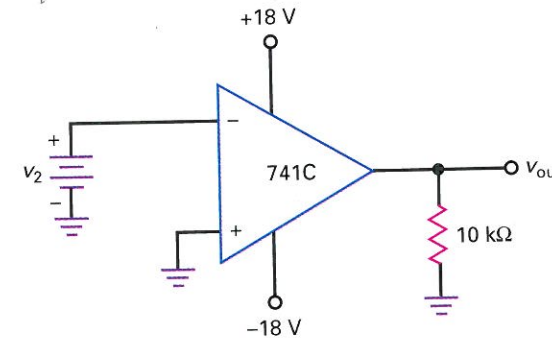

- 18-2 What is the common-mode rejection ratio of an LF157A at low frequencies? Convert this decibel value to an ordinary number.
- 18-3 What is the open-loop voltage gain of an LF157A when the input frequency is 1 kHz? 10 kHz? 100 kHz? (Assume a first-order response, that is, 20 dB per decade rolloff.)
- 18-4 The input voltage to an op amp is a large voltage step. The output is an exponential waveform that changes 2.0 V in $0.4 \mu\text{s}$. What is the slew rate of the op amp?
- 18-5 An LM318 has a slew rate of $70 \text{ V}/\mu\text{s}$. What is the power bandwidth for a peak output voltage of 7 V?
- 18-6 Use Eq. (18-2) to calculate the power bandwidth for each of the following:
- a. $S_R = 0.5 \text{ V}/\mu\text{s}$ and $V_p = 1 \text{ V}$
 - b. $S_R = 3 \text{ V}/\mu\text{s}$ and $V_p = 5 \text{ V}$
 - c. $S_R = 15 \text{ V}/\mu\text{s}$ and $V_p = 10 \text{ V}$

SEC. 18-3 THE INVERTING AMPLIFIER

- 18-7 **MultiSim** What are closed-loop voltage gain and bandwidth in Fig. 18-30? What is the output voltage at 1 kHz? At 10 MHz? Draw the ideal Bode plot of closed-loop voltage gain.

Figure 18-30


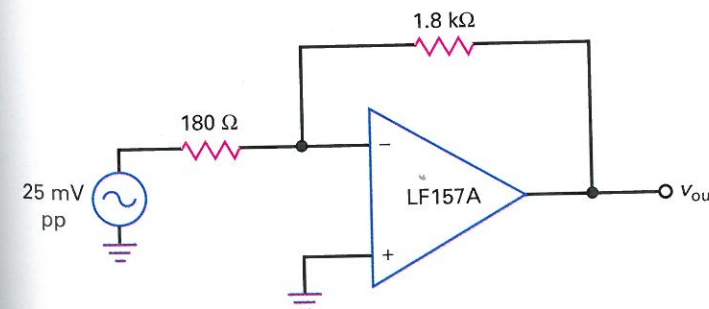


Figure 18-31

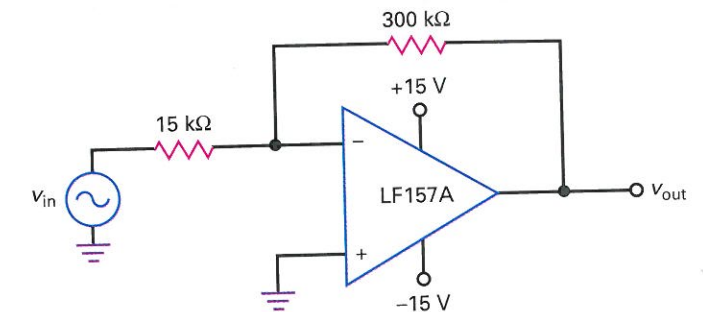

- 18-8 What is the output voltage in Fig. 18-31 when V_{in} is zero? Use the typical values of Table 18-1.
- 18-9 The data sheet of an LF157A lists the following worst-case parameters: $I_{\text{in(bias)}} = 50 \text{ pA}$, $I_{\text{in(off)}} = 10 \text{ pA}$, and $V_{\text{in(off)}} = 2 \text{ mV}$. Recalculate the output voltage when V_{in} is zero in Fig. 18-31.

SEC. 18-4 THE NONINVERTING AMPLIFIER

- 18-10 **MultiSim** In Fig. 18-32, what are the closed-loop voltage gain and bandwidth? The ac output voltage at 100 kHz?
- 18-11 What is the output voltage when V_{in} is reduced to zero in Fig. 18-32? Use the worst-case parameters given in Prob. 18-9.

Figure 18-32

