

## Problems

### SEC. 20-1 INVERTING-AMPLIFIER CIRCUITS

- 20-1 In the probe of Fig. 20-1,  $R_1 = 10\text{ M}\Omega$ ,  $R_2 = 20\text{ M}\Omega$ ,  $R_3 = 15\text{ k}\Omega$ ,  $R_4 = 15\text{ k}\Omega$ , and  $R_5 = 75\text{ k}\Omega$ . What is the attenuation of the probe in each switch position?
- 20-2 In the ac-coupled inverting amplifier of Fig. 20-2,  $R_1 = 1.5\text{ k}\Omega$ ,  $R_f = 75\text{ k}\Omega$ ,  $R_L = 15\text{ k}\Omega$ ,  $C_1 = 1\text{ }\mu\text{F}$ ,  $C_2 = 4.7\text{ }\mu\text{F}$ , and  $f_{\text{unity}} = 1\text{ MHz}$ . What is the voltage gain in the midband of the amplifier? What are the upper and lower cutoff frequencies?
- 20-3 In the adjustable-bandwidth circuit of Fig. 20-3,  $R_1 = 10\text{ k}\Omega$  and  $R_f = 180\text{ k}\Omega$ . If the  $100\text{-}\Omega$  resistor is changed to  $130\text{ }\Omega$  and the variable resistor to  $25\text{ k}\Omega$ , what is the voltage gain? What are the minimum and maximum bandwidth if  $f_{\text{unity}} = 1\text{ MHz}$ ?
- 20-4 What is the output voltage in Fig. 20-37? What are the minimum and maximum bandwidth? (Use  $f_{\text{unity}} = 1\text{ MHz}$ .)

Figure 20-37


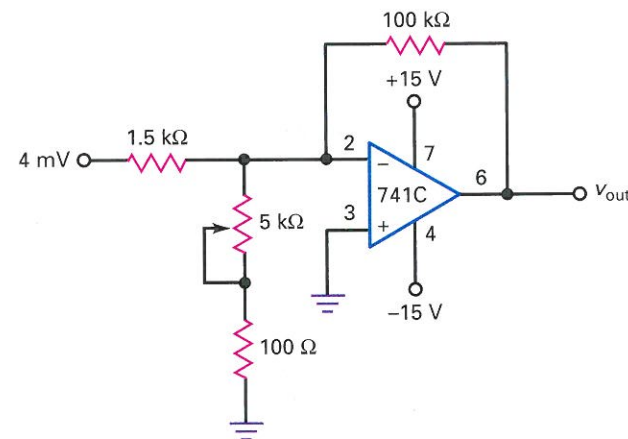


Figure 20-38

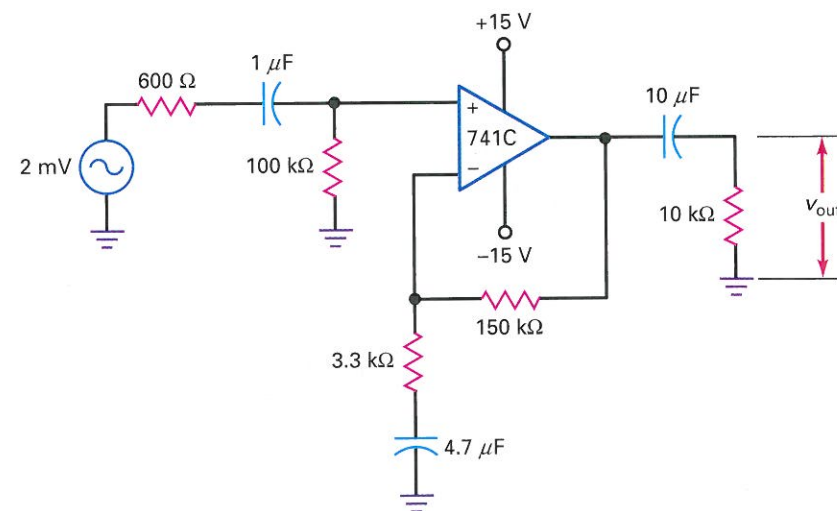


### SEC. 20-2 NONINVERTING-AMPLIFIER CIRCUITS

- 20-5 In Fig. 20-4,  $R_1 = 2\text{ k}\Omega$ ,  $R_f = 82\text{ k}\Omega$ ,  $R_L = 25\text{ k}\Omega$ ,  $C_1 = 2.2\text{ }\mu\text{F}$ ,  $C_2 = 4.7\text{ }\mu\text{F}$ , and  $f_{\text{unity}} = 3\text{ MHz}$ . What is the voltage gain in the midband of the amplifier? What are the upper and lower cutoff frequencies?
- 20-6 What is the voltage gain in the midband of Fig. 20-38? What are the upper and lower cutoff frequencies?
- 20-7 **MultiSim** In the distribution amplifier of Fig. 20-5,  $R_1 = 2\text{ k}\Omega$ ,  $R_f = 100\text{ k}\Omega$ , and  $v_{\text{in}} = 10\text{ mV}$ . What is the output voltage for A, B, and C?
- 20-8 The JFET-switched amplifier of Fig. 20-6 has these values:  $R_1 = 91\text{ k}\Omega$ ,  $R_f = 12\text{ k}\Omega$ , and  $R_2 = 1\text{ k}\Omega$ . If  $v_{\text{in}} = 2\text{ mV}$ , what is the output voltage when the gate is low? When it is high?
- 20-9 If  $V_{\text{GS(off)}} = -5\text{ V}$ , what are the minimum and maximum output voltage in Fig. 20-39?
- 20-10 The voltage reference of Fig. 20-7 is modified to get  $R_1 = 10\text{ k}\Omega$  and  $R_f = 10\text{ k}\Omega$ . What is the new output reference voltage?

### SEC. 20-3 INVERTER/NONINVERTER CIRCUITS

- 20-11 In the adjustable inverter of Fig. 20-10,  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 10\text{ k}\Omega$ . What is the maximum positive gain? The maximum negative gain?
- 20-12 What is the voltage gain in Fig. 20-11 when the wiper is at the ground end? When it is 10 percent away from ground?
- 20-13 Precision resistors are used in Fig. 20-12. If  $R = 5\text{ k}\Omega$ ,  $nR = 75\text{ k}\Omega$ , and  $nR/(n-1)R = 5.36\text{ k}\Omega$ , what are the maximum positive and negative gains?
- 20-14 In the phase shifter of Fig. 20-13,  $R' = 10\text{ k}\Omega$ ,  $R = 22\text{ k}\Omega$ , and  $C = 0.02\text{ }\mu\text{F}$ . What is the phase shift when the input frequency is 100 Hz? 1 kHz? 10 kHz?

Figure 20-39

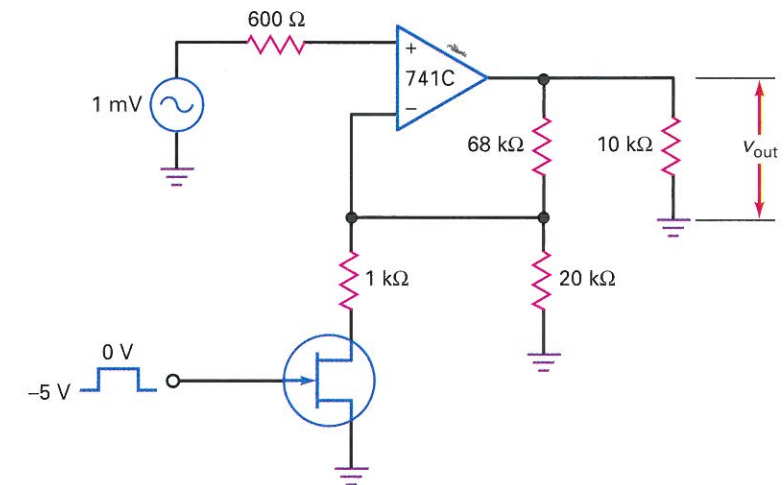

### SEC. 20-4 DIFFERENTIAL AMPLIFIERS

- 20-15 The differential amplifier of Fig. 20-14 has  $R_1 = 1.5\text{ k}\Omega$  and  $R_2 = 30\text{ k}\Omega$ . What is the differential voltage gain? The common-mode gain? (Resistor tolerance =  $\pm 0.1\text{ percent}$ .)
- 20-16 In Fig. 20-15,  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 20\text{ k}\Omega$ . What is the differential voltage gain? The common-mode gain? (Resistor tolerance =  $\pm 1\text{ percent}$ .)
- 20-17 In the Wheatstone bridge of Fig. 20-16,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 20\text{ k}\Omega$ ,  $R_3 = 20\text{ k}\Omega$ , and  $R_4 = 10\text{ k}\Omega$ . Is the bridge balanced?
- 20-18 In the typical application of Fig. 20-17, transducer resistance changes to  $985\text{ }\Omega$ . What is the final output voltage?

### SEC. 20-5 INSTRUMENTATION AMPLIFIERS

- 20-19 In the instrumentation amplifier of Fig. 20-18,  $R_1 = 1\text{ k}\Omega$  and  $R_2 = 99\text{ k}\Omega$ . What is the output voltage if  $v_{\text{in}} = 2\text{ mV}$ ? If three OP-07A op amps are used and  $R = 10\text{ k}\Omega \pm 0.5\text{ percent}$ , what is the CMRR of the instrumentation amplifier?
- 20-20 In Fig. 20-19,  $v_{\text{in(CM)}} = 5\text{ V}$ . If  $R_3 = 10\text{ k}\Omega$ , what does the guard voltage equal?
- 20-21 The value of  $R_G$  is changed to  $1008\text{ }\Omega$  in Fig. 20-20. What is the differential output voltage if the differential input voltage is  $20\text{ mV}$ ?

### SEC. 20-6 SUMMING AMPLIFIER CIRCUITS

- 20-22 What does the output voltage equal in Fig. 20-21 if  $R = 10\text{ k}\Omega$ ,  $v_1 = -50\text{ mV}$  and  $v_2 = -30\text{ mV}$ ?
- 20-23 **MultiSim** In the summing circuit of Fig. 20-22,  $R_1 = 10\text{ k}\Omega$ ,  $R_2 = 20\text{ k}\Omega$ ,  $R_3 = 15\text{ k}\Omega$ ,  $R_4 = 15\text{ k}\Omega$ ,  $R_5 = 30\text{ k}\Omega$ , and  $R_f = 75\text{ k}\Omega$ . What is the output voltage if  $v_0 = 1\text{ mV}$ ,  $v_1 = 2\text{ mV}$ ,  $v_2 = 3\text{ mV}$ , and  $v_3 = 4\text{ mV}$ ?
- 20-24 The averaging circuit of Fig. 20-23 has  $R = 10\text{ k}\Omega$ . What is the output if  $v_1 = 1.5\text{ V}$ ,  $v_2 = 2.5\text{ V}$ , and  $v_3 = 4.0\text{ V}$ ?

- 20-25 The D/A converter of Fig. 20-24 has an input of  $v_0 = 5\text{ V}$ ,  $v_1 = 0$ ,  $v_2 = 5\text{ V}$ , and  $v_3 = 0$ . What is the output voltage?
- 20-26 In Fig. 20-25, if the number of binary inputs is expanded to eight and  $D_7$  to  $D_0$  equals 10100101, determine the decimal equivalent input value, BIN.
- 20-27 In Fig. 20-25, if the binary inputs were expanded so  $D_7$  to  $D_0$  equaled 01100110, what would be the output voltage?
- 20-28 In Fig. 20-25, using an input reference voltage of  $2.5\text{ V}$ , determine the smallest incremental output voltage step.

### SEC. 20-7 CURRENT BOOSTERS

- 20-29 The noninverting amplifier of Fig. 20-40 has a current-boostered output. What is the voltage gain of the circuit? If the transistor has a current gain of 100, what is the short-circuit output current?
- 20-30 What is the voltage gain in Fig. 20-41? If the transistors have a current gain of 125, what is the short-circuit output current?

Figure 20-40

