

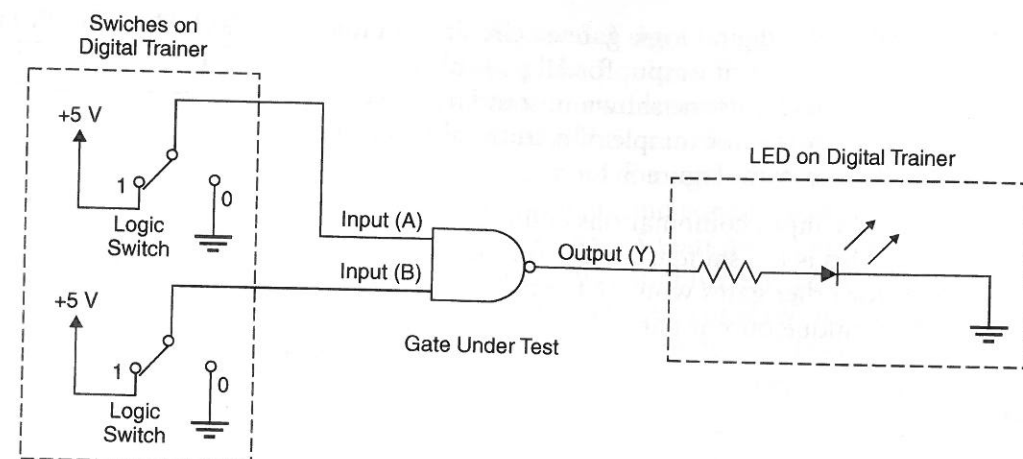


Figure 3.4 Testing a Gate in a DIP IC (with a Digital Trainer)

- Take the truth table of the gate by changing inputs A and B to make all possible combinations of input ($AB = 00, 01, 10, 11$) and writing down whether the LED at output 3 indicates logic 1 (ON) or logic 0 (OFF) for each input combination. Fill in Table 3.2 with your results.
- Move the logic input connections to pins 4 and 5 and the lamp to pin 6 and repeat Step 4. Also repeat with:
 - logic switches at pins 9 and 10 and lamp at pin 8, and;
 - logic switches at pins 12 and 13 and lamp at pin 11.

Table 3.2 NAND Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Table 3.3 AND Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Table 3.6 Inverter Truth Table

A	B
0	
1	

Table 3.4 NOR Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Table 3.7 XOR Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Table 3.5 OR Truth Table

A	B	Y
0	0	
0	1	
1	0	
1	1	

Instructor's Initials _____

Expanding Logic Gates

Name _____ Class _____ Date _____

Objectives Upon completion of this laboratory exercise, you should be able to:

- Configure a NAND or NOR gate to act as an inverter.
- Expand an AND, OR, NAND, or NOR gate from a 2-input to a 3-input gate.
- Draw a logic diagram that conforms to standard digital design practice.
- Obtain the truth tables of each gate to be tested.

Reference Ken Reid and Robert Dueck, *Introduction to Digital Electronics*
Chapter 2: Logic Functions and Gates

Equipment Required Digital trainer
Wire strippers
#22 solid-core wire, as required
Components as follows:

Part No.	Qty.	Description
74LS00 or 74HC00	1	Quad 2-input NAND gate
74LS02 or 74HC02	1	Quad 2-input NOR gate
74LS32 or 74HC32	1	Quad 2-input OR gate

Experimental Notes

When using more than one logic gate in a circuit, it is a good practice to draw a **logic diagram**, such as the one shown in Figure 4.1. Such a diagram simplifies the process of troubleshooting and allows for neat documentation of the circuit.

Figure 4.1 shows several characteristics of a good logic diagram. A logic diagram shows all connections between logic elements (the two AND gates), but may omit symbols for input devices, such as logic switches; output devices, such as LEDs; or power and ground connections of the chip.

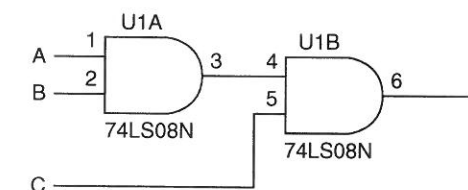


Figure 4.1 Logic Diagram Showing Two Gates from the Same Chip