

HW 28 to 34

28- 1. A 56 ohm resistor is in series with a 220 ohm inductor. The source is  $V = 6 \angle 0^\circ$  degrees. Find  $Z_T$  and  $I$ .

28- 2. A 2 Kohm resistor is in series with a 3 Kohm capacitor. The source is  $V = 10 \angle 0^\circ$  degrees. Find  $Z_T$  and  $I$ .

29- Given an R-L circuit with  $R = 15$  ohms,  $X_L = 7$  ohms, and  $E = 2$  KV  $\angle 0^\circ$  degrees, find;  $I$ ,  $P$ ,  $Q$ ,  $S$ ,  $F_p$  and sketch the impedance and power triangles.

30- A machine is rated at 56 KVA, 0.88 power factor and 760 V. Find the current, and real power in watts.

31- Given an AC machine with the following ratings;  $S = 95$  KVA,  $F_p = 0.85$ ,  $E = 760$  V, Find 1.  $Q_c$  to correct the power factor, 2.  $X_c$  3.  $C$  4.  $I$  uncompensated 5.  $I$  compensated