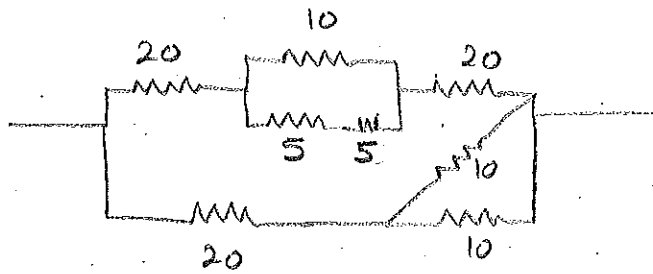



I Find Req.

DUE TUESDAY MAY


Set I



a-

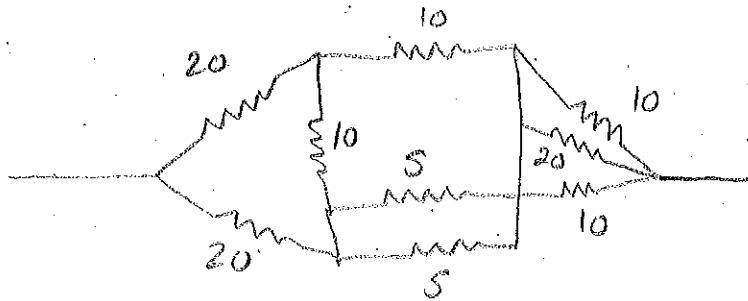


b-

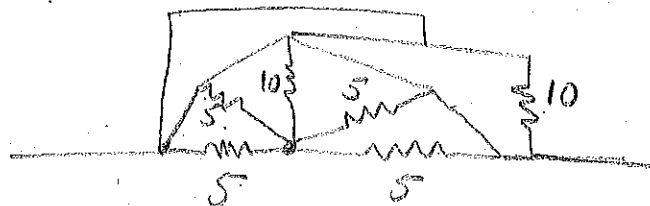


c-

II Find the time constant of the following.

a -

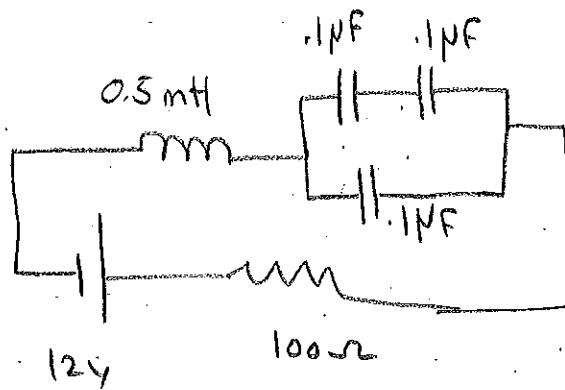

b -

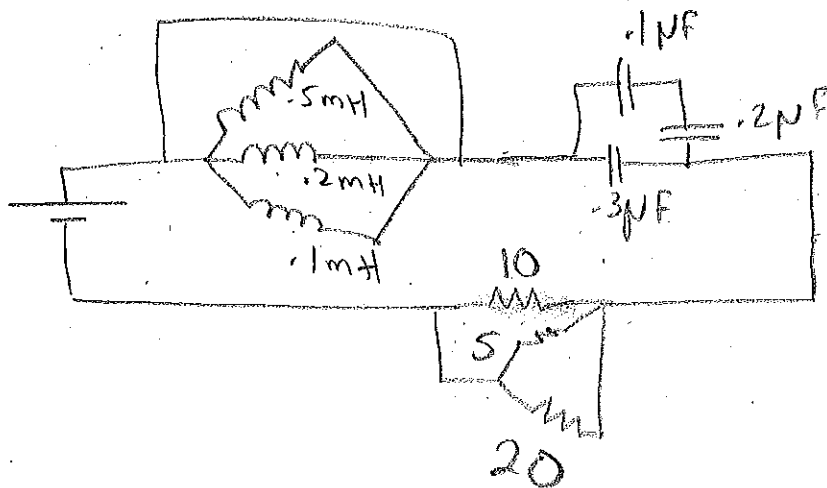

III what are the voltages across L_1 and R_1 ? Show your work. Use $t = 0.1 \text{ sec}$.

