

Discussion Questions—Make sure you answer the following questions in your discussion.

1. Report the measured values of β .
2. Graph I_C vs. V_{CE} .
3. Identify the cutoff, active, and saturation regions of the characteristic curve.
4. Using your data, explain what happens to the collector current when the base current is increased? What happens when the base current is decreased?