

1. For the system shown in Figure 1, Find $|V_{a'b'}|$, $|I_b|$, and $S^{3\phi}_{load}$.

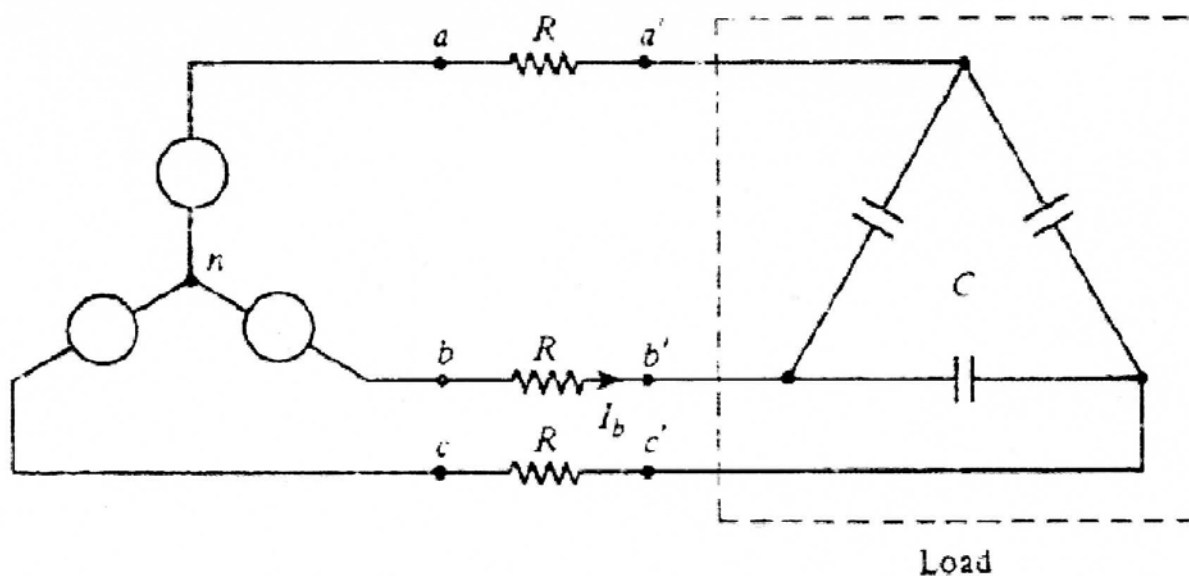


Figure 1

2. For the circuit shown in Figure 2 where $Z_s = 2 \angle 84^\circ$ and $Z_L = 50 \angle 60^\circ$, using the per unit diagrams find the per unit load voltage, current, and complex power for both cases and then convert them to actual values for:
- $V_B = 1000 \text{ V}$, $S_B = 100 \text{ kVA}$
 - $V_B = 1320 \text{ V}$, $S_B = 50 \text{ kVA}$

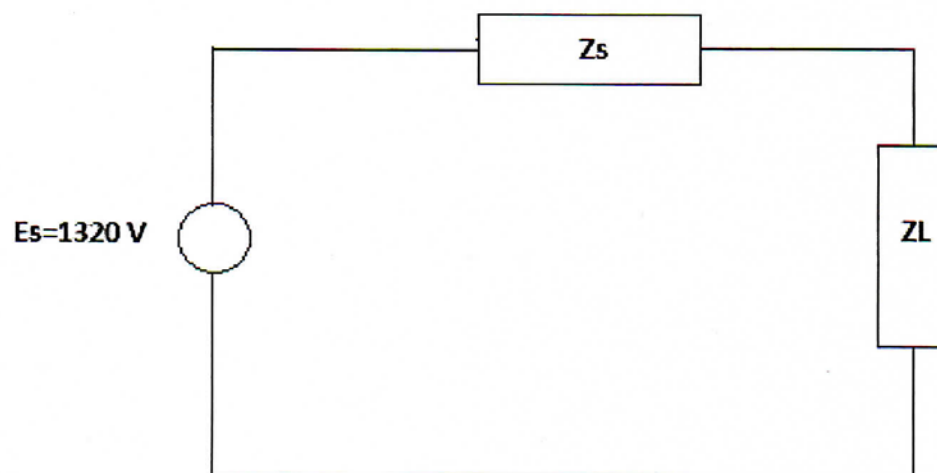


Figure 2

3. Three single-phase two winding transformer, each rated at 10 MVA, 66.4/12.5 KV, 60 Hz, with an equivalent series reactance of 0.12 are connected to form a three-phase bank. The High-Voltage side windings are connected in Y. A three-phase load operating under balanced condition on the high-voltage side receives 450 MVA at p.f. 0.6 lagging, with $V_{AN} = 66 \angle 0^\circ$ KV. Determine the voltage V_{an} at the low-voltage side if the low-voltage winding are connected

- a) In Y
- b) In Δ

The base quantities of the transformer are:

$$S_{base3\phi} = 600 \text{ MVA},$$
$$V_{baseLL} = 175 \text{ KV},$$