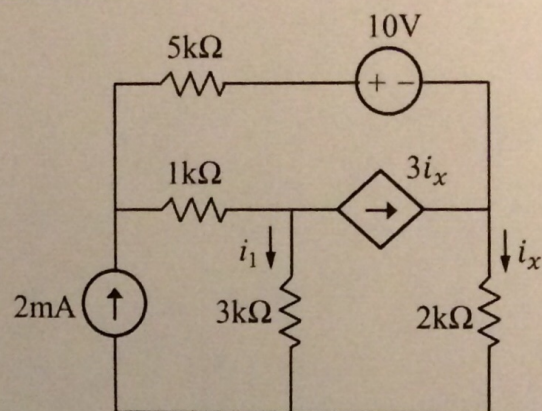



3. (25 points) Find the current  $i_1$  in the circuit using mesh analysis.



Show your work clearly and box your final answers with proper units for full credit.


**Part 3: Problems.** Show your work clearly and box your final answers with proper units for full credit.

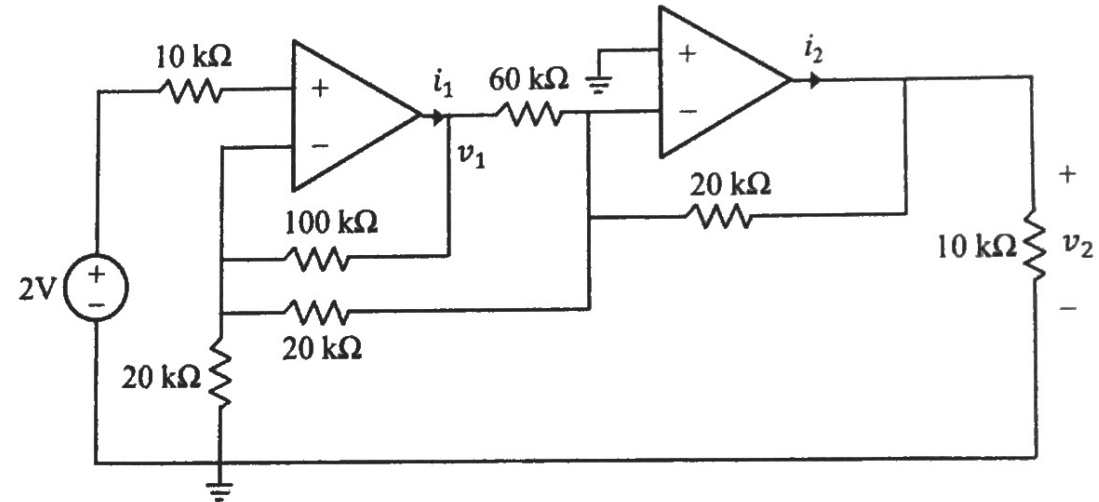1. (25 points) Assuming ideal op amps, determine  $v_1$ ,  $v_2$ ,  $i_1$ , and  $i_2$  in the circuit below.






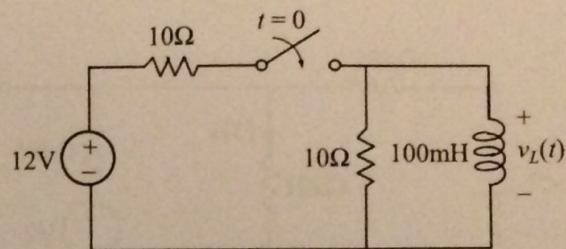2. (25 points) The switch has been open a long time. At  $t = 0$ , the switch closes. Find  $v_L(t)$  for  $t > 0$ .





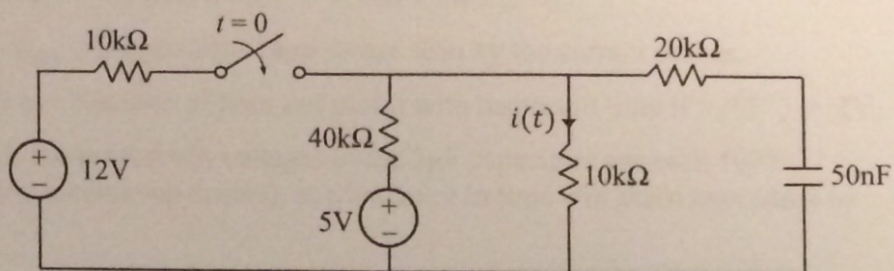3. (25 points) The switch has been open a long time. At  $t = 0$ , the switch closes. Find  $i(t)$  for  $t < 0$  and  $t > 0$ .





4. **(25 points)** Consider the network of capacitors connected to the current source that is turned on at  $t = 0$  ( $u(t)$  is the unit step function, which is 0 for  $t < 0$ , and 1 for  $t \geq 0$ ).

- (10 points)** Determine  $C_{ab}$ , the equivalent capacitance seen by the current source.
- (10 points)** Find  $v_C(t)$  as a function of time and plot it with respect to time if  $v_C(0^-) = 2V$ ,
- (BONUS: +2 points)** If the breakdown voltages of the  $2\mu F$  capacitors are each 100V (beyond which dielectric breakdown occurs), at what point in time will these capacitors be damaged?

